

Lecture
0_2.2

Boolean Primitives and Logic Gates

Test Group



Paolo PRINETTO
Politecnico di Torino (Italy)
University of Illinois at Chicago, IL (USA)

Paolo.Prinetto@polito.it

prinetto@uic.edu

www.testgroup.polito.it

www.comitato-girotondo.org

License Information

**This work is licensed under the
Creative Commons BY-NC
License**



To view a copy of the license, visit:
<http://creativecommons.org/licenses/by-nc/3.0/legalcode>

Disclaimer

- **We disclaim any warranties or representations as to the accuracy or completeness of this material.**
- **Materials are provided “as is” without warranty of any kind, either express or implied, including without limitation, warranties of merchantability, fitness for a particular purpose, and non-infringement.**
- **Under no circumstances shall we be liable for any loss, damage, liability or expense incurred or suffered which is claimed to have resulted from use of this material.**

Goal

- This lecture presents the so called *Basic Boolean Functions*, often referred to as *Boolean Primitives*, and their corresponding *Logic Gates*.

Prerequisites

- **Lecture 0_2.1**

Homework

- **None**

Further readings

- No peculiar hint

Outline

- Basic Boolean Functions:
 - . not
 - . and
 - . or
 - . nand
 - . nor
 - . exor
 - . exnor
- Complete sets of logic primitives

Outline

- Basic Boolean Functions:

- . not
- . and
- . or
- . nand
- . nor
- . exor
- . exnor

- Complete sets of logic primitives

Basic Boolean Functions

- Several “Basic” Boolean Functions, often referred to as Boolean Primitives, have been defined, each identified by a unique name, become a world-wide *de-facto* standard.

They include:

- . *not*
- . *and*
- . *or*
- . *nand*
- . *nor*
- . *exor*
- . *exnor*

Why are they so significant?

- Electronic devices (often referred to as *Logic Gates*) are available to implement each of these basic boolean functions
- Each device is usually given the same name of the corresponding boolean functions, e.g.:

AND function \Leftrightarrow *AND gate*

Outline

- Basic Boolean Functions:

- . not
- . and
- . or
- . nand
- . nor
- . exor
- . exnor

- Complete sets of logic primitives

“Logic Complement” or “NOT” function

Informal definition

It's a unary function, providing the *logic complement* of its input variable.

Representations

x' \bar{x} $\text{not}(x)$

“not” (cont'd)

Axiomatic definition

$$\begin{array}{ll} 0' = 1 & \text{not}(0) = 1 \\ 1' = 0 & \text{not}(1) = 0 \end{array}$$

Truth table

x	not(x)
0	1
1	0

“not” (cont'd)


Functional definition

```
if x = 1 then not(x) = 0  
else not(x) = 1
```

Theorems

$$(x')' = x \quad \text{not (not (x))} = x$$

NOT gate, or inverter

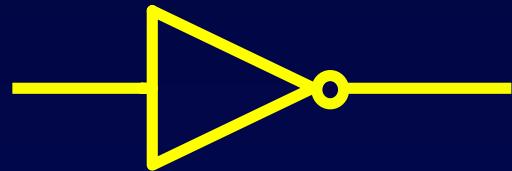

traditional symbol



IEEE symbol

[ANSI/IEEE standard STD 91-1984
“Graphics symbols for logic functions”]

Outline

- Basic Boolean Functions:
 - . not
 - . and
 - . or
 - . nand
 - . nor
 - . exor
 - . exnor
- Complete sets of logic primitives

“Logic product” or “AND” function

Informal definition

The AND function on 2 (or more) input variables provides the value 1 iff all its input variables get the value 1.

Representations

$x \cdot y$

$x \ y$

and (x, y)

“and” (cont'd)

Axiomatic definition

$$0 \cdot 0 = 0 \quad \text{and}(0,0) = 0$$

$$0 \cdot 1 = 0 \quad \text{and}(0,1) = 0$$


$$1 \cdot 0 = 0 \quad \text{and}(1,0) = 0$$

$$1 \cdot 1 = 1 \quad \text{and}(1,1) = 1$$

Truth table

x	y	and(x,y)
0	0	0
0	1	0
1	0	0
1	1	1

Karnaugh map

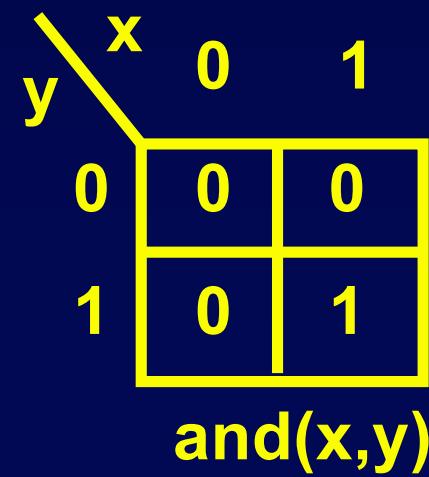

“and” (cont'd)

Functional representation

```
if x = 1 then and(x,y) = y  
else and(x,y) = 0
```

“and” (cont'd)

Theorems

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$


$$x \cdot x = x$$

$$x \cdot x' = 0$$


$$x \cdot y = y \cdot x$$

$$x \cdot y \cdot z = (x \cdot y) \cdot z = x \cdot (y \cdot z)$$

AND gate

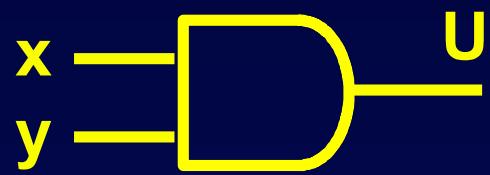

traditional symbol

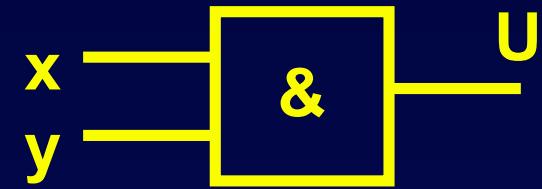

IEEE symbol

Outline

- Basic Boolean Functions:
 - . not
 - . and
 - . or
 - . nand
 - . nor
 - . exor
 - . exnor
- Complete sets of logic primitives

“Logic sum” or “OR” function

Informal definition

The OR function on 2 (or more) input variables provides the value 1 iff *at least one* of its input variables get the value 1.

Representations

$$x + y \quad \text{or} \quad (x, y)$$

8. A logician's wife is having a baby. The doctor immediately hands the newborn to the dad.

His wife asks impatiently: "So, is it a boy or a girl" ?

The logician replies: "yes".

“or” (cont'd)

Functional representation

```
if x = 1 then or(x,y) = 1  
else or(x,y) = y
```

“or” (cont'd)

Axiomatic definition

$$0 + 0 = 0 \quad \text{or}(0,0) = 0$$

$$0 + 1 = 1 \quad \text{or}(0,1) = 1$$


$$1 + 0 = 1 \quad \text{or}(1,0) = 1$$

$$1 + 1 = 1 \quad \text{or}(1,1) = 1$$

Truth table

x	y	or(x,y)
0	0	0
0	1	1
1	0	1
1	1	1

Karnaugh map

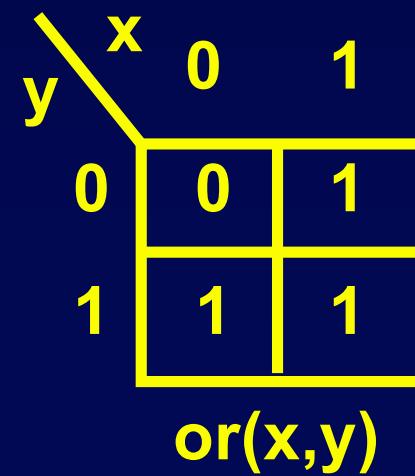

“or” (*cont'd*)

Theorems

$$x + 0 = x$$

$$x + 1 = 1$$


$$x + x = x$$

$$x + x' = 1$$


$$x + y = y + x$$

$$x + y + z = (x + y) + z = x + (y + z)$$

OR gate

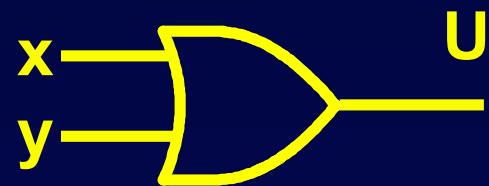

traditional symbol

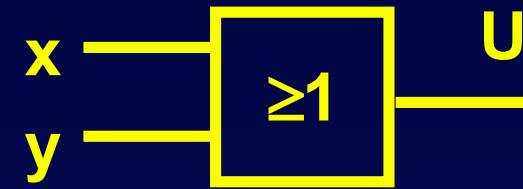

IEEE symbol

Outline

- Basic Boolean Functions:
 - . not
 - . and
 - . or
 - . nand
 - . nor
 - . exor
 - . exnor
- Complete sets of logic primitives

“NAND” function

Informal definition

The NAND function on 2 (or more) input variables provides the value 1 iff *at least one* of its input variables get the value 0.

Representations

$\text{nand} (x, y)$

“nand” (cont'd)

Axiomatic definition

$$\text{nand}(0,0) = 1$$

$$\text{nand}(0,1) = 1$$


$$\text{nand}(1,0) = 1$$

$$\text{nand}(1,1) = 0$$

Truth table

x	y	nand(x,y)
0	0	1
0	1	1
1	0	1
1	1	0

Karnaugh map

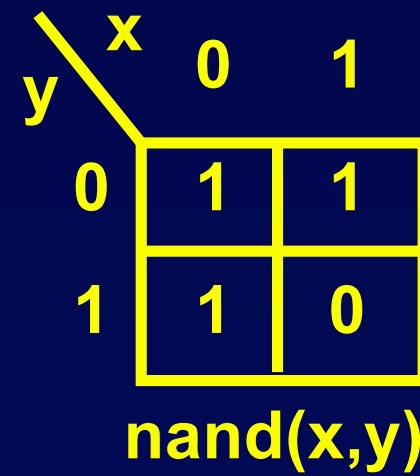

“nand” (cont'd)

Functional representation

```
if x = 1 then nand(x,y) = not(y)  
else nand(x,y) = 1
```

“nand” (cont'd)

Theorems

$$\text{nand}(x, 0) = 1$$

$$\text{nand}(x, 1) = x'$$

$$\text{nand}(x, x) = x'$$

$$\text{nand}(x, x') = 1$$


$$\text{nand}(x, y) = \text{nand}(y, x)$$

$$\text{nand}(x, y) = \text{not}(\text{and}(x, y))$$


$$\text{nand}(x, y, z) = \text{nand}(x, \text{and}(y, z)) =$$

$$= \text{nand}(\text{and}(x, y), z) = \text{nand}(x, \text{and}(y, z))$$

NAND gate

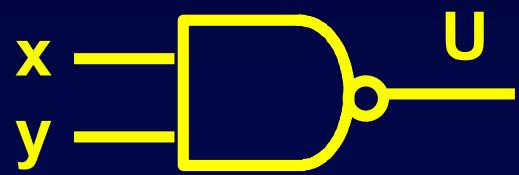

traditional symbol

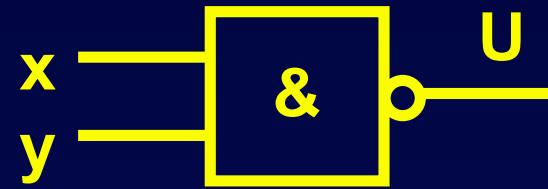

IEEE symbol

Outline

- Basic Boolean Functions:
 - . not
 - . and
 - . or
 - . nand
 - . nor
 - . exor
 - . exnor
- Complete sets of logic primitives

“NOR” function

Informal definition

The NOR function on 2 (or more) input variables provides the value 1 iff *none* of its input variables get the value 1.

Representations

nor (x, y)

“nor” (cont'd)

Axiomatic definition

$$\text{nor}(0,0) = 1$$

$$\text{nor}(0,1) = 0$$


$$\text{nor}(1,0) = 0$$

$$\text{nor}(1,1) = 0$$

Truth table

x	y	$\text{nor}(x,y)$
0	0	1
0	1	0
1	0	0
1	1	0

Karnaugh map

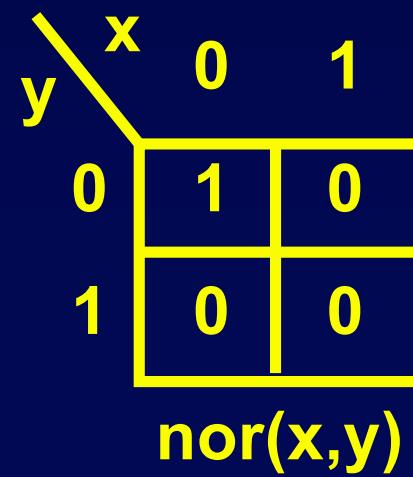

“nor” (cont'd)

Functional representation

```
if x = 1 then nor(x,y) = 0  
else nor(x,y) = not(y)
```

“nor” (cont'd)

Theorems

$$\text{nor}(x, 0) = x'$$

$$\text{nor}(x, 1) = 0$$

$$\text{nor}(x, x) = x'$$

$$\text{nor}(x, x') = 0$$


$$\text{nor}(x, y) = \text{nor}(y, x)$$

$$\text{nor}(x, y) = \text{not}(\text{or}(x, y))$$


$$\text{nor}(x, y, z) = \text{nor}(x, \text{or}(y, z)) =$$

$$= \text{nor}(\text{or}(x, y), z) = \text{nor}(x, \text{or}(y, z))$$

NOR gate

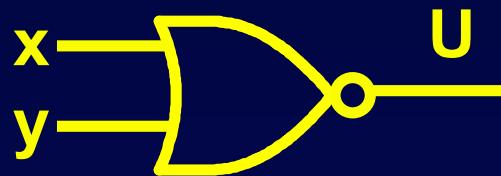

traditional symbol

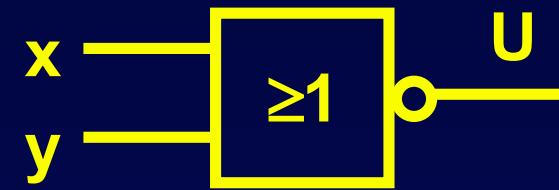

IEEE symbol

Outline

- Basic Boolean Functions:
 - . not
 - . and
 - . or
 - . nand
 - . nor
 - . exor
 - . exnor
- Complete sets of logic primitives

“Exclusive OR” (or “EXOR” function)

Informal definition

The EXOR function on 2 (or more) input variables provides the value 1 iff *an odd #* of its input variables get the value 1.

Representations

$x \oplus y$

exor (x, y)

xor (x, y)

“exor” (cont'd)

Axiomatic definition

$$0 \oplus 0 = 0$$

$$0 \oplus 1 = 1$$


$$1 \oplus 0 = 1$$

$$1 \oplus 1 = 0$$


Truth table

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0


Karnaugh map

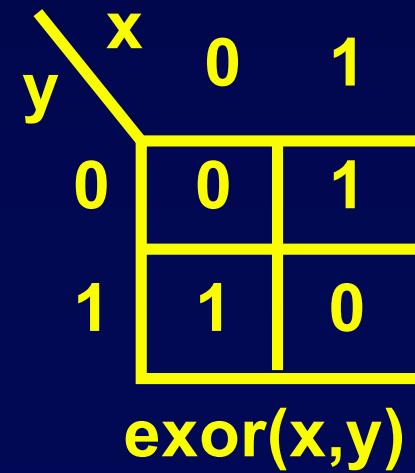

EXOR gate

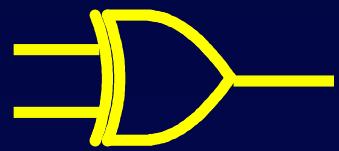

traditional symbol

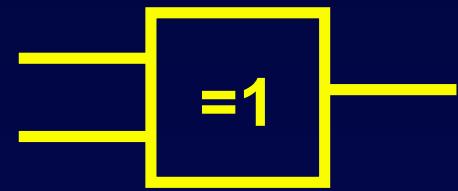

IEEE symbol

“exor” (cont'd)

1st functional representation

```
if x = 1 then exor(x,y) = not(y)  
else exor(x,y) = y
```

The exor function can be seen as a
controlled inverter :

x	y	exor(x,y)
0	0	0
0	1	1
1	0	1
1	1	0

“exor” (cont'd)

2nd functional representation

```
if x = y then exor(x,y) = 0  
else exor(x,y) = 1
```

The exor function can be seen as a
comparator :

x	y	exor(x,y)
0	0	0
1	1	0
1	0	1
0	1	1

“exor” (cont'd)

3rd functional representation

if $(x+y) \bmod 2 = 0$ then $\text{exor}(x,y) = 0$
else $\text{exor}(x,y) = 1$

The exor function can be seen as a
modulo 2 adder

x	y	$(x+y) \bmod 2$	$\text{exor}(x,y)$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

Exor - Theorems

$$\text{exor}(x, 0) = x$$

$$\text{exor}(x, 1) = x'$$

$$\text{exor}(x, x) = 0$$

$$\text{exor}(x, x') = 1$$

$$\text{exor}(x, y) = \text{exor}(y, x)$$

$$\text{exor}(x, y) = \text{exor}(x', y')$$

$$\text{exor}(x, y') = \text{exor}(x', y) = \text{not}(\text{exor}(x, y))$$

$$\text{exor}(x, y) = xy' + x'y = (xy)'(x + y)$$

Exor - Composition

$$\begin{aligned}\text{exor}(x, y, z) &= \text{exor}(x, \text{exor}(y, z)) \\ &= \text{exor}(\text{exor}(x, y), z)\end{aligned}$$


Exor - Composition

$$\begin{aligned}\text{exor}(x, y, z) &= \text{exor}(x, \text{exor}(y, z)) \\ &= \text{exor}(\text{exor}(x, y), z)\end{aligned}$$

Exor - Composition - Remark


When using 2-input exor gates to implement N-input exor functions, 2 solutions are possible:

Exor - Composition – 1st solution

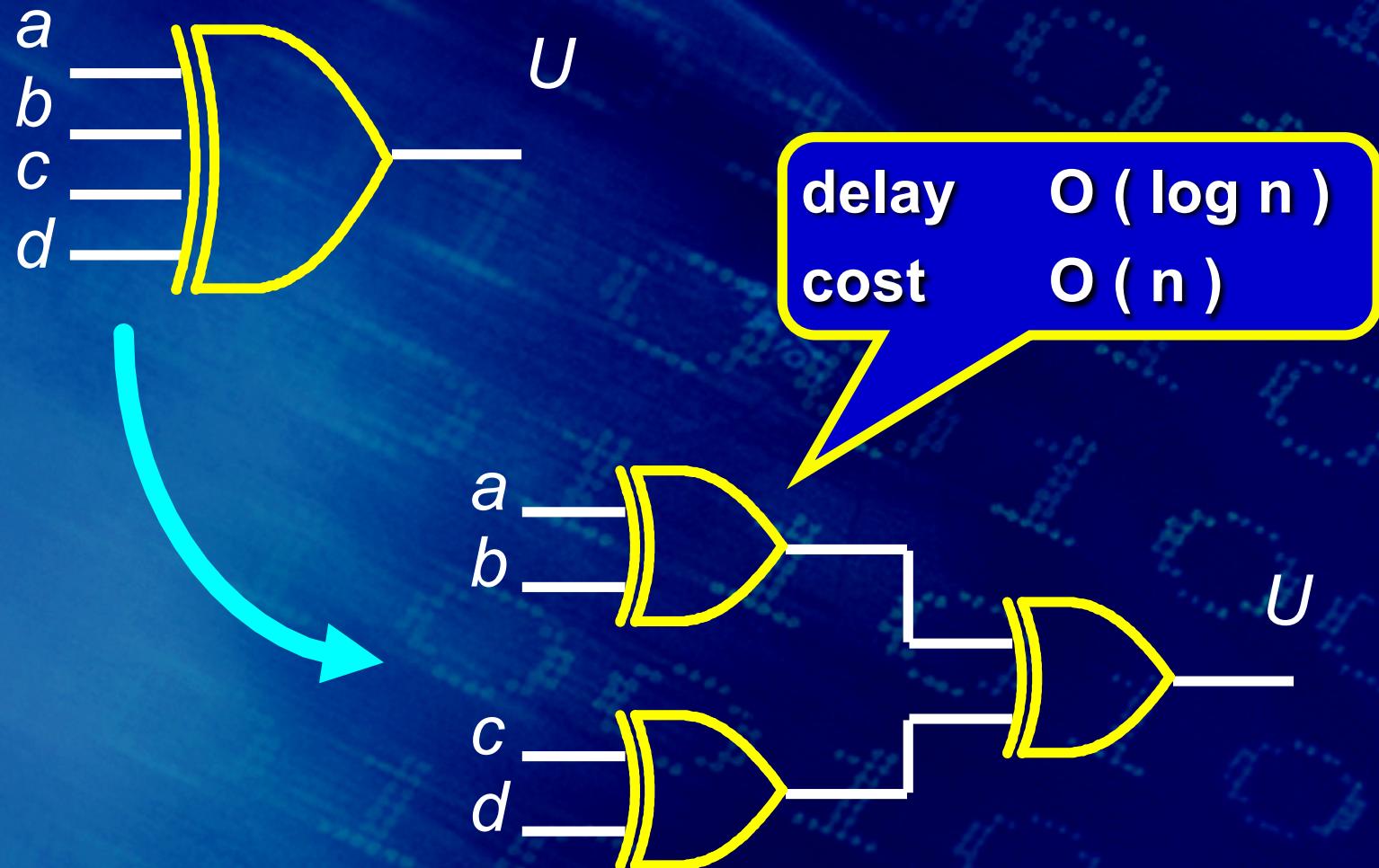


Exor - Composition – 1st solution

Homework:
prove it

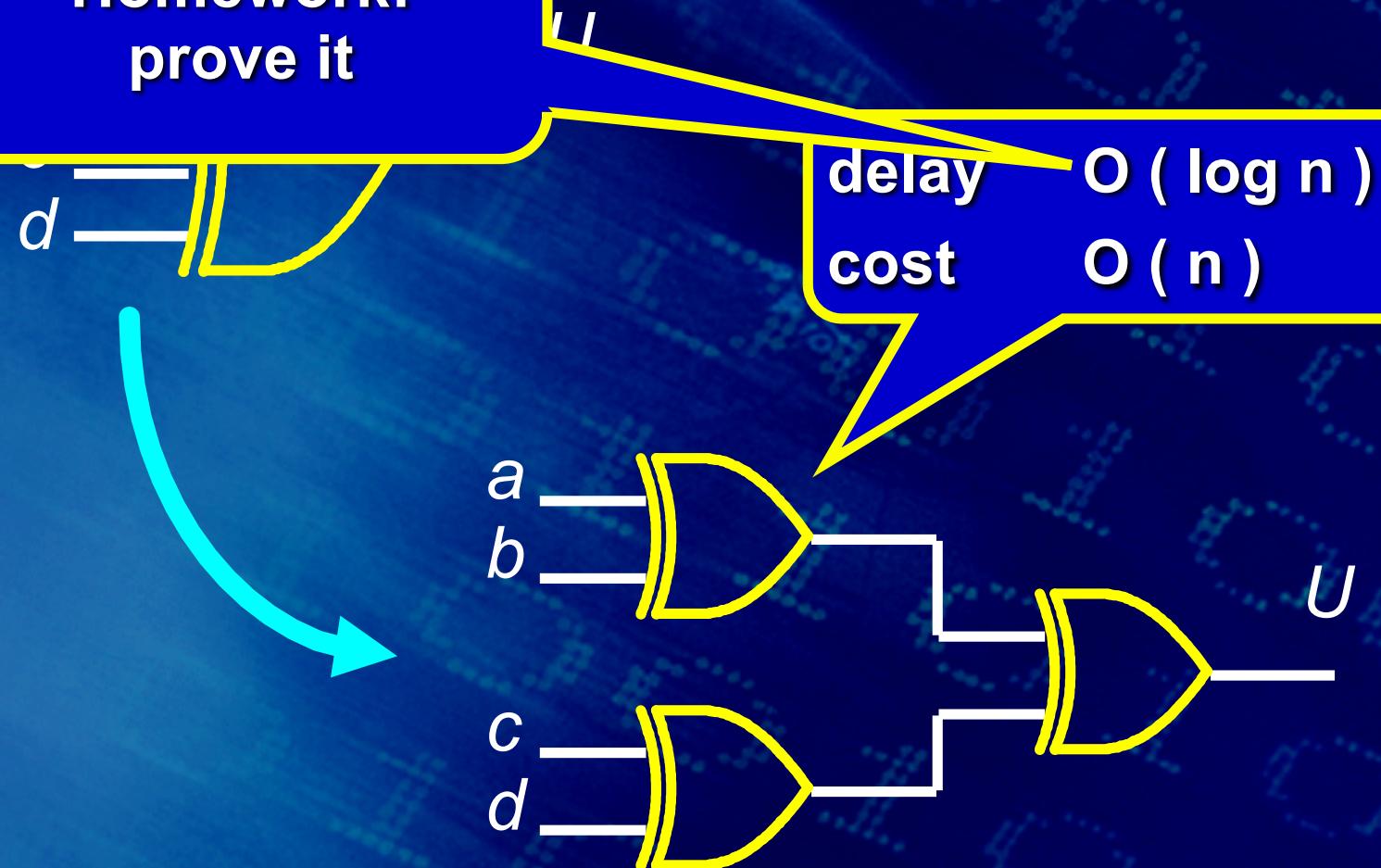

Exor - Composition – 2nd solution

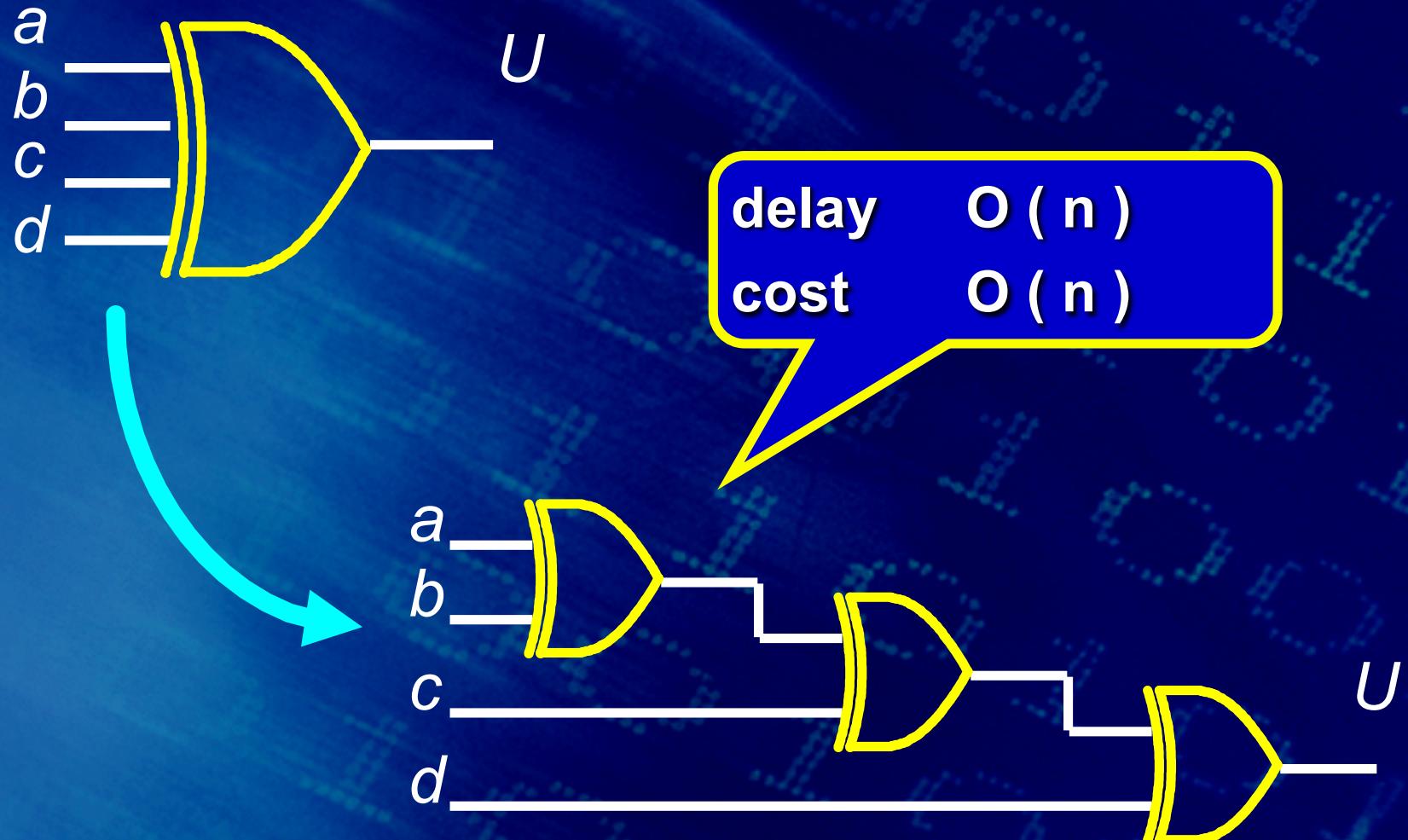

Karnaugh map for a 4-inputs exor

		ab	00	01	11	10
		cd	00	01	11	10
		00	0	1	0	1
		01	1	0	1	0
		11	0	1	0	1
		10	1	0	1	0
exor (a,b,c,d)						

Outline

- Basic Boolean Functions:
 - . not
 - . and
 - . or
 - . nand
 - . nor
 - . exor
 - . exnor
- Complete sets of logic primitives

“EXNOR” function

Informal definition

The EXNOR function on 2 (or more) input variables provides the value 1 iff *an even #* of its input variables get the value 1.

Representations

$x \odot y$

exnor (x, y)

“exnor” (cont'd)

Axiomatic definition

$$\text{exnor}(0,0) = 1$$

$$\text{exnor}(0,1) = 0$$


$$\text{exnor}(1,0) = 0$$

$$\text{exnor}(1,1) = 1$$

Truth table

x	y	exnor(x,y)
0	0	1
0	1	0
1	0	0
1	1	1

Karnaugh map

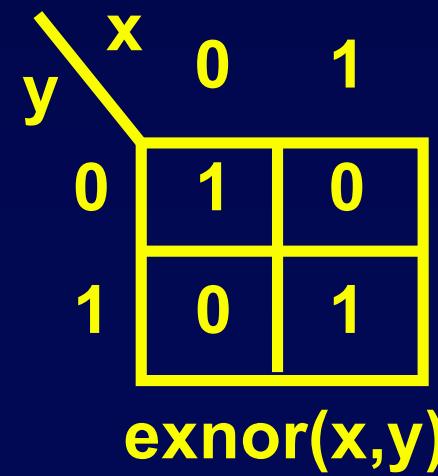

“exnor” (cont'd)

Functional representations

```
if x = 1 then exor(x,y) = y  
else exor(x,y) = not(y)
```

```
if x = y then exor(x,y) = 1  
else exor(x,y) = 0
```

Theorems

$$\begin{aligned}\text{exnor}(x, y) &= \text{exor}(x, y)' = \text{exor}(x', y) = \text{exor}(x, y') \\ \text{exnor}(x, y) &= xy + x'y'\end{aligned}$$

Outline

- Basic Boolean Functions:
 - . not
 - . and
 - . or
 - . nand
 - . nor
 - . exor
 - . exnor
- Complete sets of logic primitives

Complete sets of logic primitives

- **Question:**
 - Is it possible to represent any Boolean Function resorting to a whatever subset of the basic functions (or primitives) seen so far?

Complete sets of logic primitives

- **Question:**
 - Is it possible to represent any Boolean Function resorting to a whatever subset of the basic functions (or primitives) seen so far?
- **Answer:**
 - No: you have to carefully select the subset!

Strongly complete set

- A set of logic primitives is said to be ***strongly complete*** if any arbitrary logic function $f(x_1, x_2, \dots, x_n)$ can be implemented by connecting a finite number of them, assuming the only asserted input variables x_1, x_2, \dots, x_n be available.

Strongly complete set (2)

The definition implies that, in particular, the constant functions:

- $f(x_1, x_2, \dots, x_n) = 1$
- $f(x_1, x_2, \dots, x_n) = 0$

must also be producible.

Examples of Strongly complete sets

- **and, or, not**
- **and, not**
- **or, not**
- **nand**
- **nor**
- ...

Problem

- How determining whether a set of primitives is strongly complete?

Intuitive approach

- Check whether the set one can generate the 3 functions and, or and not.

Example

The set { nand } is strongly complete since:

- $x' = (x \cdot x)'$
- $x \cdot y = ((x \cdot y)')'$
- $x + y = ((x + y)')' = (x' \cdot y')'$
- $1 = (x \cdot x')' = (x \cdot (x \cdot x)')''$
- $0 = ((x \cdot (x \cdot x)') \cdot (x \cdot (x \cdot x)')')'$

Systematic approach

- It resorts to the Theorem of Post.

Function properties

- Some properties need to be preliminarily defined.

Property 1 : Zero Preservation

A boolean function $f(x_1, x_2, \dots, x_n)$ is said to be a ***preserving zero function*** iff

$$f(0, 0, \dots, 0) = 0$$

Property 2 : One Preservation

A boolean function $f(x_1, x_2, \dots, x_n)$ is said to be a *preserving one function* iff

$$f(1, 1, \dots, 1) = 1$$

Property 3 : Self-Duality

A boolean function $f(x_1, x_2, \dots, x_n)$ is said to ***Self-dual*** iff

$$f(x_1, x_2, \dots, x_n) = f'(x_1', x_2', \dots, x_n')$$

Property 4 : Monotonicity

A boolean function $f(x_1, x_2, \dots, x_n)$ is said to *monotonic* iff

$$f(a) \geq f(b) \quad \forall a, b \mid a \geq b$$

Property 5 : Linearity

A boolean function $f(x_1, x_2, \dots, x_n)$ is said to **linear** iff it can be expressed as

$$f(x_1, x_2, \dots, x_n) = a_0 \oplus a_1x_1 \oplus a_2x_2 \oplus \dots \oplus a_nx_n$$

where

$$a_i \in \{ 0,1 \} \quad \text{for } i = 0, 1, 2, \dots, n$$

Theorem

Be $S = \{ f_1, f_2, \dots, f_n \}$ a set of functions, all having one of the 5 previous properties.

Any boolean function obtained combining the functions of S has the same property, i.e., :

- a linear function of linear functions is a linear function
- a monotonic function of monotonic functions is a monotonic function
- ...

Theorem of Post

A set of functions is strongly complete iff it contains:

- ***at least one function not zero preserving***
- ***at least one function not one preserving***
- ***at least one non-self-dual function***
- ***at least one non-linear function***
- ***at least one non-monotonic function.***

Малые Автюхи, Калинковичский район, Республики Беларусь

