

Lecture
0_2.3

From Boolean Functions to Digital Circuits

Test Group



Paolo PRINETTO
Politecnico di Torino (Italy)
University of Illinois at Chicago, IL (USA)

Paolo.Prinetto@polito.it

prinetto@uic.edu

www.testgroup.polito.it

www.comitato-girotondo.org

License Information

**This work is licensed under the
Creative Commons BY-NC
License**



To view a copy of the license, visit:
<http://creativecommons.org/licenses/by-nc/3.0/legalcode>

Disclaimer

- **We disclaim any warranties or representations as to the accuracy or completeness of this material.**
- **Materials are provided “as is” without warranty of any kind, either express or implied, including without limitation, warranties of merchantability, fitness for a particular purpose, and non-infringement.**
- **Under no circumstances shall we be liable for any loss, damage, liability or expense incurred or suffered which is claimed to have resulted from use of this material.**

Goal

- This lecture presents a global overview of how a Boolean Function can be mapped into (implemented by) a digital circuit

Prerequisites

- Lecture 0_2.2

Homework

– None

Outline

- Geometric interpretation of Boolean Algebras
- Values taken by functions
- How representing functions?
- Problems to face
- From functions to circuits
- Remarks
- Lessons learned

Geometric interpretation


The carrier B^n of a Boolean Algebra can be seen as an *n-dimensional space*, where each generic element $v \in B^n$ (usually called a *vertex*), is represented by a vector of n coordinates, each $\in B$

1-input functions

- $B = \{ 0, 1\}$
- B
- $F = F(x)$




2-input functions

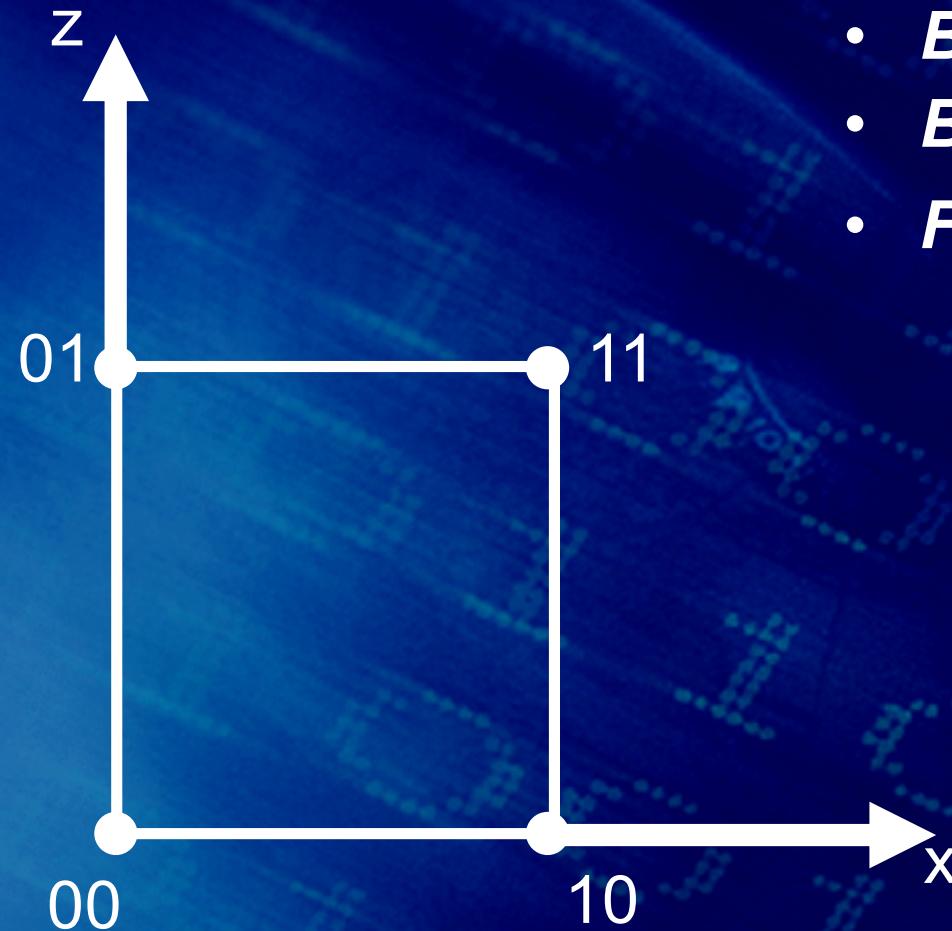


- $B = \{ 0, 1\}$
- B^2
- $F = F(x, z)$

3-input functions

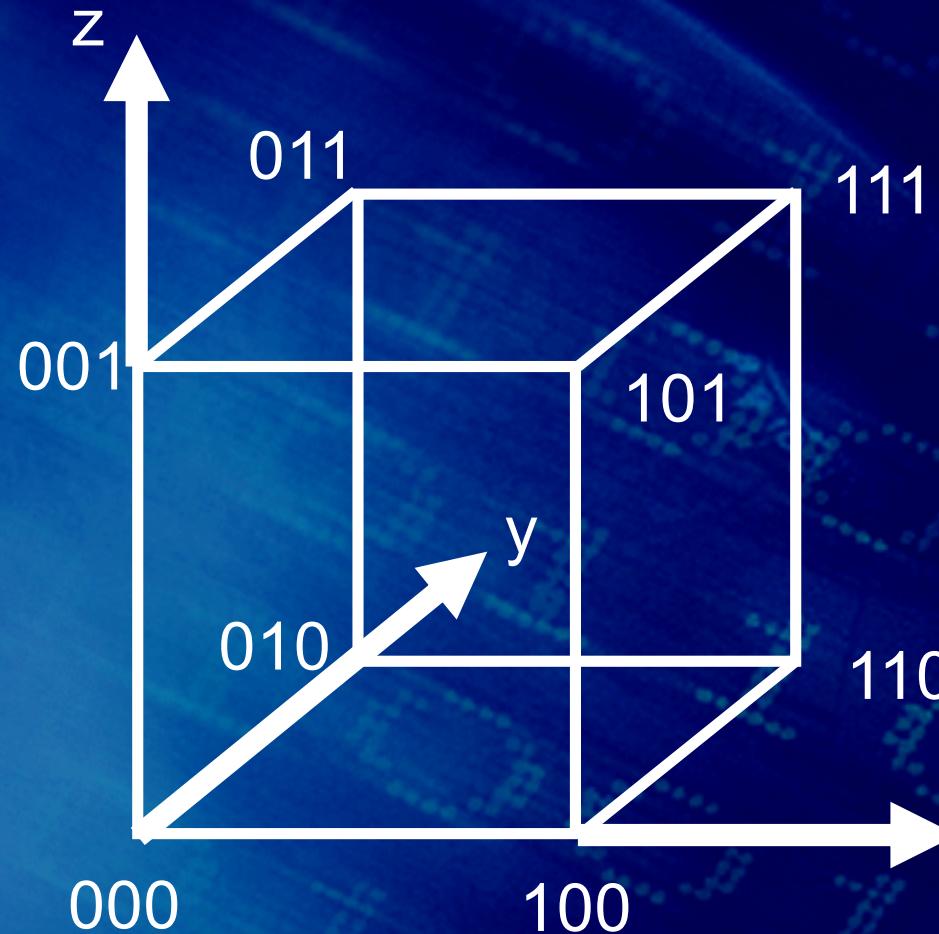

- $B = \{ 0, 1 \}$
- B^3
- $F = F(x, y, z)$

4-input functions

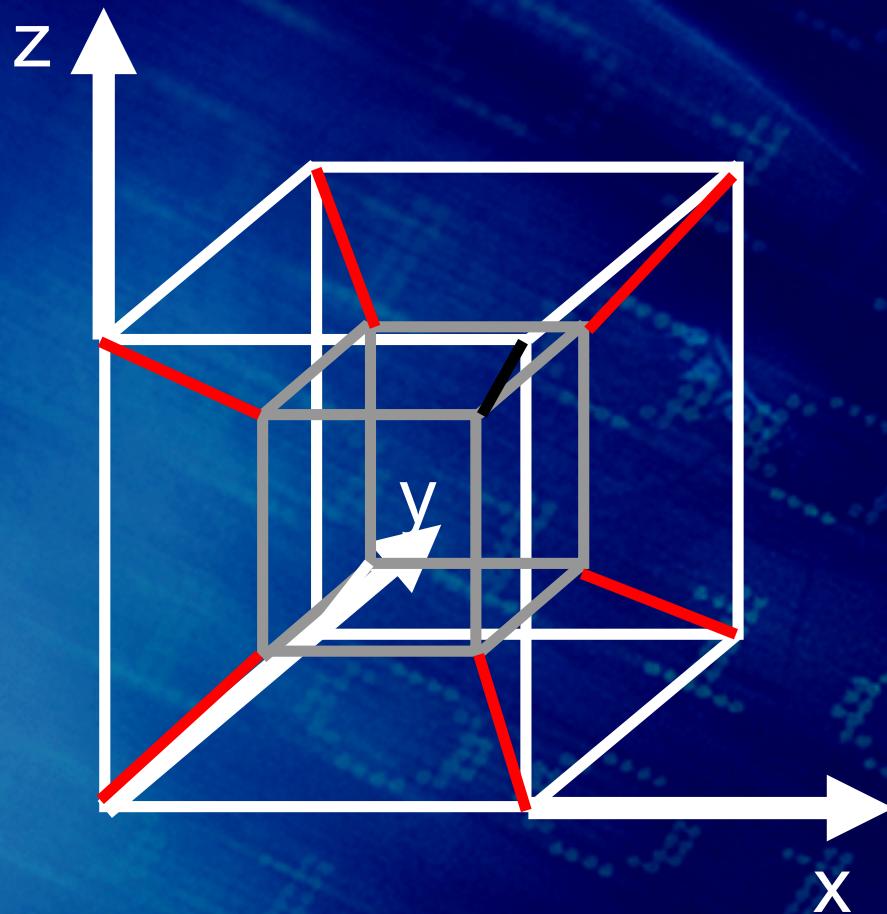

- $B = \{ 0, 1 \}$
- B^4
- $F = F(x, y, z, w)$

Outline

- Boolean Algebras Definitions
- Examples of Boolean Algebras
- Geometric interpretation of Boolean Algebras
- Values taken by functions
- How representing functions?
- Boolean Algebras properties



Values taken by functions

- In general, in each vertex V , a function may:
 - . *get the value 0* $\Rightarrow V \in \text{off-set}$
 - . *get the value 1* $\Rightarrow V \in \text{on-set}$
 - . *be not specified* $\Rightarrow V \in \text{don't-care set}$

Values taken by functions


- In general, in each vertex V , a function may:
 - . *get the value 0* $\Rightarrow V \in \text{off-set}$
 - . *get the value 1* $\Rightarrow V \in \text{on-set}$
 - . *be not specified* $\Rightarrow V \in \text{don't-care set}$

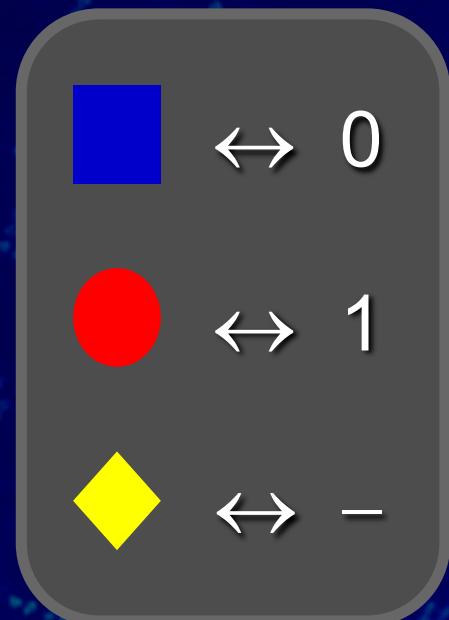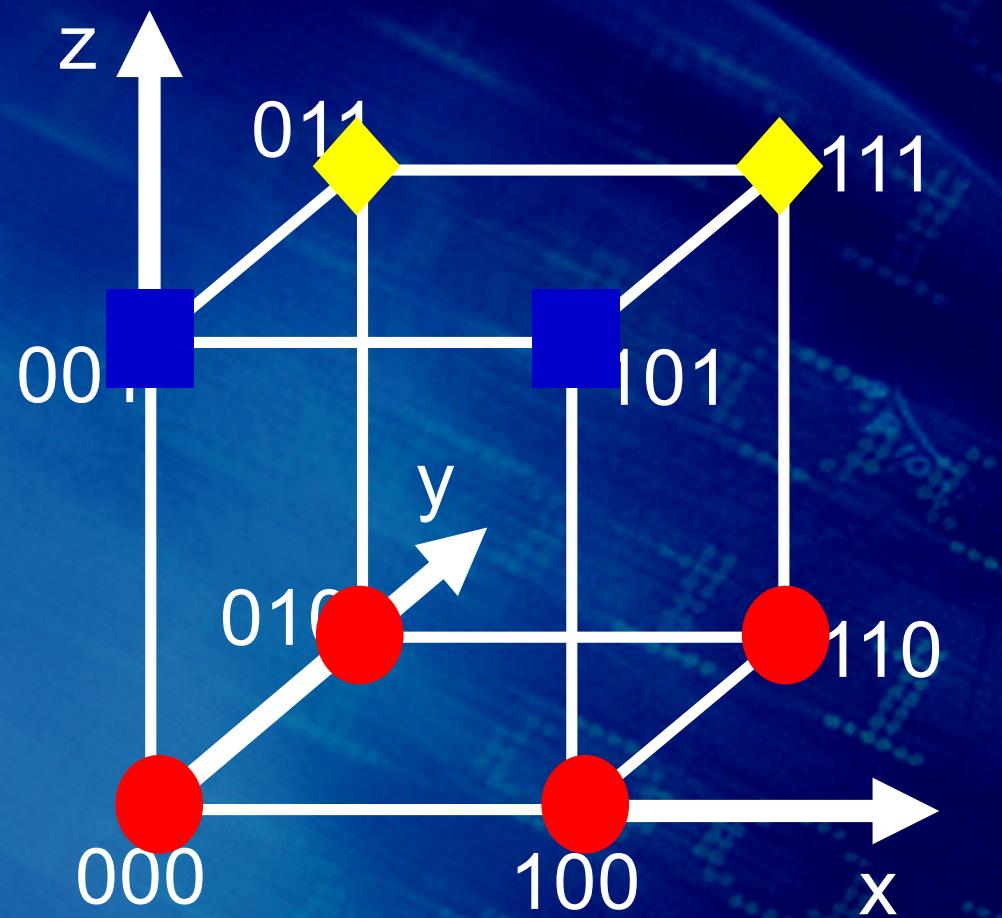Typically used to represent
combinations of input variables
not relevant in a given design




Completely vs. incompletely specified functions

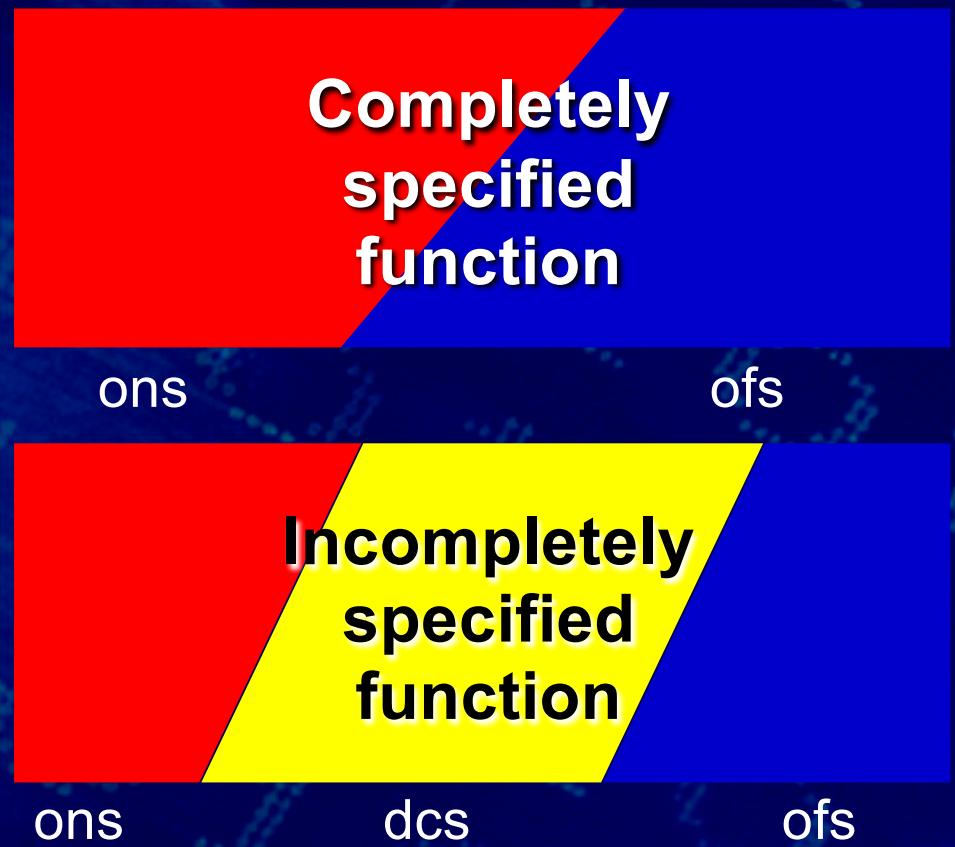- A function f is ***completely specified*** iff $dcs(f) = \emptyset$
- f is ***incompletely specified*** otherwise



Note

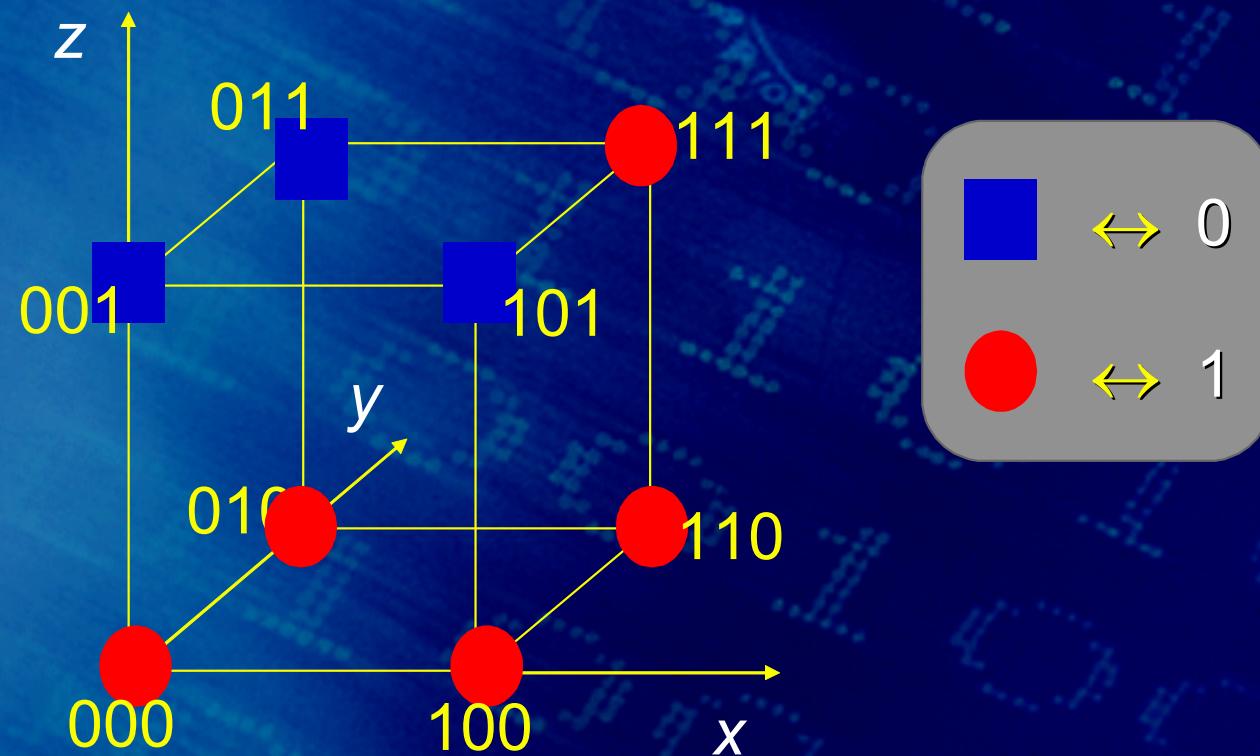- For sake of simplicity, without loosing generality, in the sequel of the lecture we shall use, as a case study, the following completely specified 3-input function $F = F(x, y, z)$:



Outline

- Boolean Algebras Definitions
- Examples of Boolean Algebras
- Geometric interpretation of Boolean Algebras
- Values taken by functions
- How representing functions?
- Boolean Algebras properties


How representing functions?

- We need a way “*to represent*” or “*to express*” the value that the function F gets in each vertex, i.e., in each point of its domain.

Boolean Functions representation

- Boolean Functions are mostly represented by stating their on-set and don't-care set.
- These can, in turn, be represented according to several criteria, each particularly suited for a target application.

An example

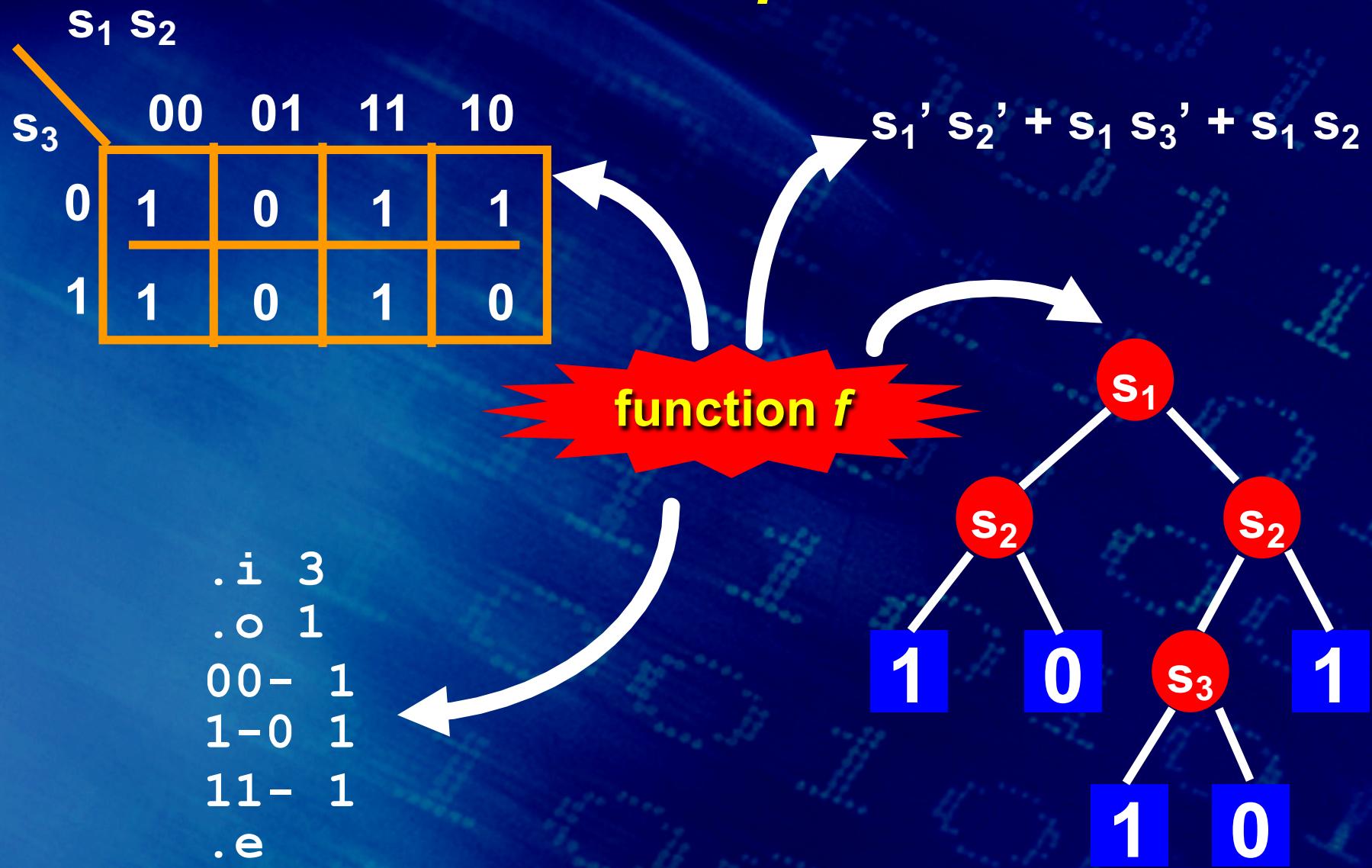

Boolean Functions representation

**Exhaustive
Representations**

**Compact
Representations**

ITE Expressions

Graphs

Boolean Functions representation

**Exhaustive
Representations**

**Compact
Representations**

ITE Expressions


Graphs

An exhaustive approach

- We could explicitly represent the values assumed by the function for each of the possible combinations of the input variables $\Rightarrow 2^n$ entries !!!
- Two alternatives:
 - Tabular representation: *Truth Table*
 - Matrix representation: *Karnaugh maps*

Truth table

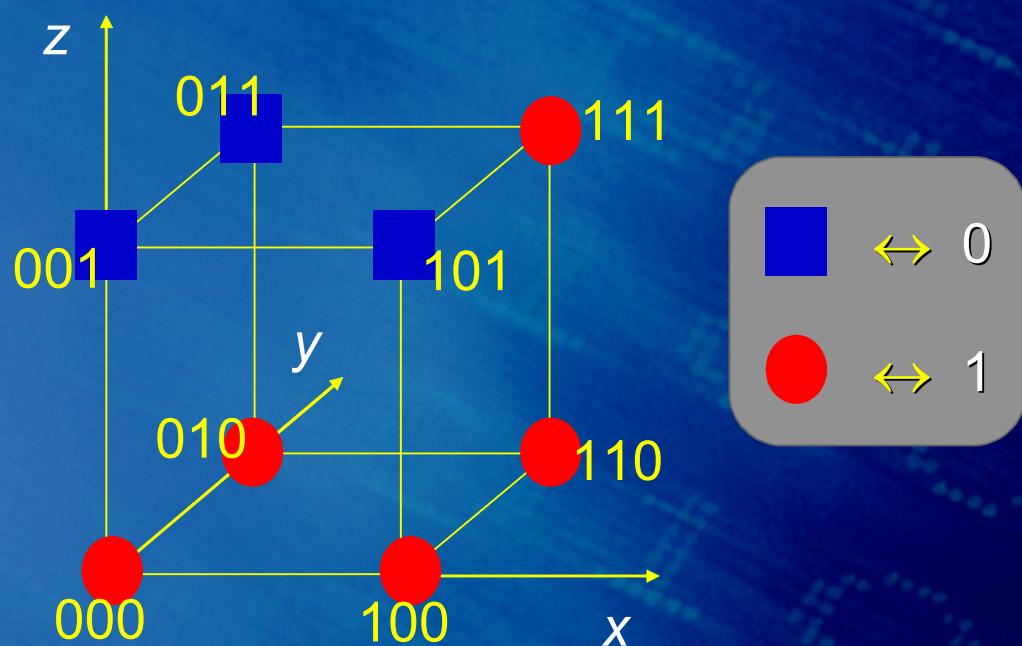- It specifies the value the function gets for each input combination:



x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Usage


- When dealing with few inputs, they can be used to prove theorems
- Sometimes helpful in manual design, as preliminary step to generate the equivalent Karnaugh maps

Karnaugh maps

*Karnaugh maps (**K-map** for short) were first introduced by Maurice Karnaugh in 1953.*

An n input variable boolean function is represented by a matrix of 2^n cells.

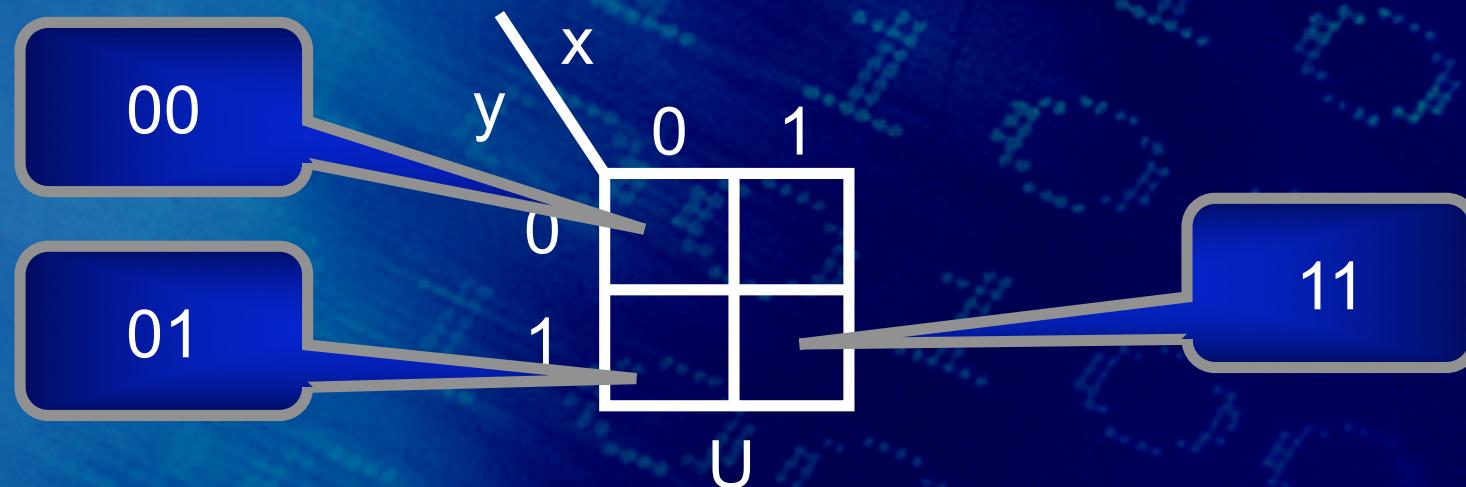Each cell specifies the value of the function when its input variables get the values of the corresponding row and column.



Karnaugh maps

x y z	F
0 0 0	1
0 0 1	0
0 1 0	1
0 1 1	0
1 0 0	1
1 0 1	0
1 1 0	1
1 1 1	1



Boolean Functions representation

**Exhaustive
Representations**


**Compact
Representations**

ITE Expressions

Graphs



An intuitive approach

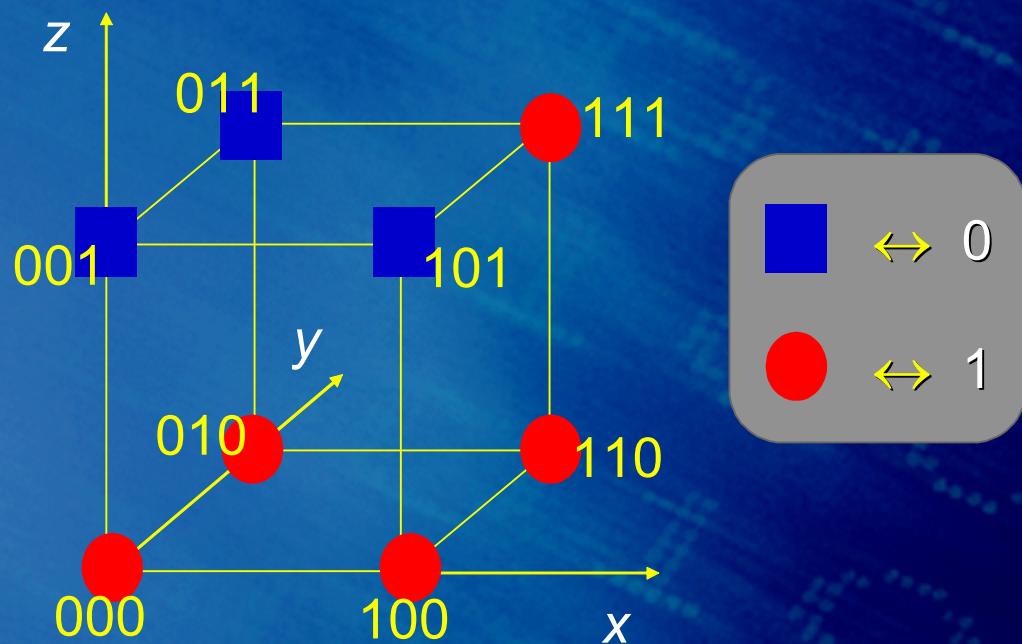
- We could, for instance, deciding of expressing only the vertices in which the function gets the value 1:



An intuitive approach

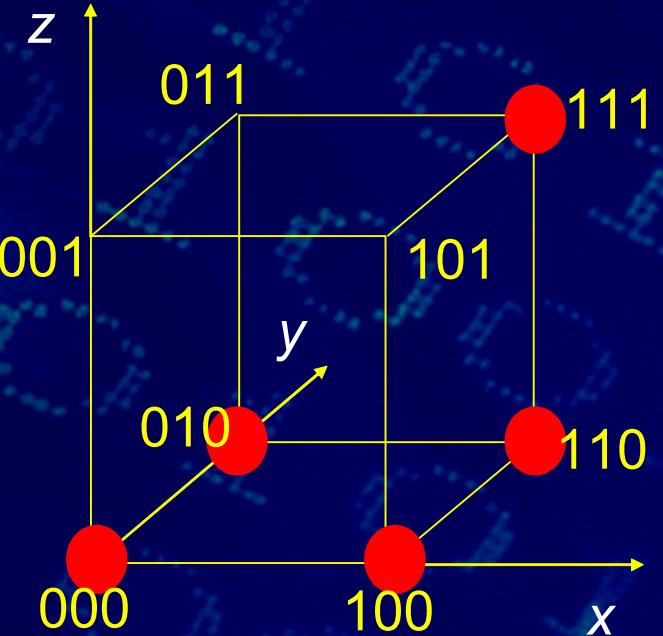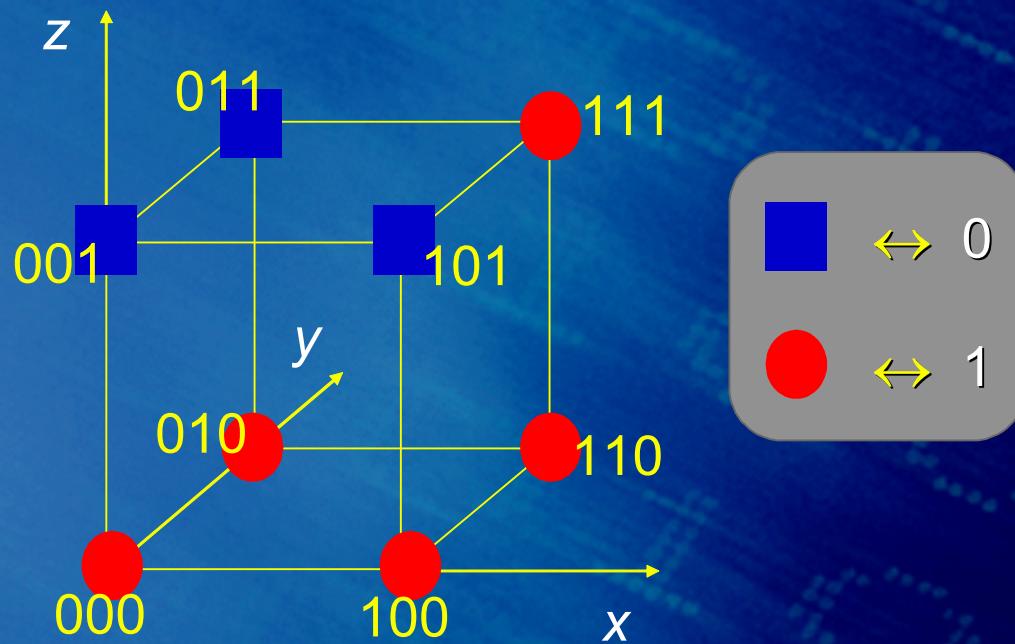
We could, for instance, deciding of expressing only the vertices in which the function gets the value 1:



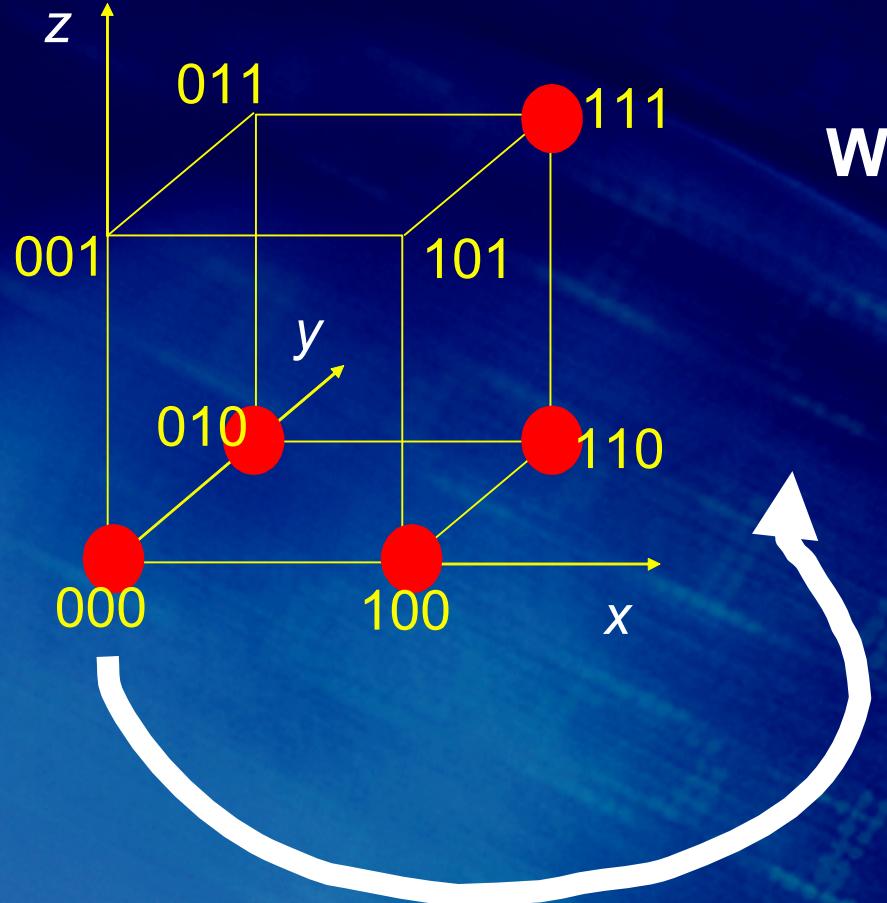

We could write:

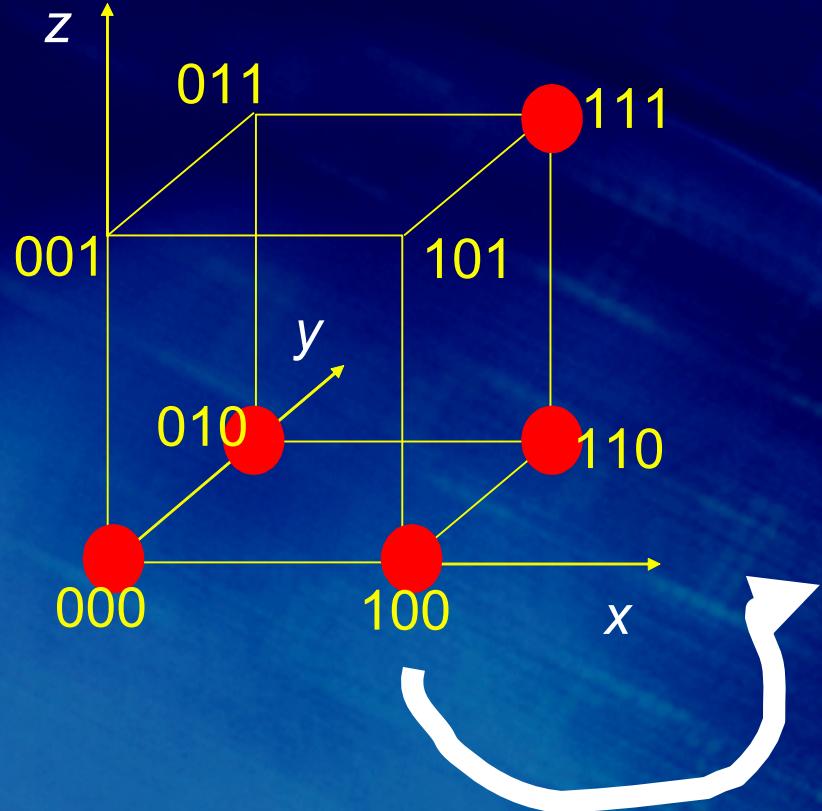$F = 1$ when
 $((x=0) \text{ and } (y=0) \text{ and } (z=0))$




We could write:

$F = 1$ when

($(x=0)$ and $(y=0)$ and $(z=0)$)

or

($(x=1)$ and $(y=0)$ and $(z=0)$)

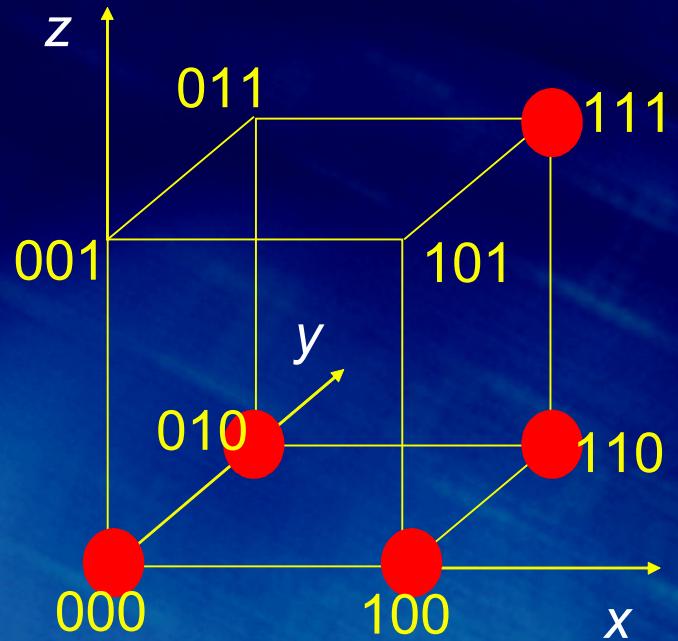

We could write:

$F = 1$ when

($(x=0)$ and $(y=0)$ and $(z=0)$)

or

($(x=1)$ and $(y=0)$ and $(z=0)$)

or



($(x=1)$ and $(y=1)$ and $(z=0)$)

or

($(x=0)$ and $(y=1)$ and $(z=0)$)

or

($(x=1)$ and $(y=1)$ and $(z=1)$).

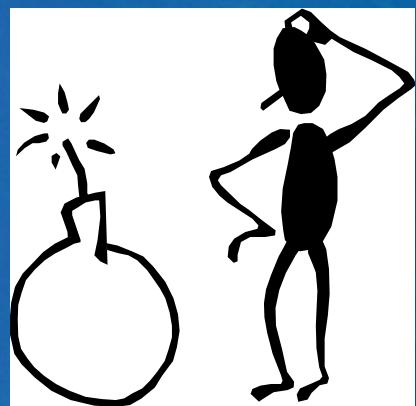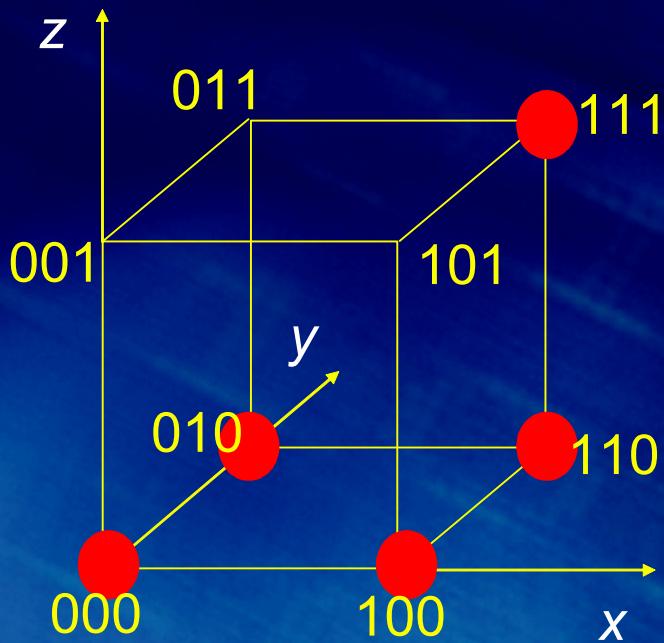

We could write:

$F = 1$ when

($(x=0)$ and $(y=0)$ and $(z=0)$)

or

($(x=1)$ and $(y=0)$ and $(z=0)$)

or

($(x=1)$ and $(y=1)$ and $(z=0)$)

or

($(x=0)$ and $(y=1)$ and $(z=0)$)

or

($(x=1)$ and $(y=1)$ and $(z=1)$).

Let's try to simplify

$(x=1) \rightarrow x$

$(x=0) \rightarrow x'$

and $\rightarrow \cdot \rightarrow$

or $\rightarrow +$

Let's try to simplify

$(x=1) \rightarrow x$

$(x=0) \rightarrow x'$

and $\rightarrow \cdot \rightarrow$

or $\rightarrow +$

$F = 1$ when

$((x=0) \text{ and } (y=0) \text{ and } (z=0)) \text{ or}$

$((x=1) \text{ and } (y=0) \text{ and } (z=0)) \text{ or}$

$((x=1) \text{ and } (y=1) \text{ and } (z=0)) \text{ or}$

$((x=0) \text{ and } (y=1) \text{ and } (z=0)) \text{ or}$

$((x=1) \text{ and } (y=1) \text{ and } (z=1))$

Let's try to simplify

$(x=1) \rightarrow x$

$(x=0) \rightarrow x'$

and $\rightarrow \cdot \rightarrow$

or $\rightarrow +$

$F = 1$ when

$((x=0) \text{ and } (y=0) \text{ and } (z=0)) \text{ or}$

$((x=1) \text{ and } (y=0) \text{ and } (z=0)) \text{ or}$

$((x=1) \text{ and } (y=1) \text{ and } (z=0)) \text{ or}$


$((x=0) \text{ and } (y=1) \text{ and } (z=0)) \text{ or}$

$((x=1) \text{ and } (y=1) \text{ and } (z=1))$

$F =$
 $x'y'z' +$
 $x y'z' +$
 $x y z' +$
 $x'y z' +$
 $x y z$

A further step

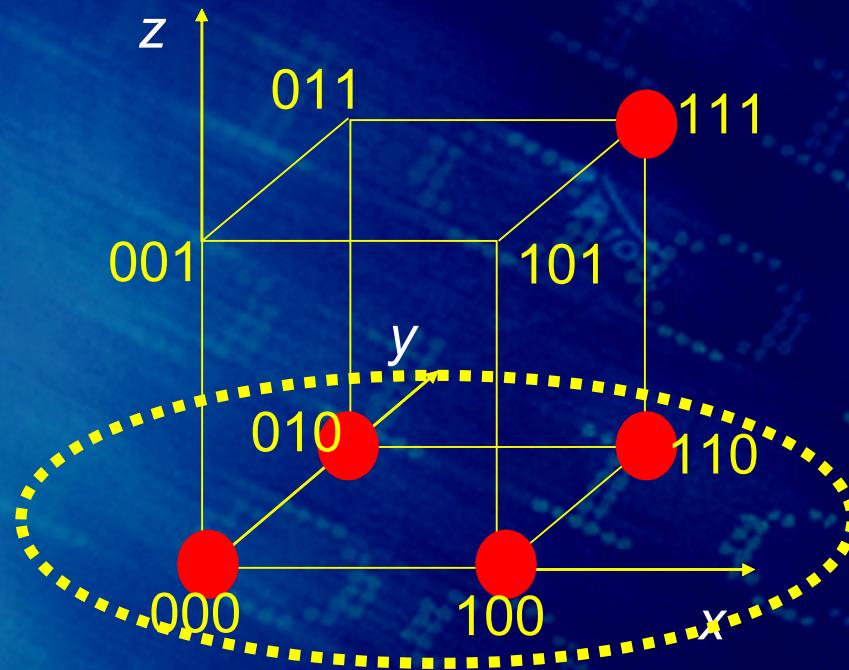
Instead of representing separately the 4 vertices



we could represent the whole “face”

A further step

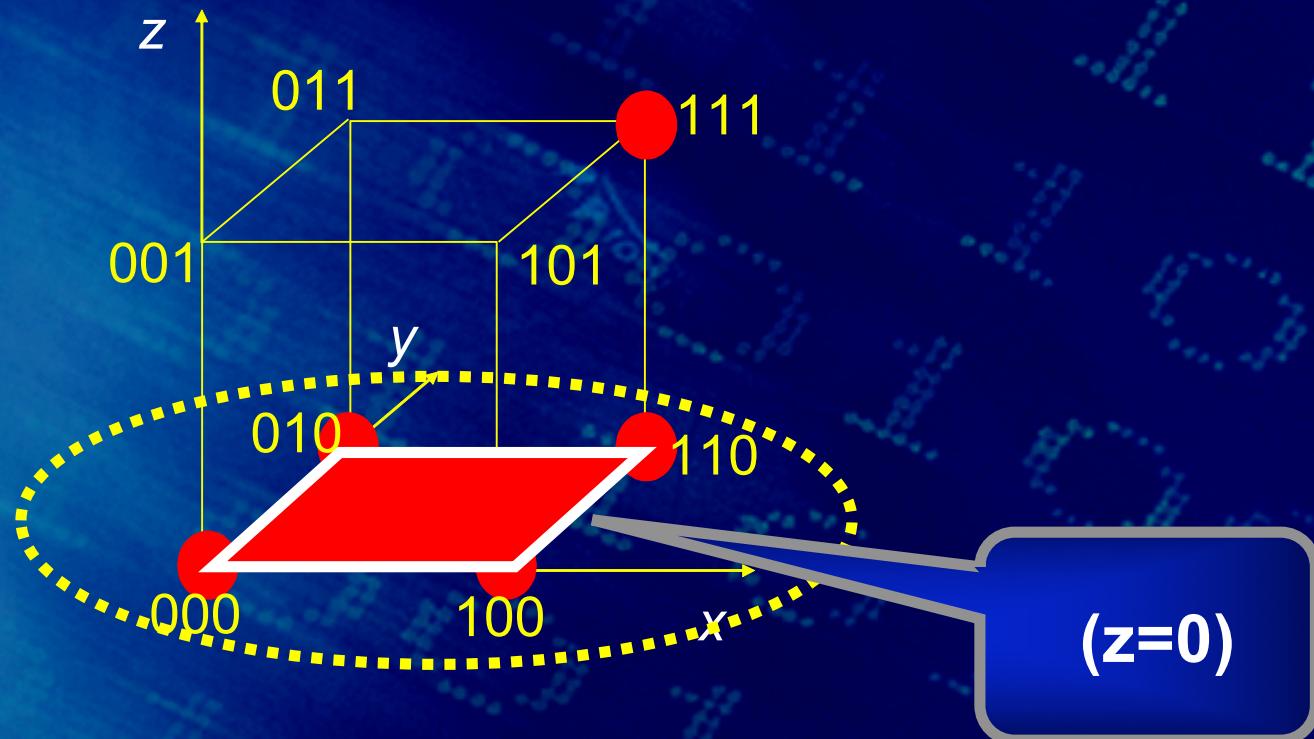
Instead of representing separately the 4 vertices



we could represent the whole “face”

A further step

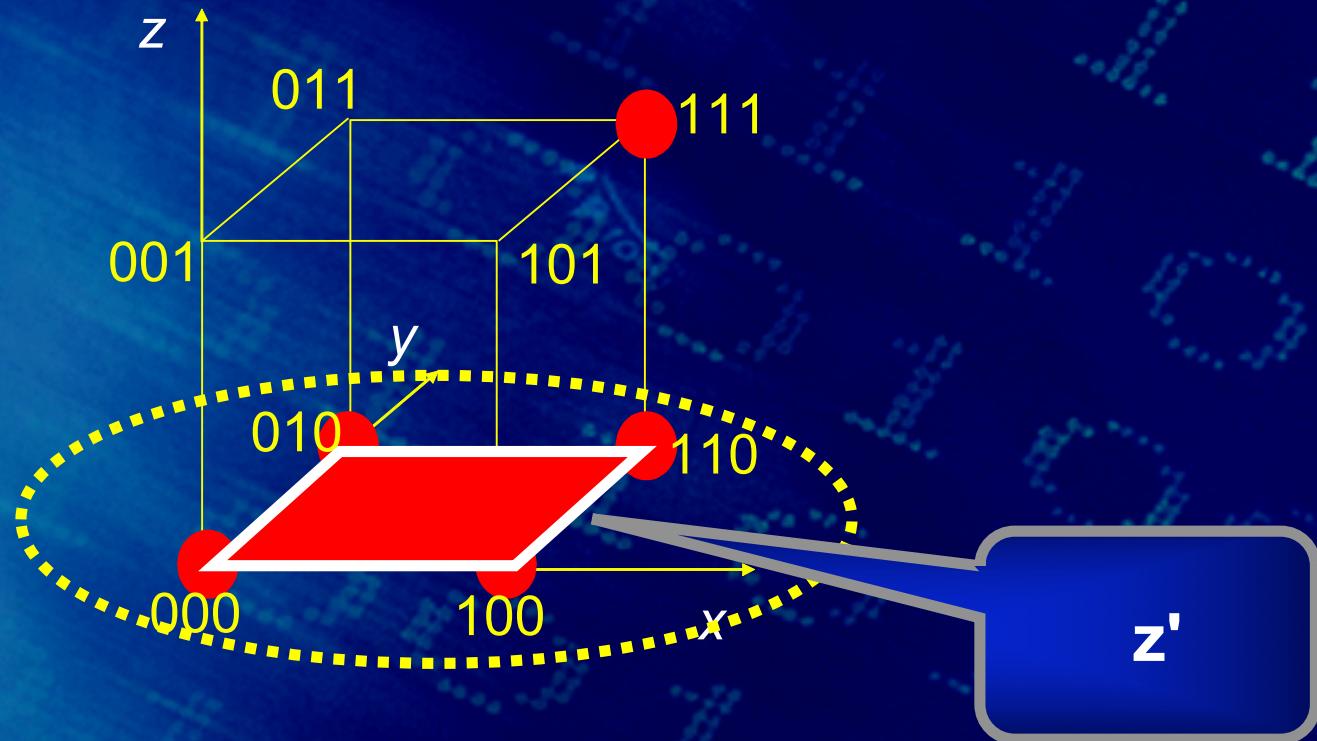
Instead of representing separately the 4 vertices



we could represent the whole “face”

A further step (3)

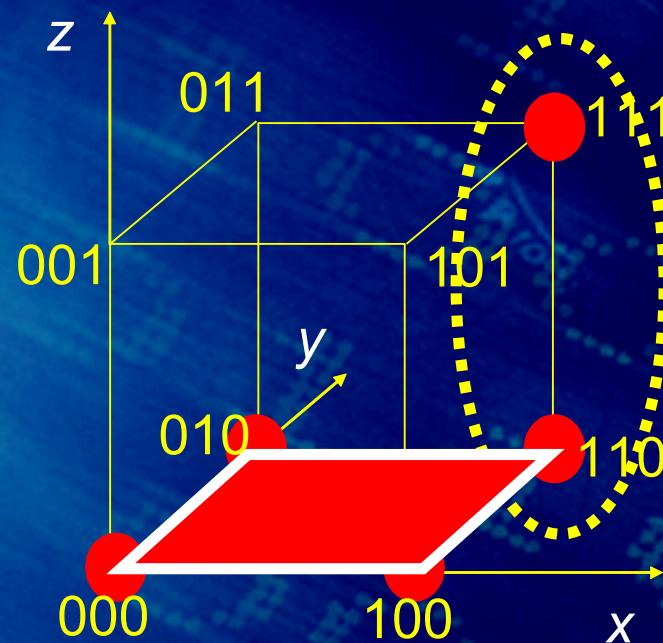
... and instead of representing separately the 2 vertices



we could represent the related “edge”

A further step (3)

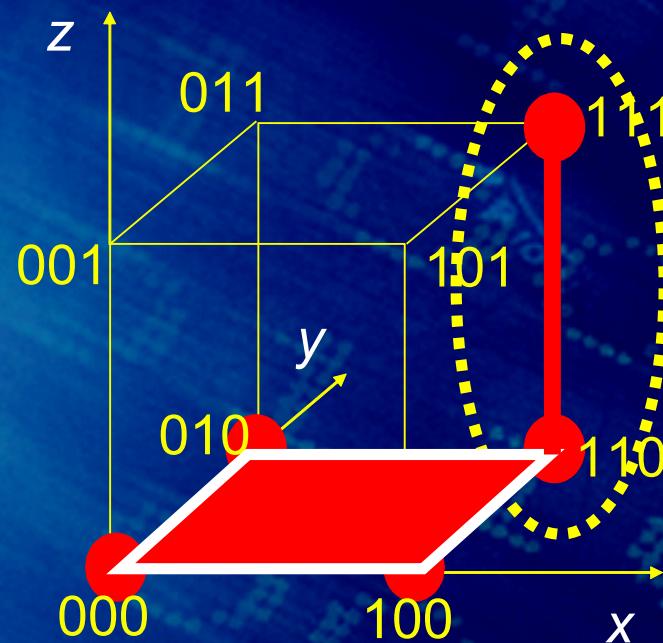
... and instead of representing separately the 2 vertices



we could represent the related “edge”

A further step (4)

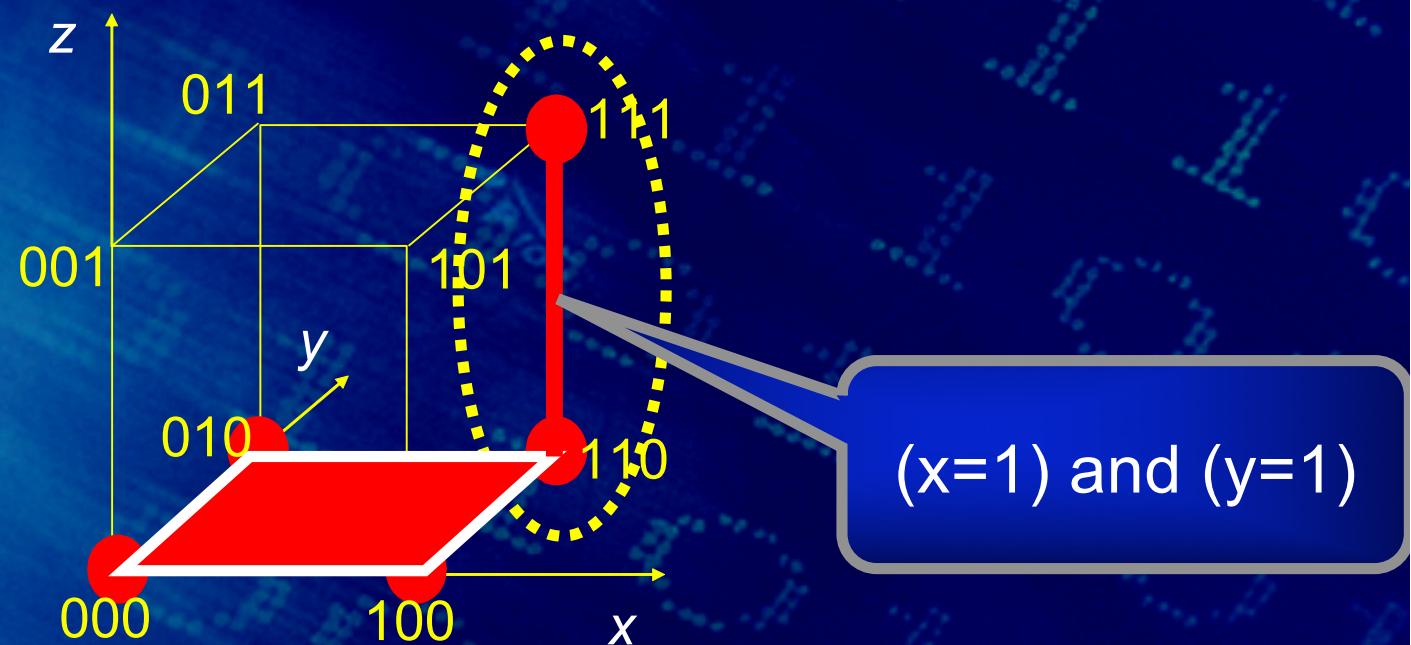
... and instead of representing separately the 2 vertices



we could represent the related “edge”

A further step (5)

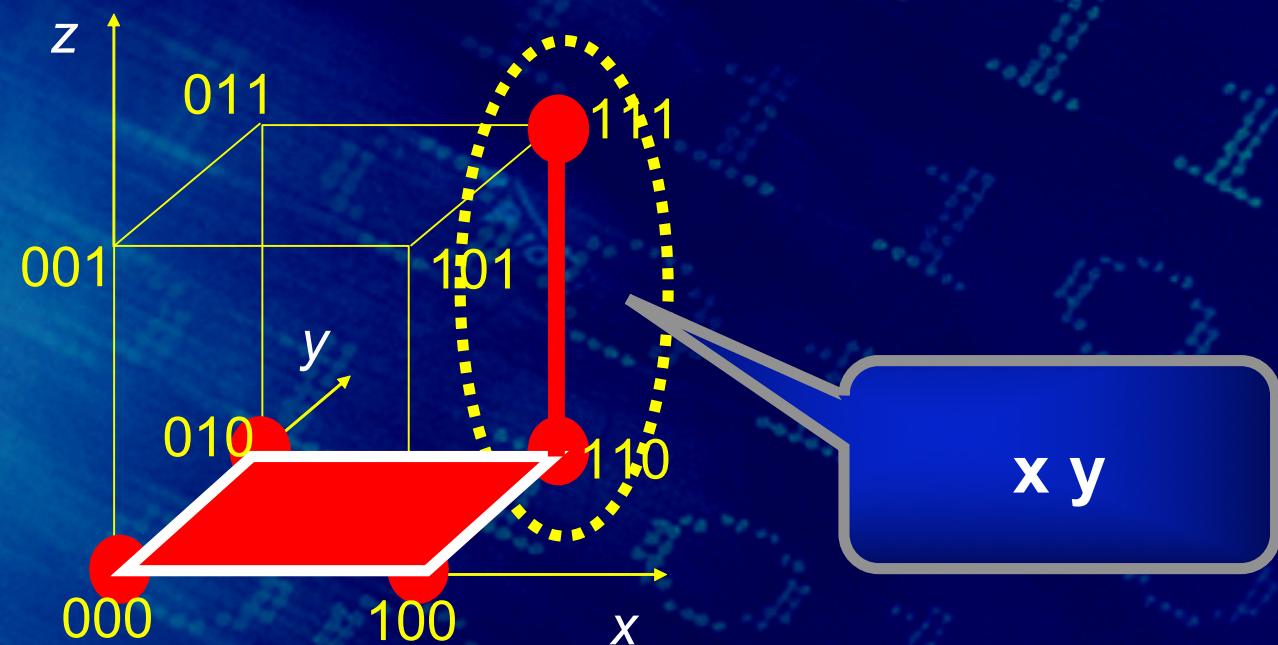... and instead of representing separately the 2 vertices



we could represent the related “edge”

Thus obtaining

$$F =$$

$$x'y'z' +$$

$$x'y'z +$$

$$x'y z' +$$

$$x'y z +$$

$$x y z$$

→

$$F = z' + x y$$

Let's formalized the concept

K-cube


A k-dimensional sub-space
(or k-cube)

$$S_k \subseteq B^n$$

is a set of 2^k vertices, in which $n-k$
input variables get a same constant
value



0-cube = vertex

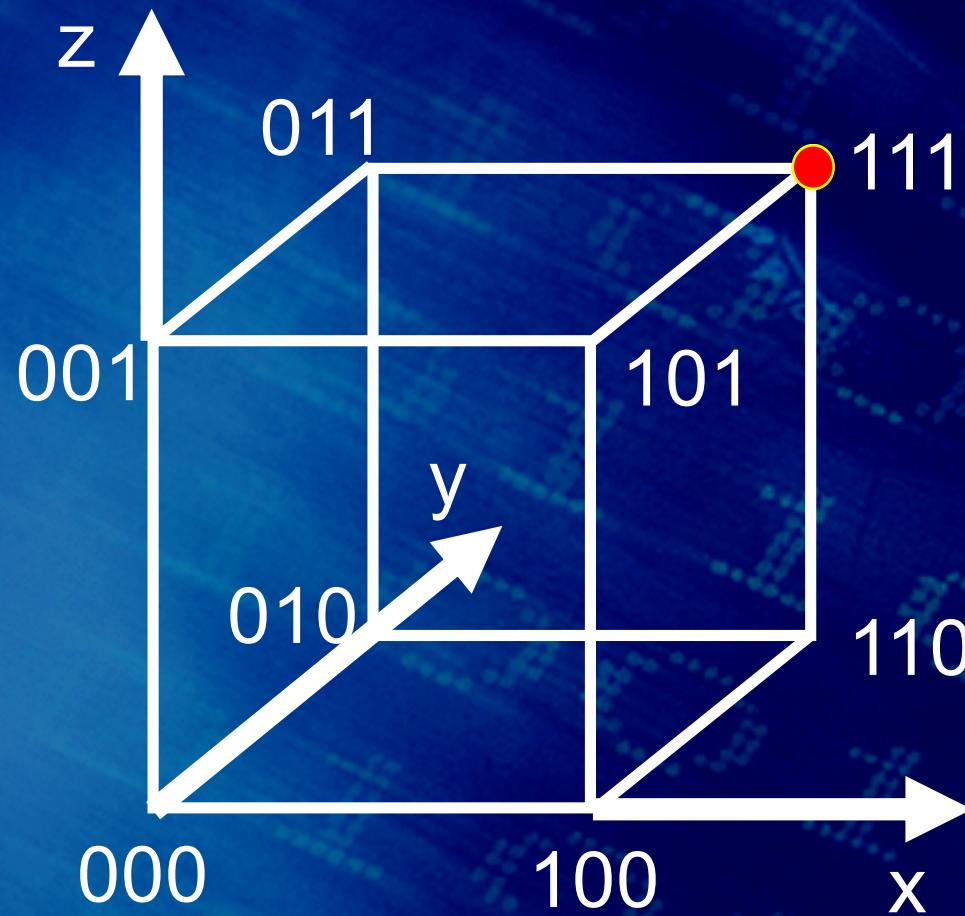


$$B = \{ 0, 1 \}$$
$$B^3$$

$$n = 3$$

$$k = 0$$

$$n-k = 3$$

1-cube = edge

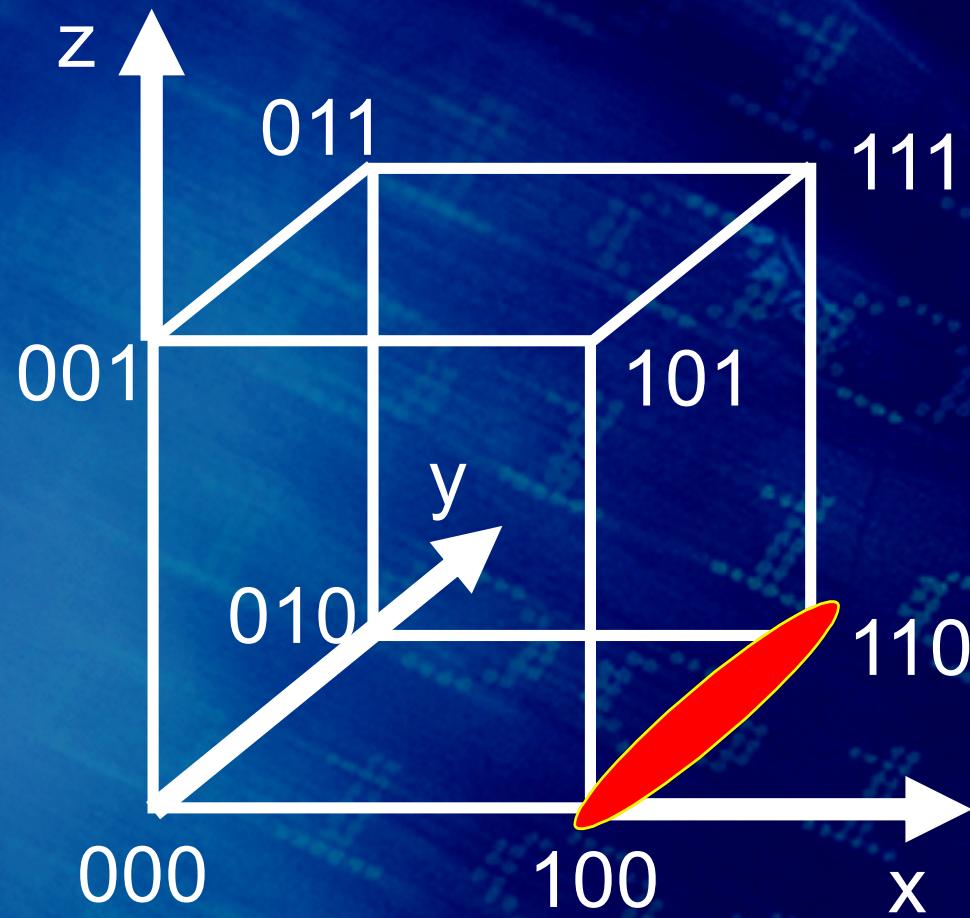

$$B = \{ 0, 1 \}$$


$$B^3$$

$$n = 3$$

$$k = 1$$

$$n-k = 2$$

2-cube = face

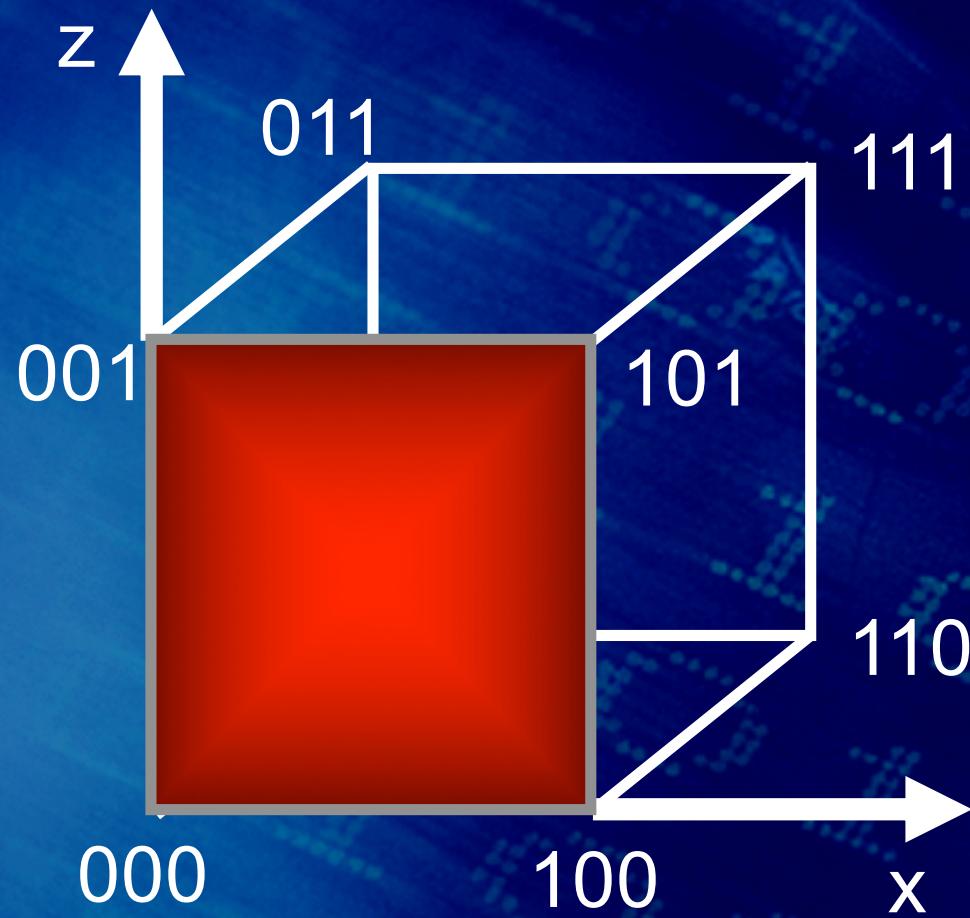

$$B = \{ 0, 1 \}$$
$$B^3$$

$$n = 3$$


$$k = 2$$

$$n-k = 1$$

Remark #1

- Not all the sub-sets of B^n with cardinality 2^k are k-cubes.

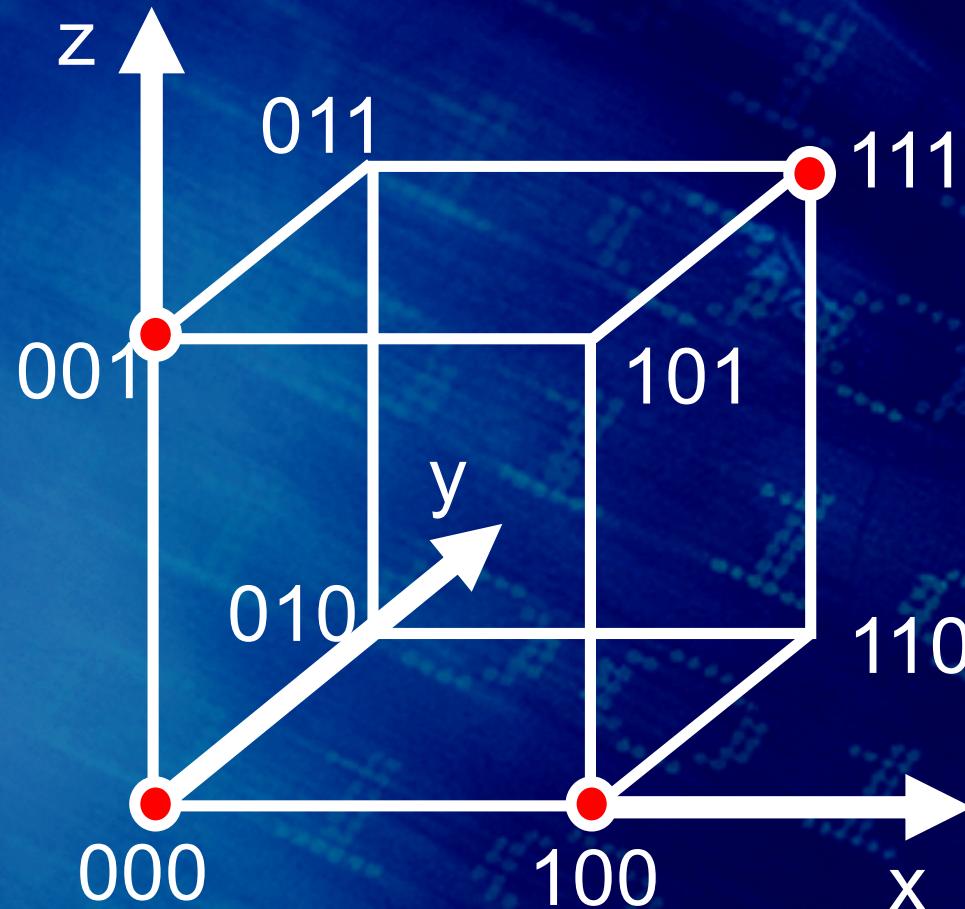An example of set of 2^2 vertices which is NOT a 2-cube



$$B = \{ 0, 1 \}$$
$$B^3$$

Remark #2

- K-cubes are easy to find when resorting to geometrical (spatial) representations, since we look for physically adjacent vertices...
- But not so easy when the function is represented in 2 dimensions, only

Karnaugh Maps


They try to make the task easier...





Karnaugh maps

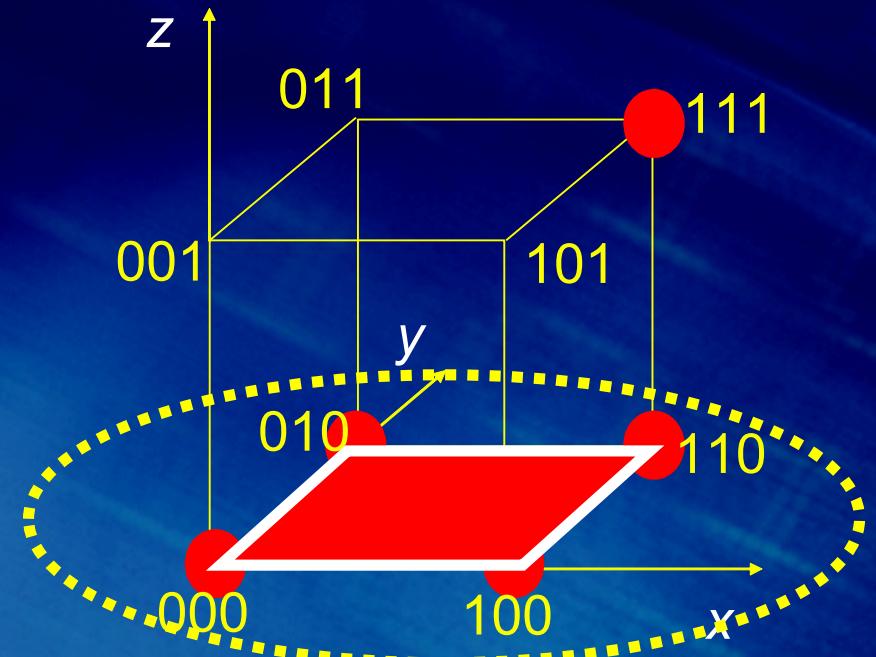
- **Values are assigned to rows and columns in such a way that cells that are physically adjacent in the geometric representation be physically adjacent in the planar representation, as well.**
- **Rows and columns are thus usually labeled to follow the reflected Gray code sequence:**






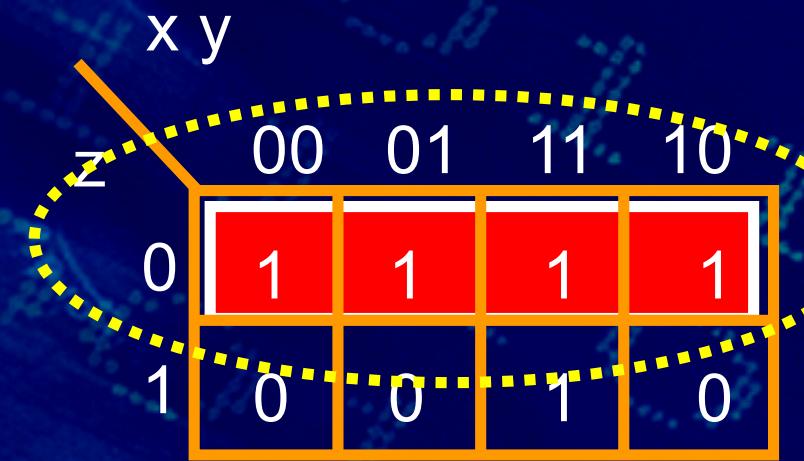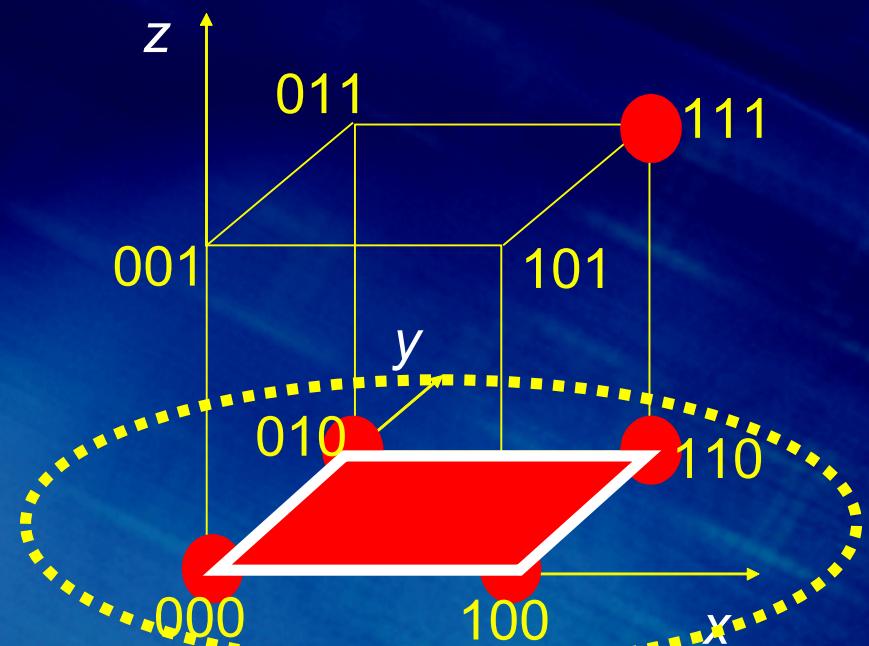

3 input maps

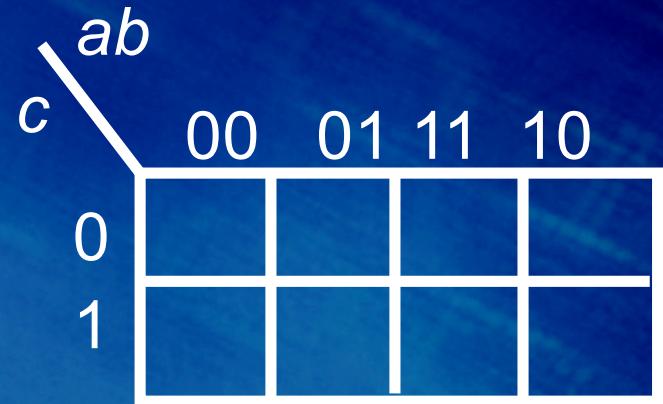


3 input maps

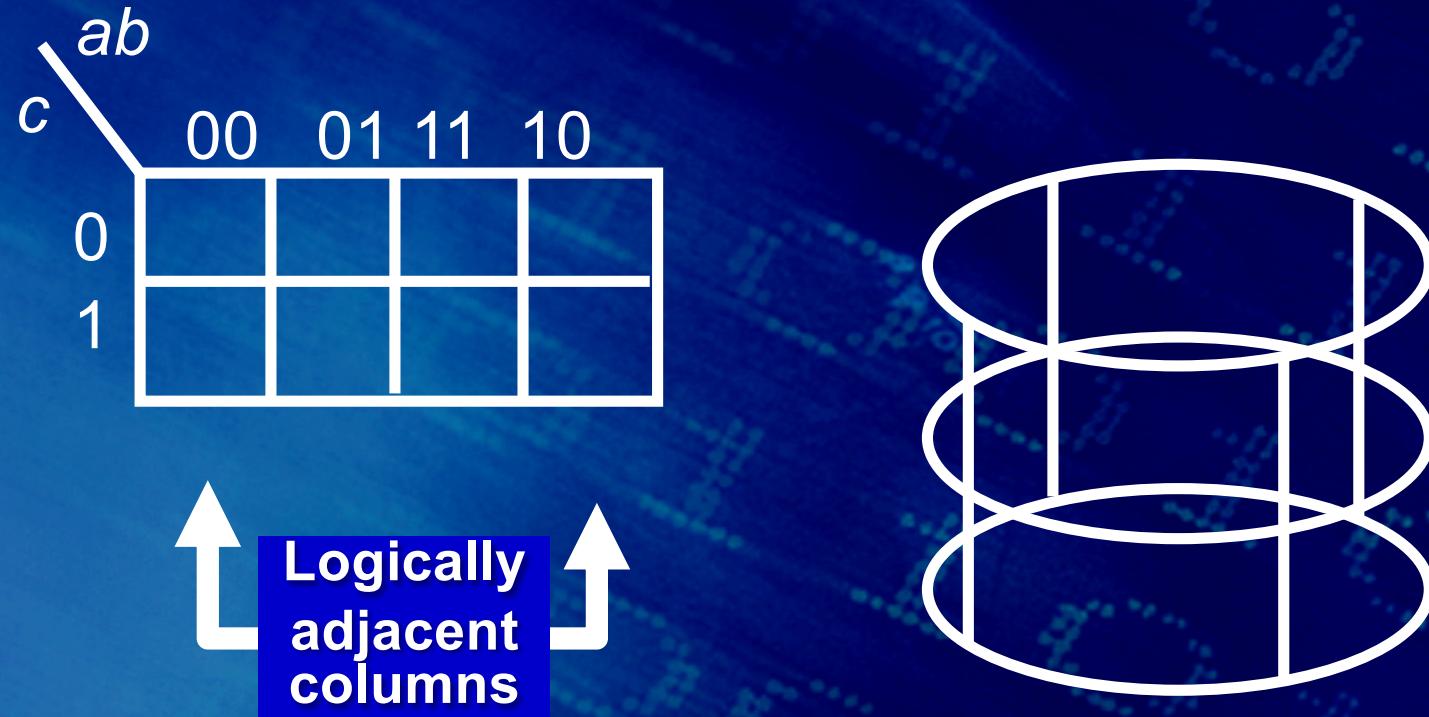


4 input maps


cd	ab	00	01	11	10
00					
01					
11					
10					

4 input maps

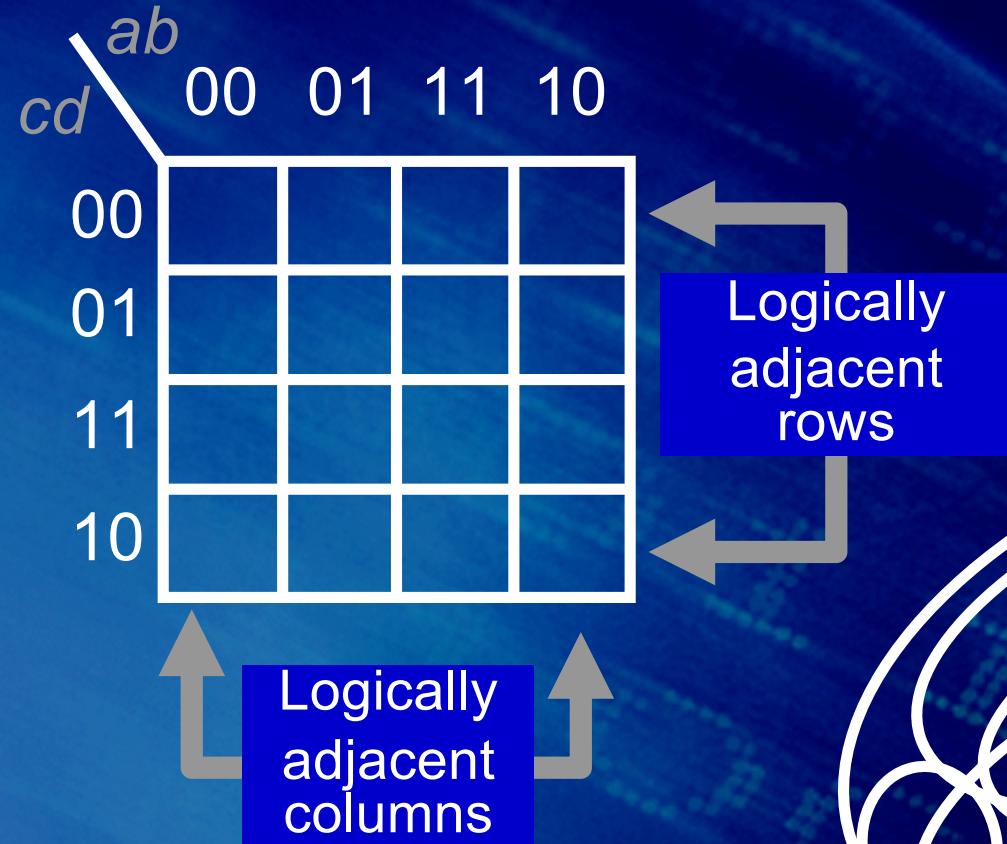

5 input maps

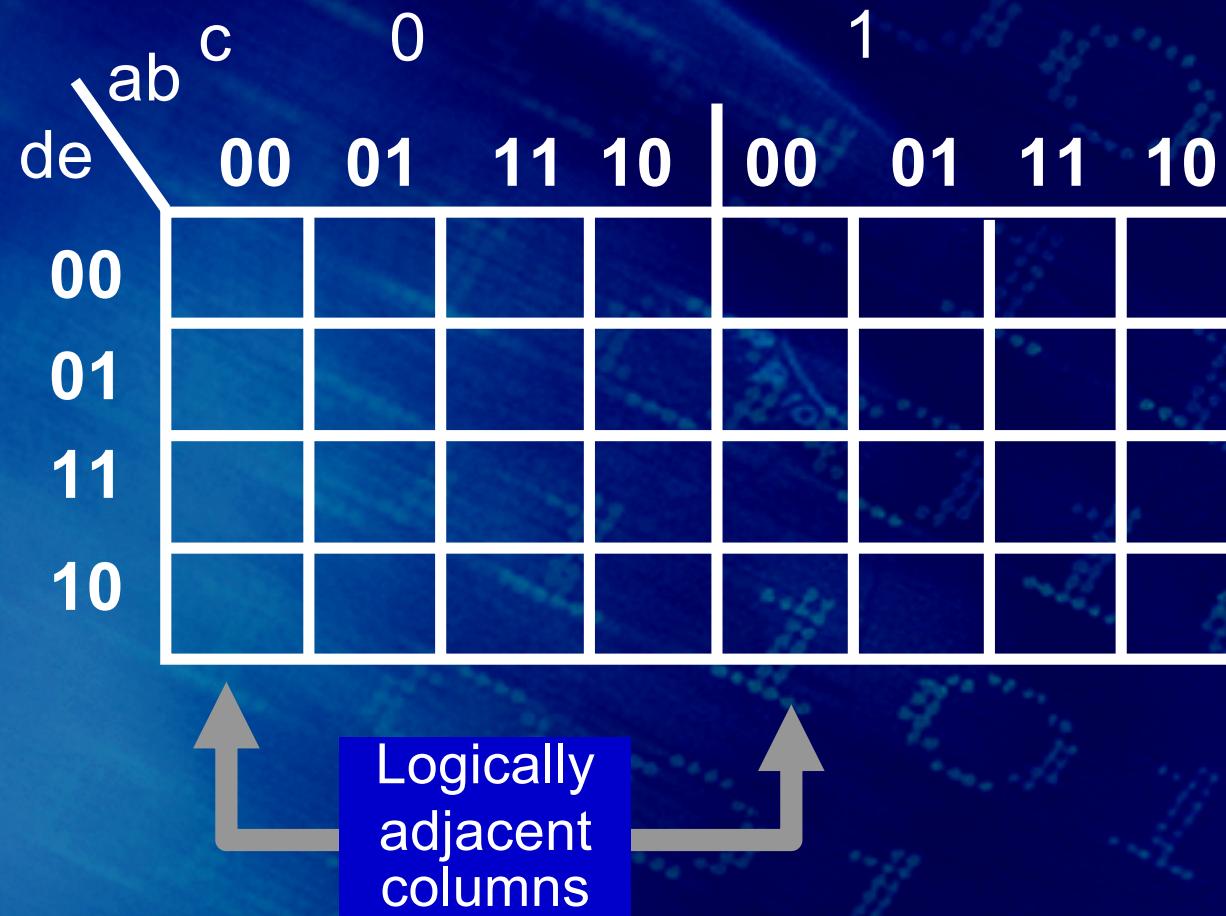


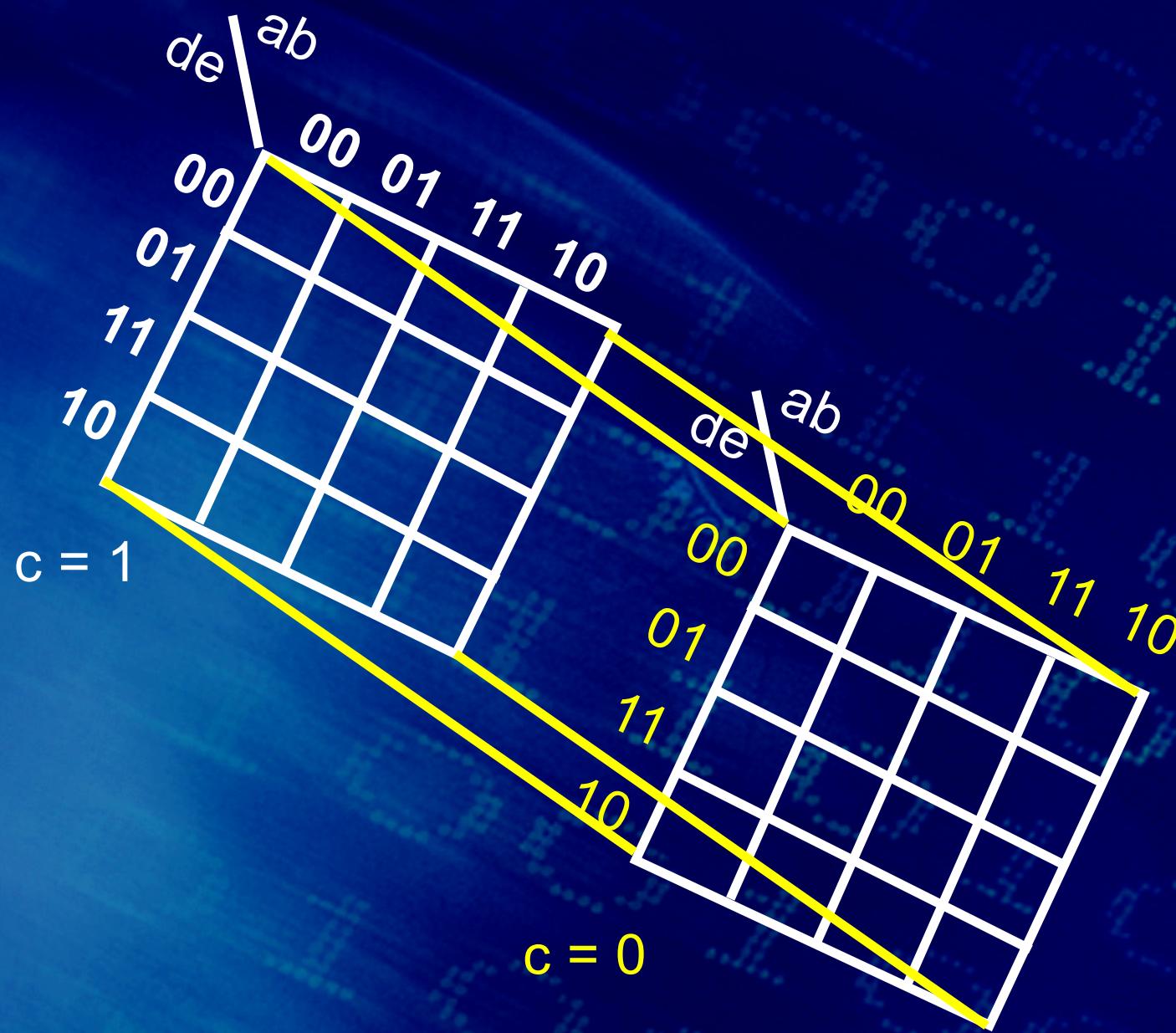

Remark #3

- The adopted solution is perfect for humans but not so efficient for machines...

Machine oriented representation

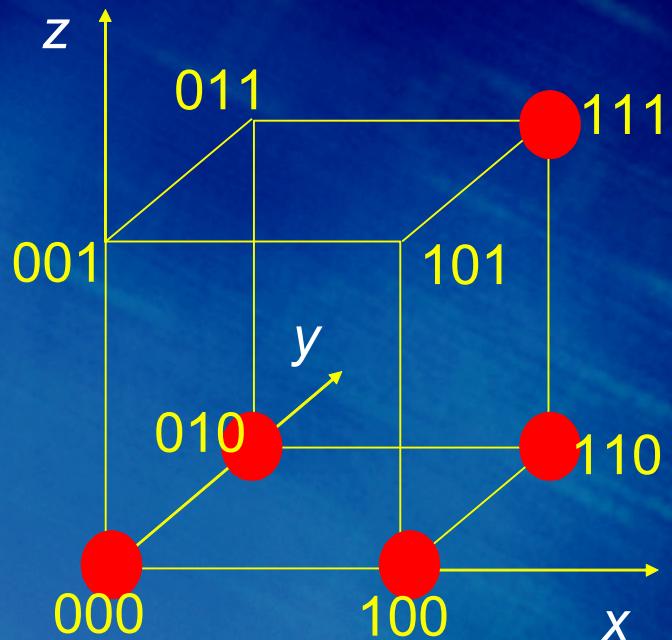


We could write:

$$\begin{aligned} F = & \\ 000 + & \\ 010 + & \\ 110 + & \\ 100 + & \\ 111 \end{aligned}$$


A further step

The whole “face” could be represented as

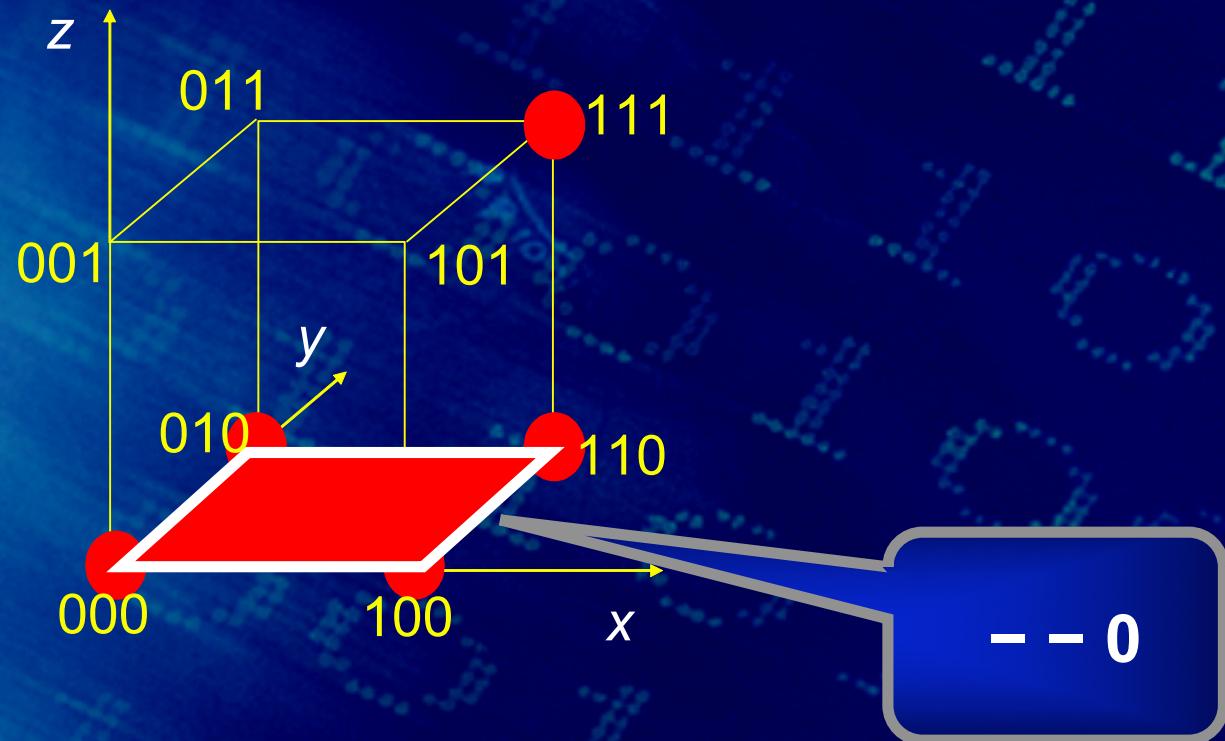

A further step (2)

... and the edge could be represented as

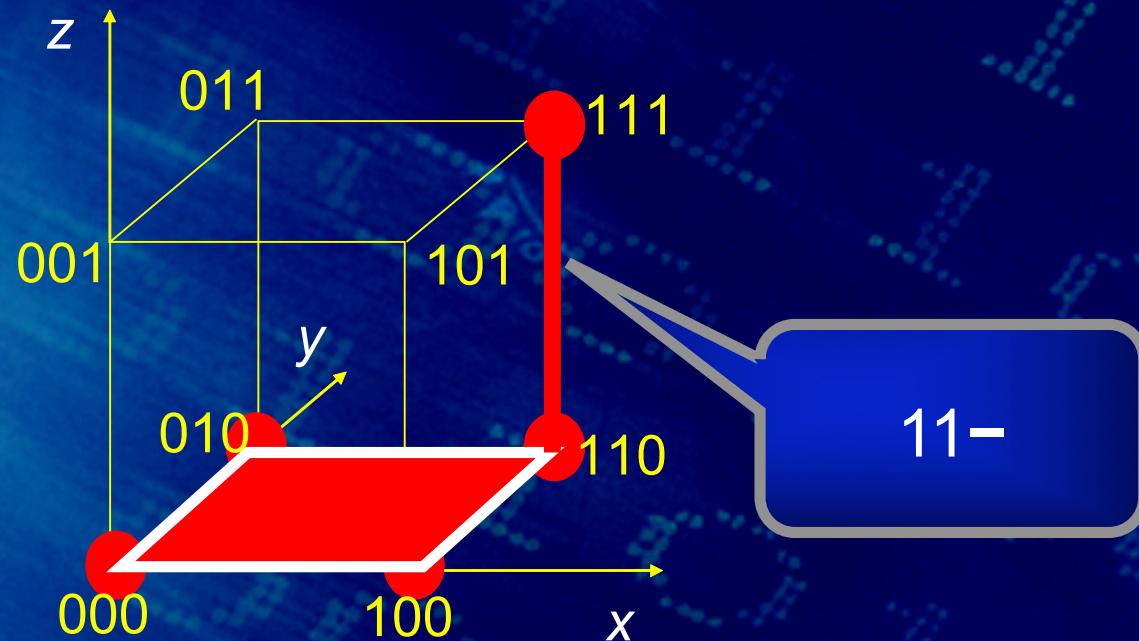

Thus obtaining

$$\begin{aligned} F = \\ 000 + \\ 010 + \\ 110 + \\ 100 + \\ 111 \end{aligned}$$




$$\begin{aligned} F = \\ - - 0 + \\ 11 - \end{aligned}$$

Outline

- From functions to circuits
- Remarks
- **Problems to face**
- Lessons learned

CAVEAT

*A Boolean function
can be represented
by an infinite # of
Boolean expressions*

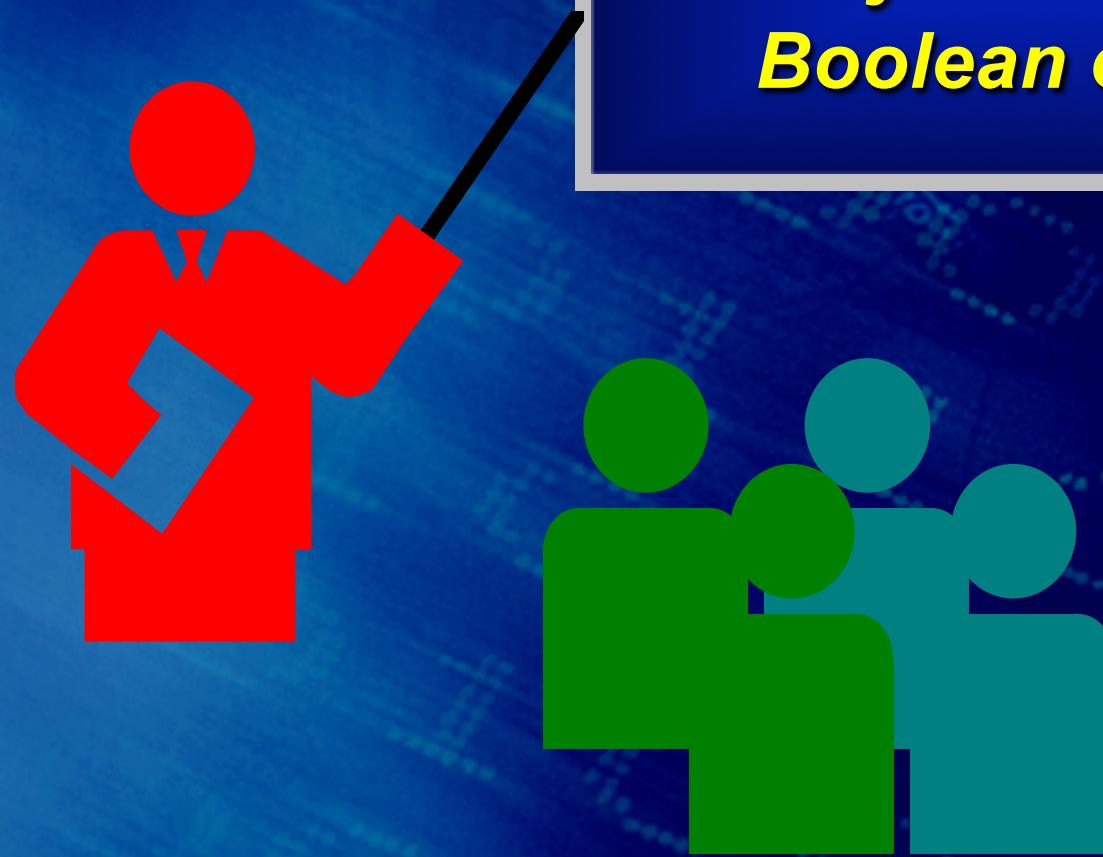

Example 1

The following **Boolean expressions** all represent the same **Boolean function**:

a

$a + a$

$a + a + a$

$a + a + a + a$

...

Example 2

The following **Boolean expressions** all represent the same **Boolean function**:

$$a + x$$

$$a x' + x$$

$$a + a' x$$

$$a + a + x$$

$$(a + x) a + a' x$$

Problems to face

- Check whether two representations are equivalent (*equivalence checking*)
- Find an equivalent representation having “minimum cost” (*minimization*)
- Guarantee that, for each representation method, each function have a unique representation (*canonicity*)



Caveat

The three above problems have different complexity and different solutions for each representation method.





Equivalence checking with Boolean Expressions

The equivalence between two boolean expressions can be verified:

- ***manually***, resorting to a set of re-write rules, mainly based on postulates, properties and theorems of boolean algebras
- ***automatically***, resorting to ad-hoc tools, such as ***tautology checkers*** or, more in general, ***theorem provers***.

Example 1

Prove that the following two expressions

$$F = z' + xy$$

$$F = x'y'z' + xy'z' + xyz' + x'y'z' + xyz$$

are equivalent

Solutions

$$\begin{aligned} F &= x'y'z' + xy'z' + xy z' + x'y z' + xy z = \\ &= (x' + x) y'z' + (x' + x) y z' + xy z = \\ &= y'z' + y z' + xy z = \\ &= (y' + y) z' + xy z = \\ &= z' + xy z = \\ &= z' + xy \end{aligned}$$

q.e.d.

Example 2

Prove that:

$$\begin{aligned}(c' + abd + b'd + a'b)(c + ab + bd) &= \\ &= b(a + c)(a' + c') + d(b + c)\end{aligned}$$

Solution (1)

$$(c' + abd + b'd + a'b) (c + ab + bd) =$$

$$c' (ab + bd) + c (abd + b'd + a'b) =$$

$$abc' + bc'd + abcd + b'cd + a'bc =$$

$$abc' + abcd + bc'd + a'bc + b'cd =$$

$$ab (c' + cd) + bc'd + a'bc + b'cd =$$

$$ab (c' + d) + bc'd + a'bc + b'cd =$$

$$ab (c' + d) + bc'd + a'bc + a'bd + b'cd =$$

$$abc' + abd + bc'd + a'bc + a'bd + b'cd =$$

$$(abd + a'bd) + abc' + bc'd + a'bc + b'cd =$$

Solution (2)

$$bd(a + a') + abc' + bc'd + a'bc + b'cd =$$

$$bd(1) + abc' + bc'd + a'bc + b'cd =$$

$$bd + abc' + bc'd + a'bc + b'cd =$$

$$bd + bc'd + abc' + a'bc + b'cd =$$

$$bd + abc' + a'bc + b'cd =$$

$$d(b + b'c) + abc' + a'bc =$$

$$d(b + c) + abc' + a'bc =$$

$$d(b + c) + b(ac' + a'c) =$$

$$d(b + c) + b(a + c)(a' + c')$$

q.e.d.

Equivalence checker

Equivalence checker:

$$f_1 = f_2 \ ?$$

$f_1 :=$ boolean function
of circuit #1

$f_2 :=$ boolean function
of circuit #2



Minimizing Boolean Expressions

Example

One could derive the expression:

$$F = z' + xy$$

from the expression:

$$F = x'y'z' + xy'z' + xyz' + x'y'z + xy z$$

By applying the rewriting rules and Boolean
Algebra theorems:

Solution

$$\begin{aligned} F &= x'y'z' + xy'z' + xy z' + x'y z' + xy z = \\ &= (x' + x) y'z' + (x' + x) y z' + xy z = \\ &= y'z' + y z' + xy z = \\ &= (y' + y) z' + xy z = \\ &= z' + xy z = \\ &= z' + xy \end{aligned}$$



Canonicity with Boolean Expressions

An **SOP** expression is **canonical** iff is composed of minterms, only.

Canonicity with Boolean Expressions

An SOP expression is ***canonical*** iff is composed of minterms, only.

$$f = x' y z' + \\ x y' z + \\ x y z$$

canonical

Canonicity with Boolean Expressions

An SOP expression is **canonical** iff is composed of minterms, only.

$$f = x' y z' + x y' z + x y z$$

canonical

$$f = x' y z' + x z$$

not canonical

Outline

- From functions to circuits
- Remarks
- Problems to face
- Lessons learned

From functions to circuits (Library binding)

The library binding of boolean expressions is trivial:


<i>logic operation</i>	<i>logic gate</i>
sum	or
product	and
complement	not

Example

$$U = A'B' + AD$$

Example

$$U = A'B' + AD$$

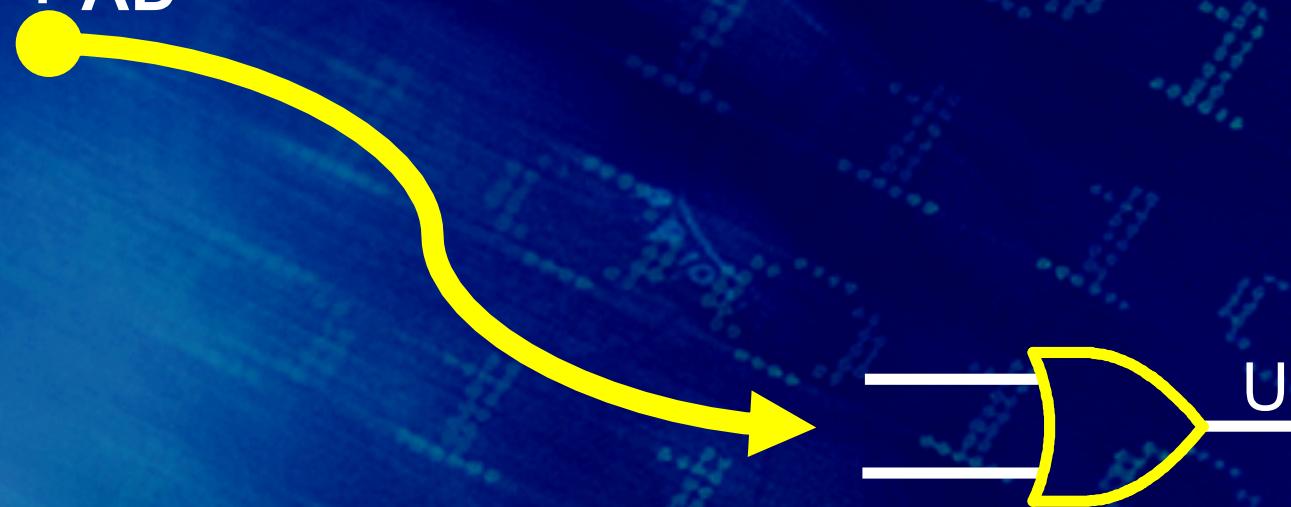


Example

$$U = A'B' + AD$$




Example

$$U = A'B' + AD$$

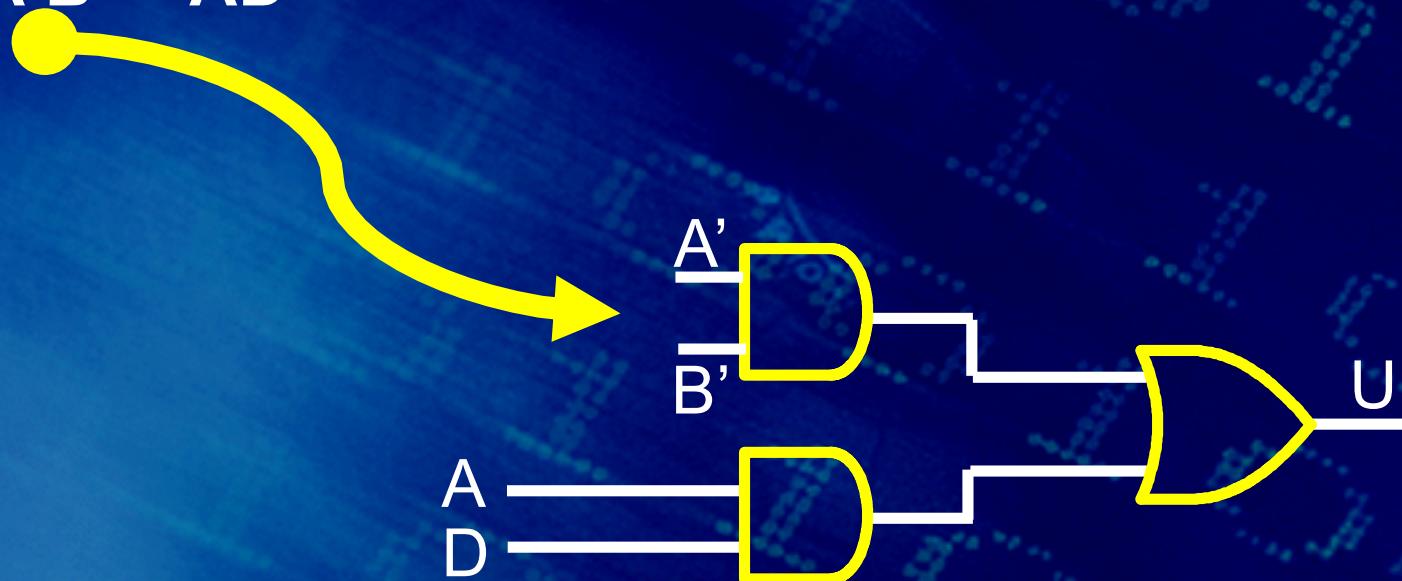


Example

$$U = A'B' + AD$$

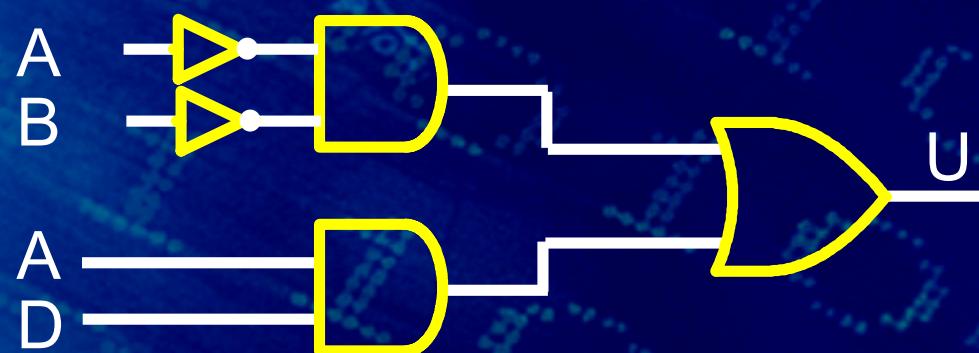


Alternative implementation

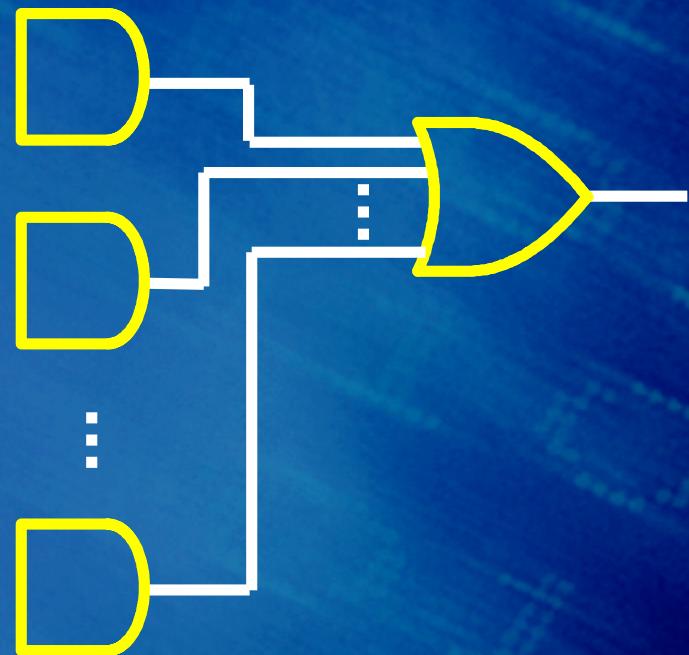The above presented approach always leads to circuits implemented as 2-level networks:



or

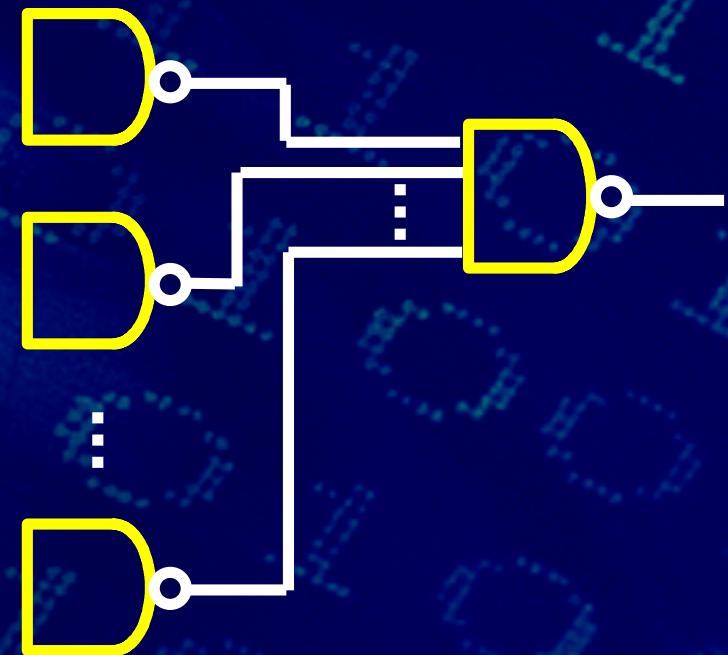


Alternative implementation (2)

In order to use different gates or to get different circuit “shapes”, algebraic transformations on the obtained logic expressions have to be performed.

Example 1


Starting from:

$$U = A'B' + AB$$

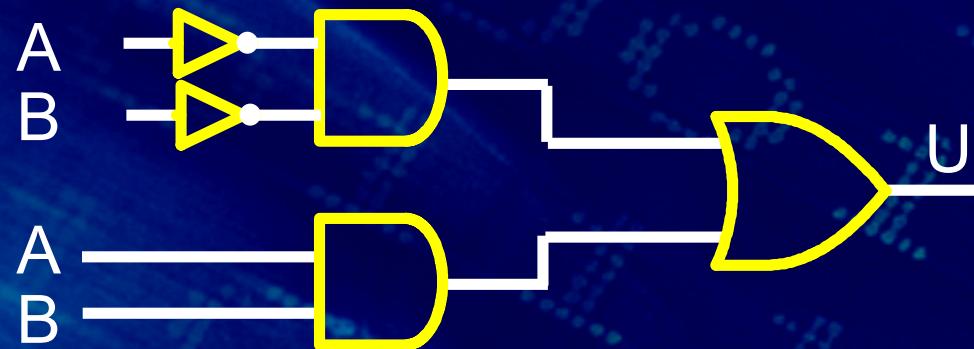

applying the De Morgan Theorem, one gets:


$$U = (A + B)' + AB$$

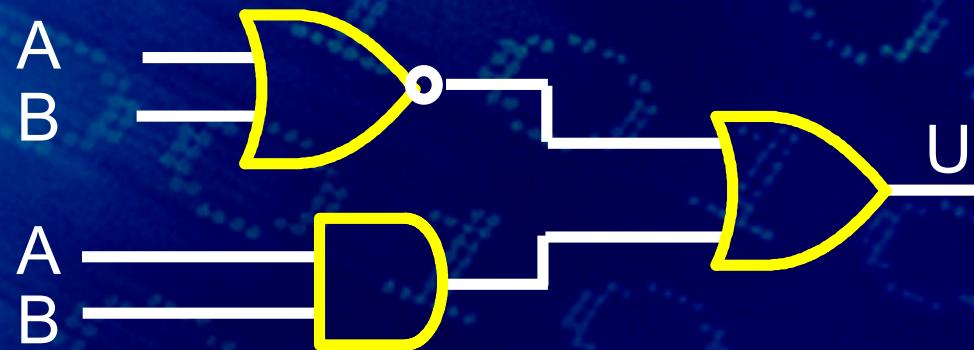

Example 2

Starting from:

$$U = A'B' + AB$$

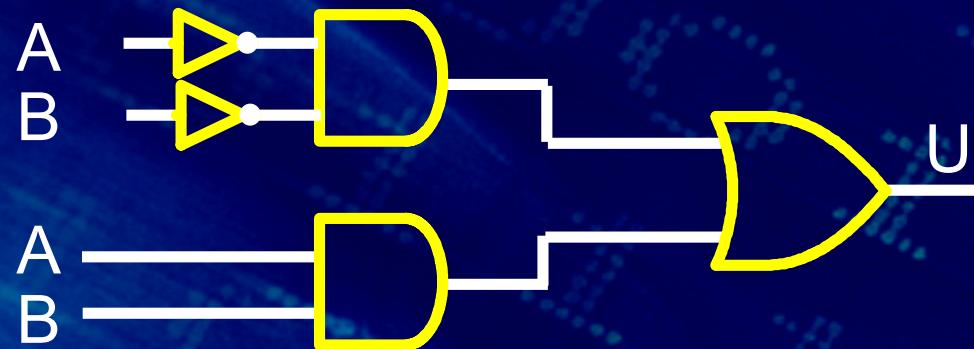

applying the ex-nor definition, one gets:

$$U = (A+B)' + AB$$



Practical implication

- If we use logic gates to implement the function

$$F = z' + x y$$

we obtain:

Practical implication

- If we use logic gates to implement the function

$$F = z' + x y$$

we obtain:




Practical implication (2)

- If we use logic gates to implement the equivalent function

$$F = x'y'z' + x'y'z + x'y z' + x'y z + x y z$$

we obtain:

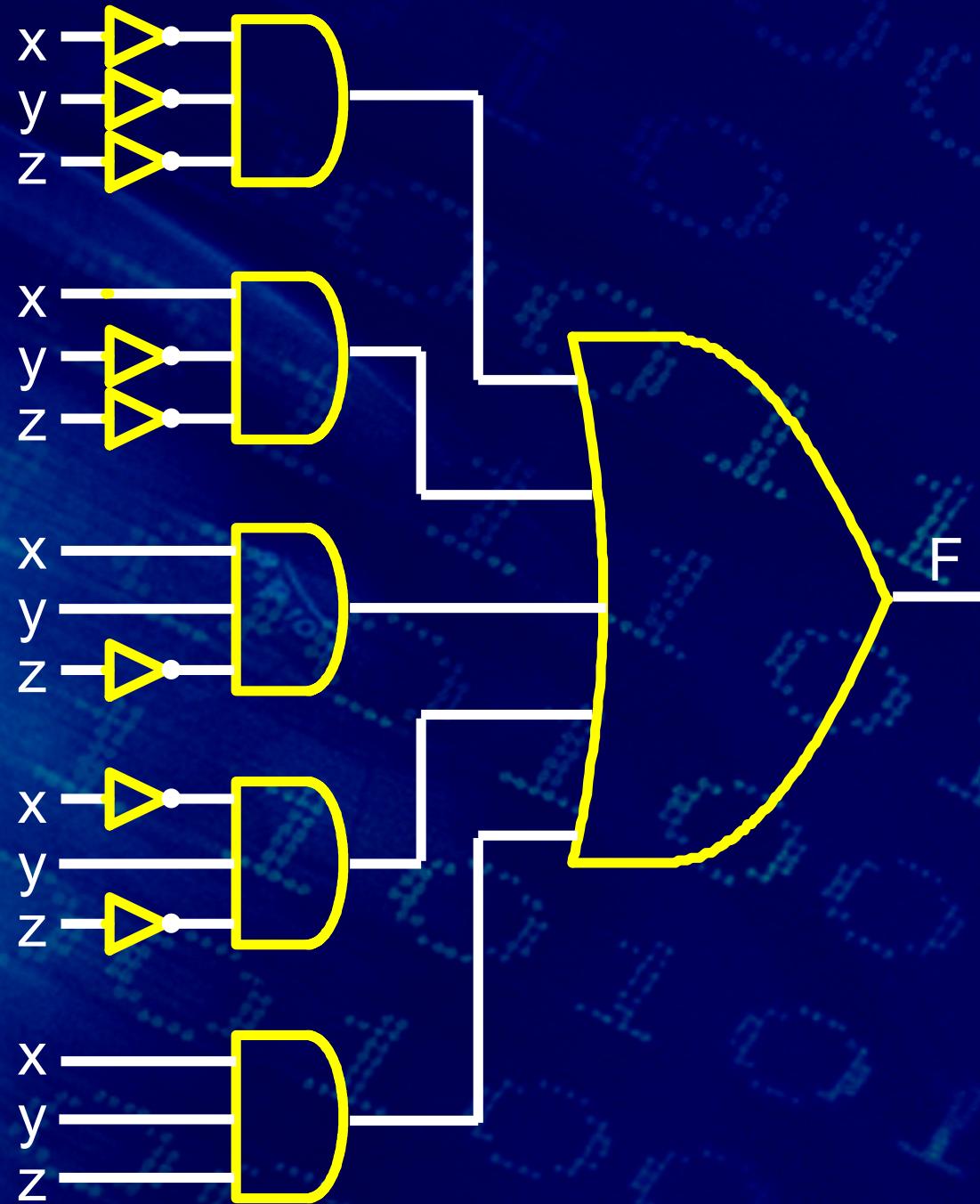- $F =$
 $x'y'z' +$
 $x'y'z' +$
 $x'y z' +$
 $x'y z' +$
 $x y z$



Lessons learned

1. Concept of “**cost**”

- The “**cost**” of an implementation is proportional to the “**cost**” of the expression to be implemented
- Minimizing expressions implies minimizing the implementation cost.

Малые Автюхи, Калинковичский район, Республики Беларусь

