

**Lecture
0_4.4**

Digital Network Modeling



cini
Cybersecurity
National Lab

Paolo PRINETTO

Politecnico di Torino (Italy)

Univ. of Illinois at Chicago, IL (USA)

CINI Cybersecurity Nat. Lab. (Italy)

Paolo.Prinetto@polito.it

www.consorzio-cini.it

www.comitato-girotondo.org

License Information

This work is licensed under the
Creative Commons BY-NC
License



To view a copy of the license, visit:
<http://creativecommons.org/licenses/by-nc/3.0/legalcode>

Disclaimer

- **We disclaim any warranties or representations as to the accuracy or completeness of this material.**
- **Materials are provided “as is” without warranty of any kind, either express or implied, including without limitation, warranties of merchantability, fitness for a particular purpose, and non-infringement.**
- **Under no circumstances shall we be liable for any loss, damage, liability or expense incurred or suffered which is claimed to have resulted from use of this material.**

Goal

- The lecture aims at presenting the basic concepts in modeling digital networks, focusing, in particular, on:
 - . Combinational vs. sequential
 - . Mealy vs. Moore
 - . I/O clustering.

Prerequisites

– Lecture 0_4.2

Homework

– None

Further readings

- Students interested in making a reference to a text book on the arguments covered in this lecture can refer, for instance, to:

- *G. Conte, A. Mazzeo, N. Mazzocca, P. Prinetto: “Architettura dei calcolatori”, Città Studi, 2015 (Chapter 1: Classificazioni e Concetti base & App. B: Modellizzazione di circuiti digitali)) (In Italian)*



Outline

- **Combinational vs. sequential networks**
- **Moore vs. Mealy machines**
- **I/O clustering**

Outline

- **Combinational vs. sequential networks**
- **Moore vs. Mealy machines**
- **I/O clustering**

Some graphic conventions

Hereinafter:

wires

will identify a bus or a set of

will identify a single bit wire

Model

***A model is a
simplification of
another entity, which
can be a physical
thing or another model***

[Jantsch, 2004]

Model's features

The model contains exactly those characteristics and properties of the modeled entity that are relevant for a given task



Minimal models

A model is minimal with respect to a task if it does not contain any other characteristics than those relevant for the task





Digital network


**A proper assembly of
electronic devices,
designed to store,
transform, and
communicate
information items
in **digital** form**


**Primary Inputs
(PIs)**

**Primary Outputs
(POs)**

**Digital
networks**

Digital networks classification

 


 

Combinational network

 A digital network is **combinational** iff its POs are completely determined by its present PIs, only






Combinational network

 A digital network is **combinational** iff its netlist doesn't contain any feedback loop






Sequential network

 A digital network is **sequential** if its POs are a function of past as well as present values of the PIs






1

Sequential network



A digital network is **sequential** if its netlist contains one, or more, feedback loops



An example

 


An example

  

Feedback

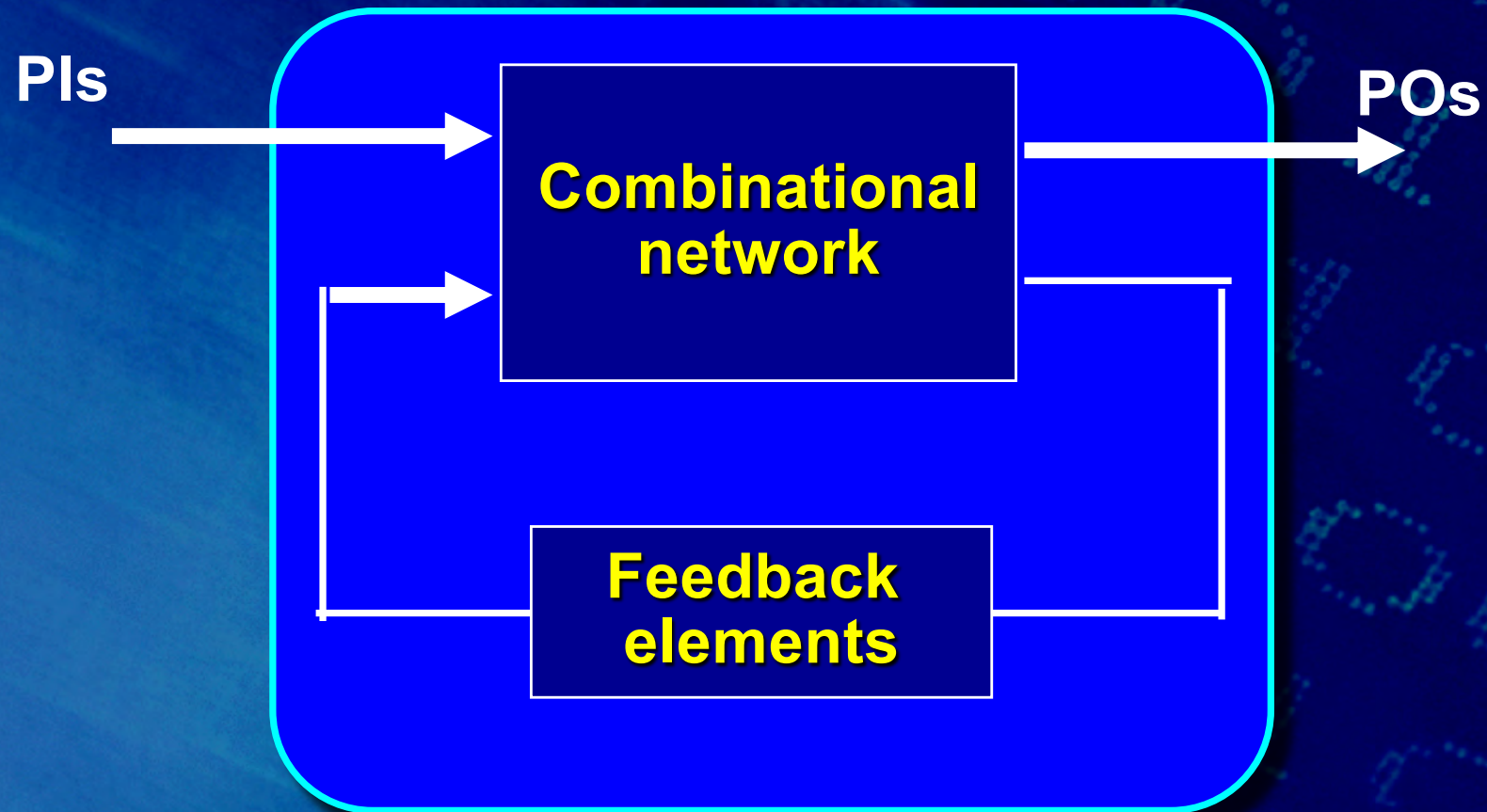
General structure of a sequential network




The concept of state

- A sequential circuit must be able to “remember”, or “store”, some information items related to the values the PIs have got.
- Such a storing capability is accomplished in terms of “**internal states**”: in any instant, the circuit is in a well defined “state”, univocally represented by the values got by the set of “internal state variables”.

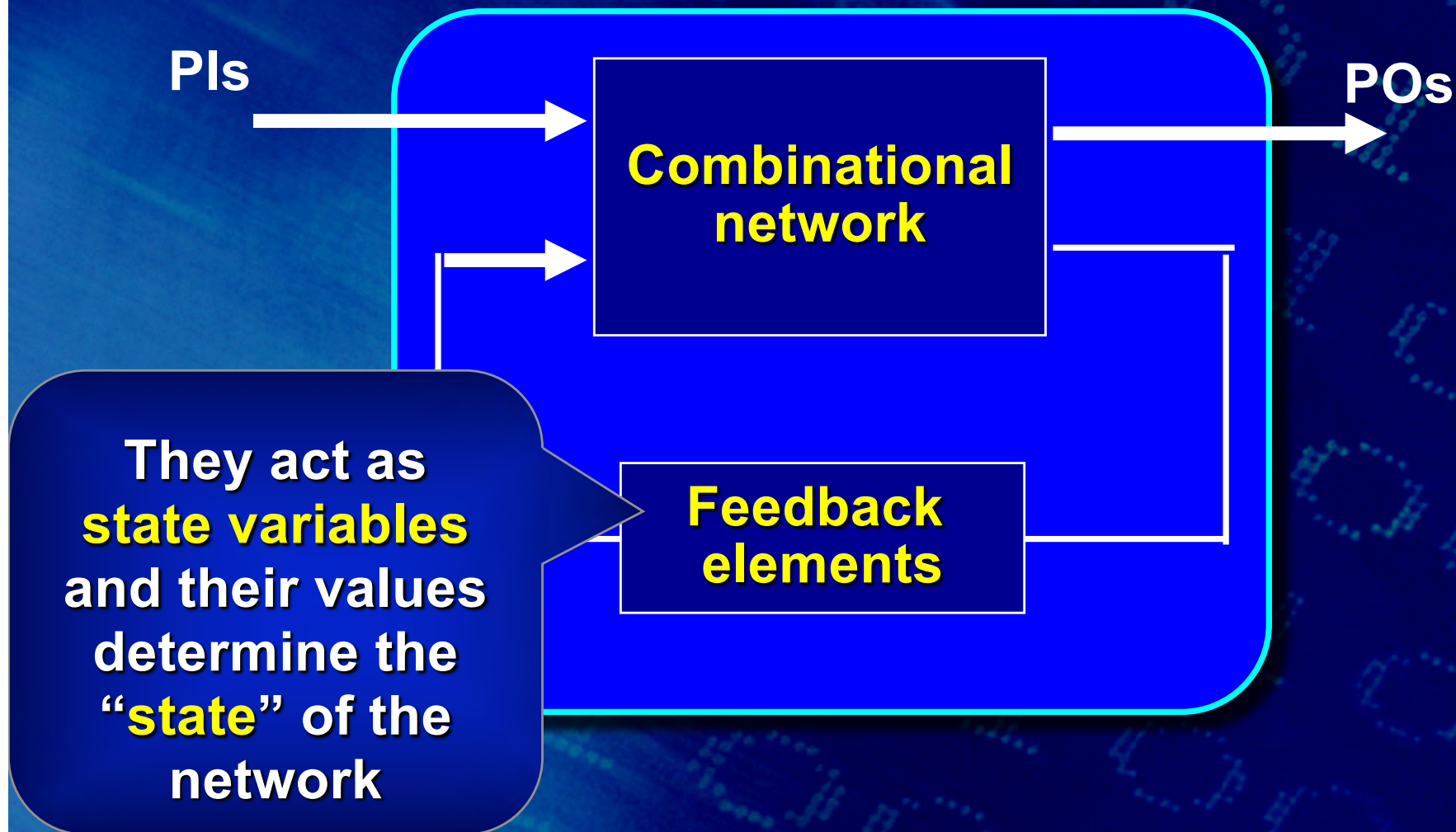
General structure of a sequential network



 General structure of a sequential network



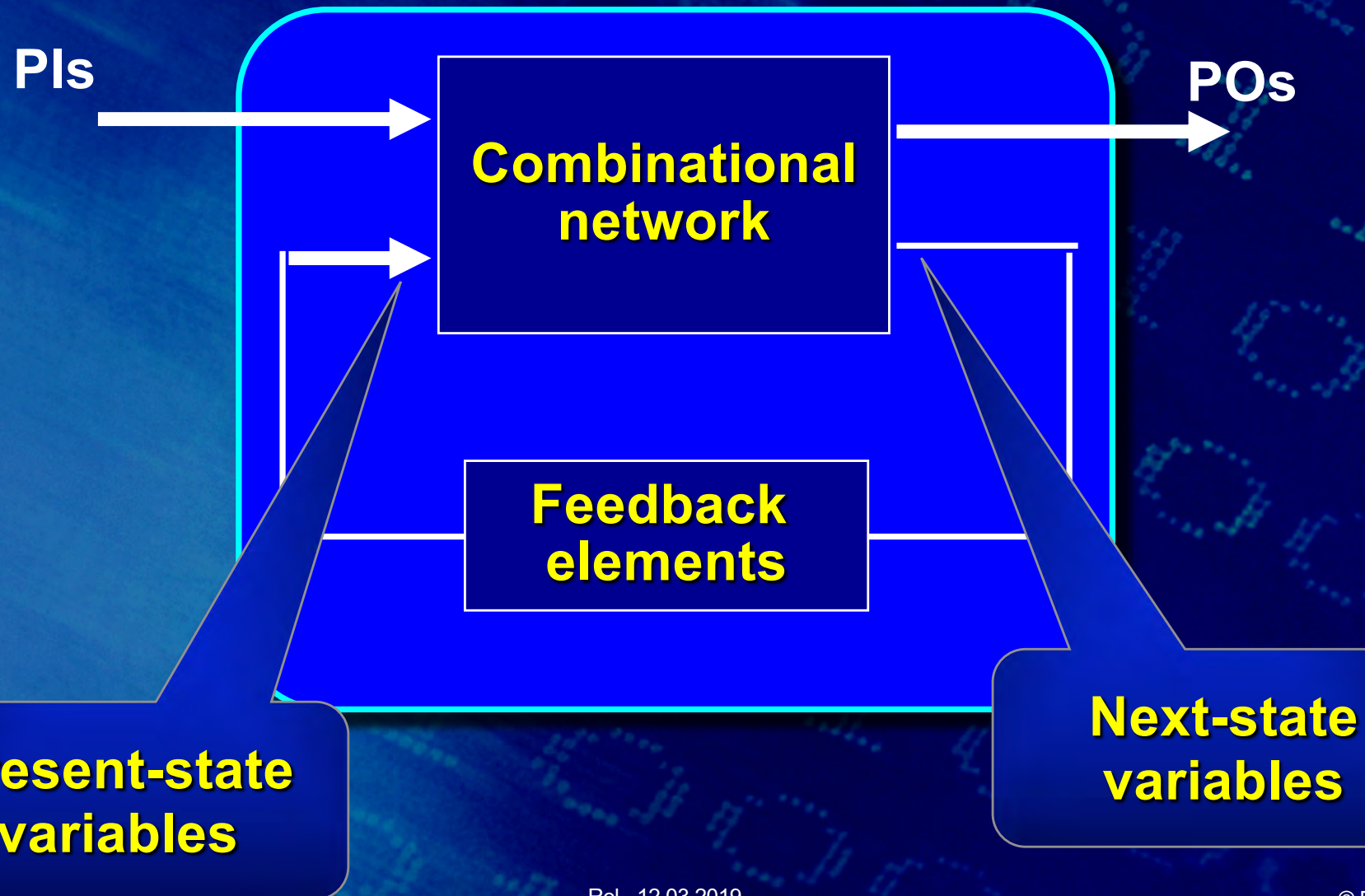
General structure of a sequential network




State variables

- A sequential network has as many state variables as feedback elements
- Each state variables can get **2** possible values
- A network with **n** state variables is characterized by **2^n** possible states.

Sequential network classification

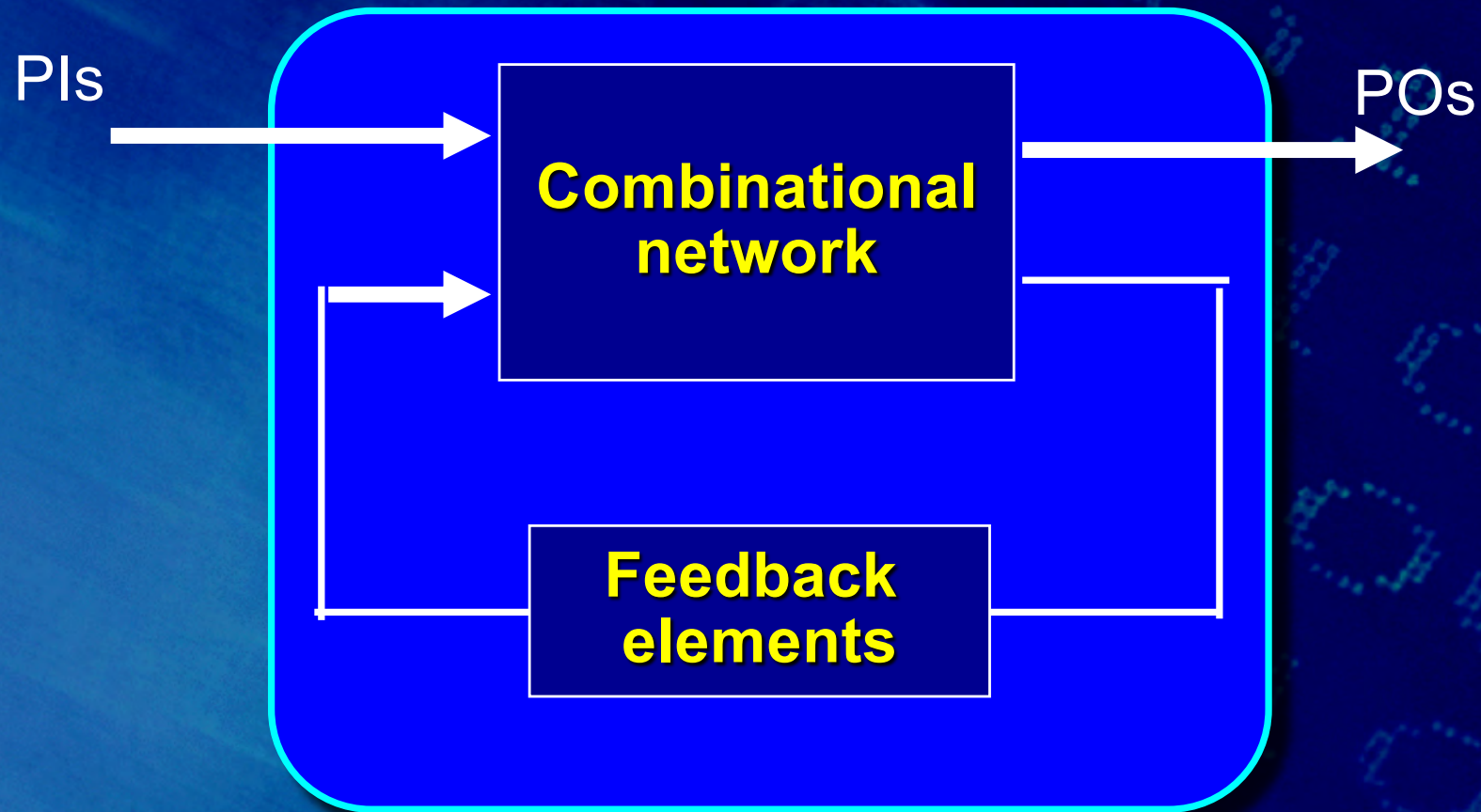


Sequential network classification

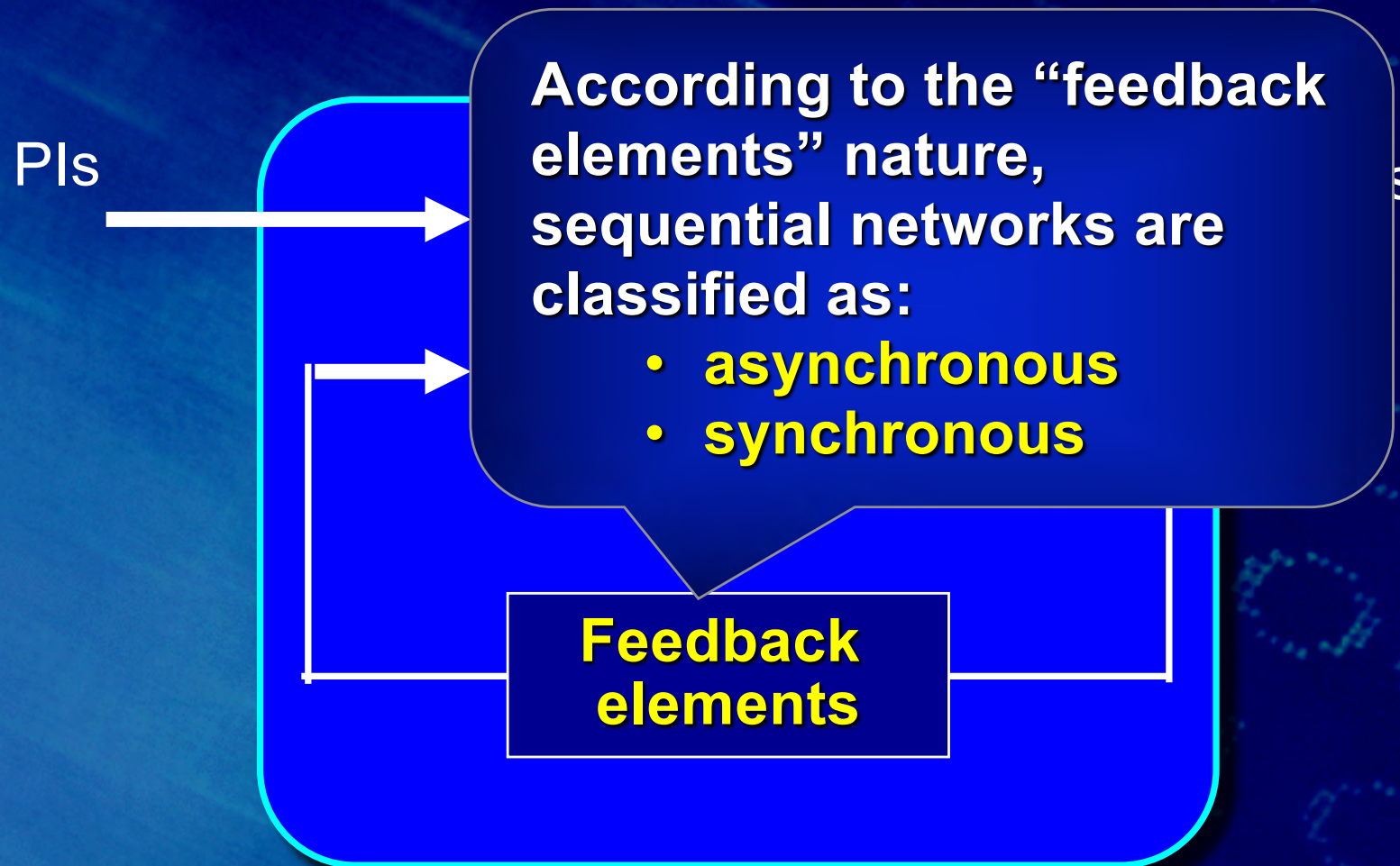


Asynchronous networks

- Each feedback element is just a wire
- The information flows through feedback elements is a continuum and not **synchronized** by any external event

Asynchronous network structure

 

Asynchronous network structure

 


Synchronous networks

- Each feedback is always performed via a particular device, named *Flip-Flop*
- Flip-Flop behavior is controlled and timed by an ad-hoc signal, usually referred to as *clock*
- The information flow through the feedback elements is thus “synchronized” by the *clock*

CLK

Flip-Flop behavior

 

Flip-Flop behavior




CLK

Flip-Flop behavior

D

Q

 


Clock

CLK



Input

D

 

CLK


Flip-Flop behavior

  

State register

- The set of Flip-Flops is often referred to as “**State Register**”, since it stores the network state variables.

Synchronous network structure

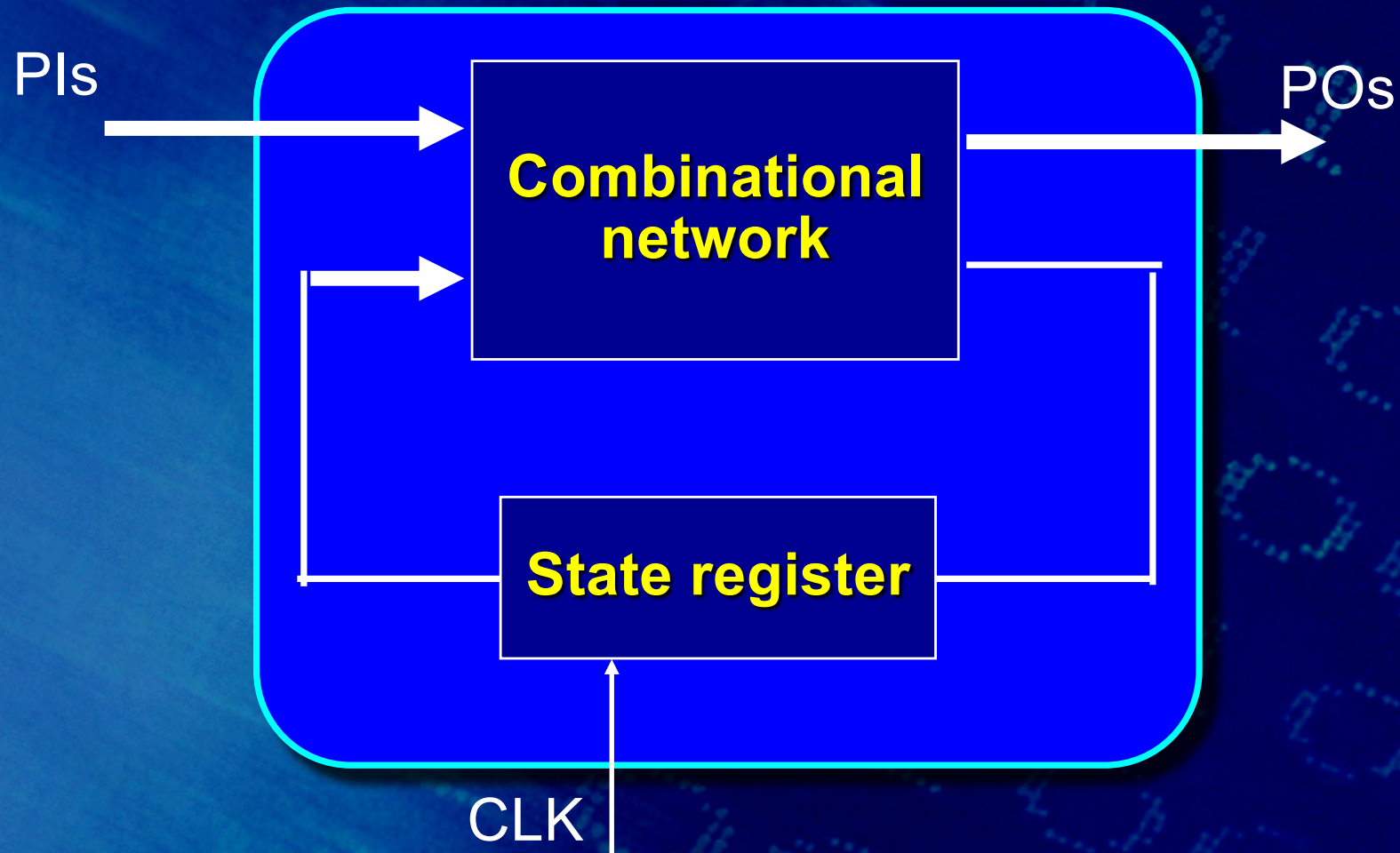

Finite State Machines


- Synchronous networks, being characterized by a finite # of flip-flops, and thus of states, are very often referred to as ***Finite State Machines*** (FSMs).

Any FSM, regardless its complexity,
MUST have:

- a particular control input signal, named **reset signal** (or simply **reset**) characterized by the highest priority
- a particular state, named **reset state**, in which the network moves whenever the reset signal is asserted.




Asynchronous reset

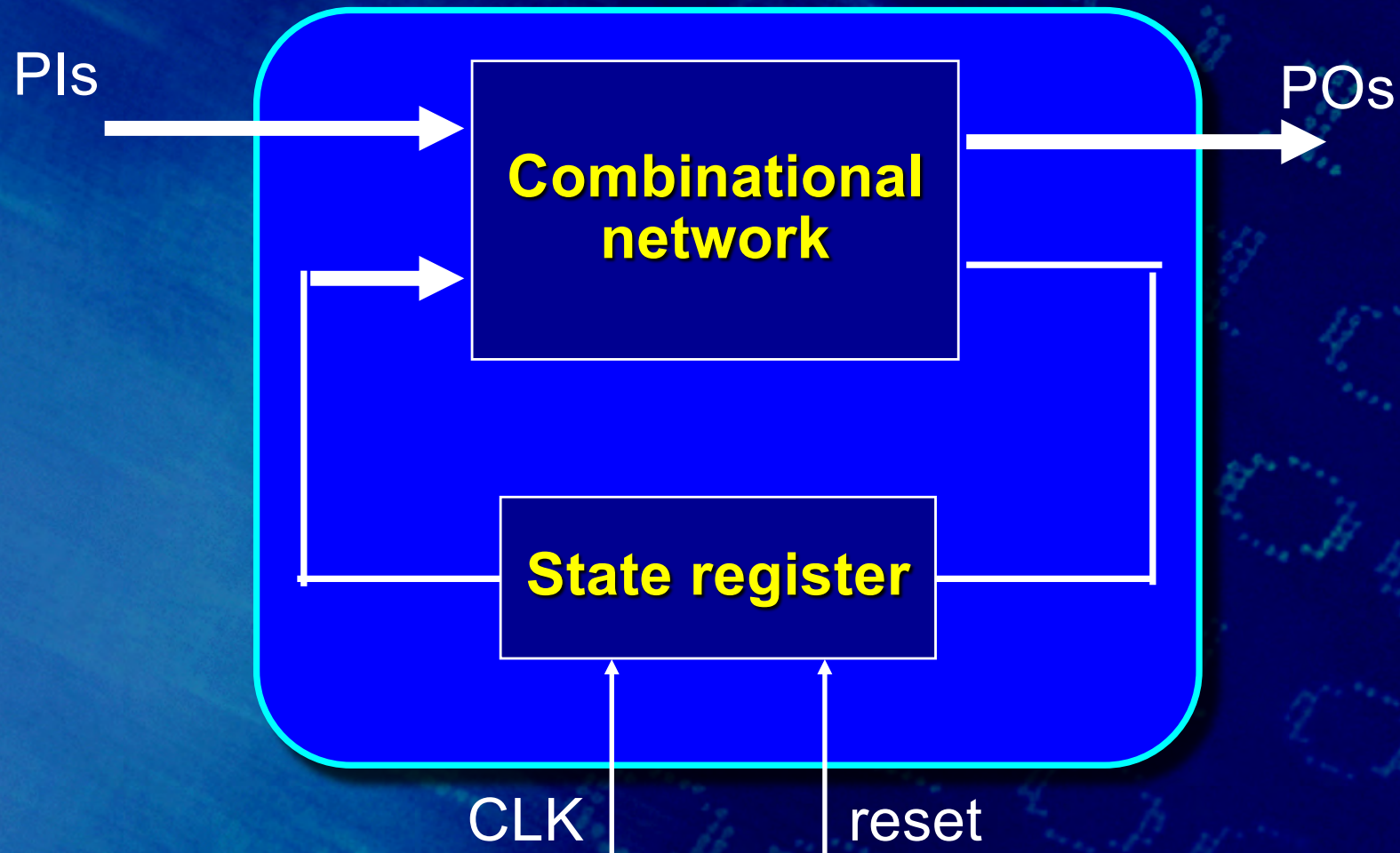


Outline


- Combinational vs. sequential networks
- Moore vs. Mealy machines
- I/O clustering


Combinational network splitting

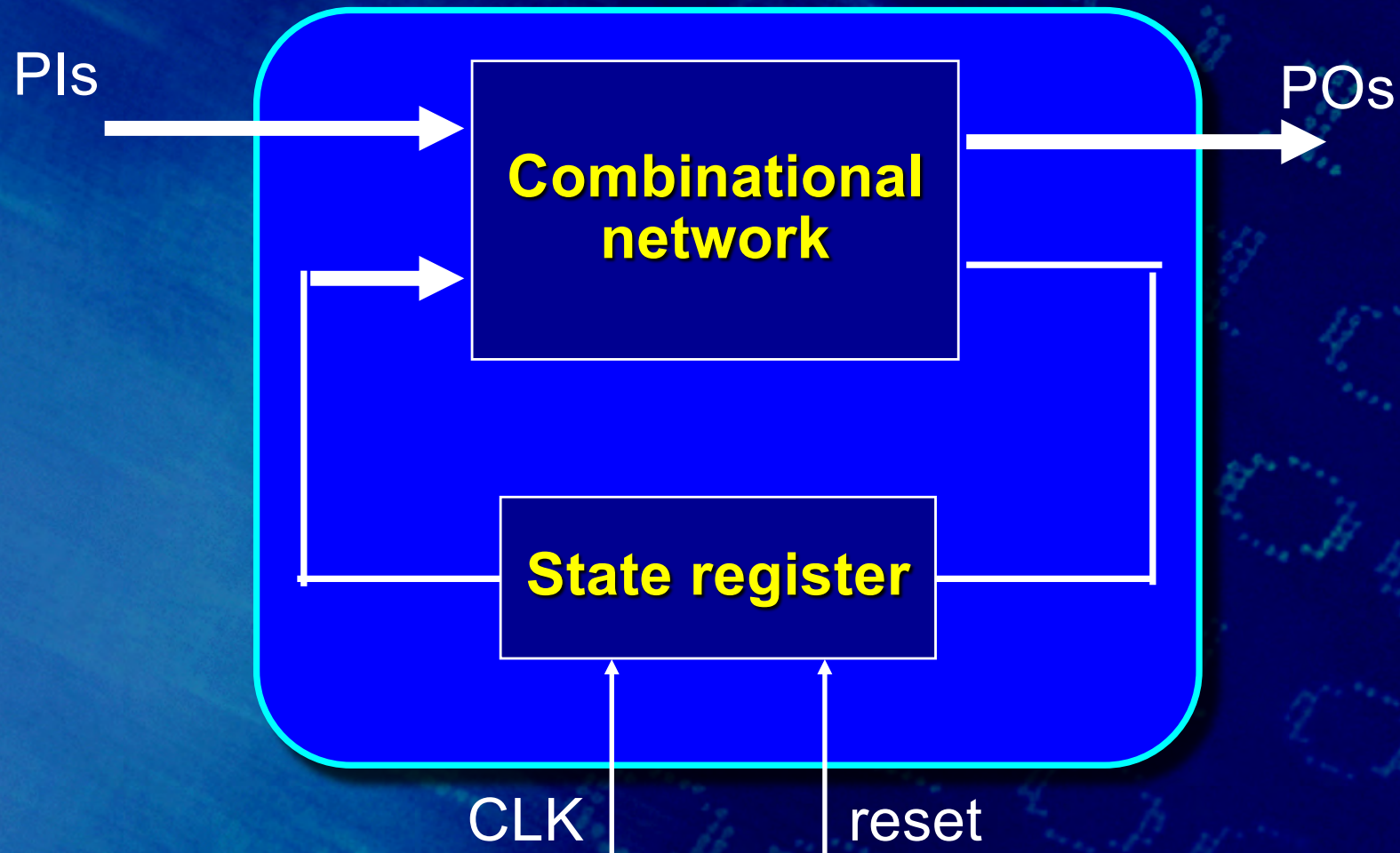

Combinational network splitting

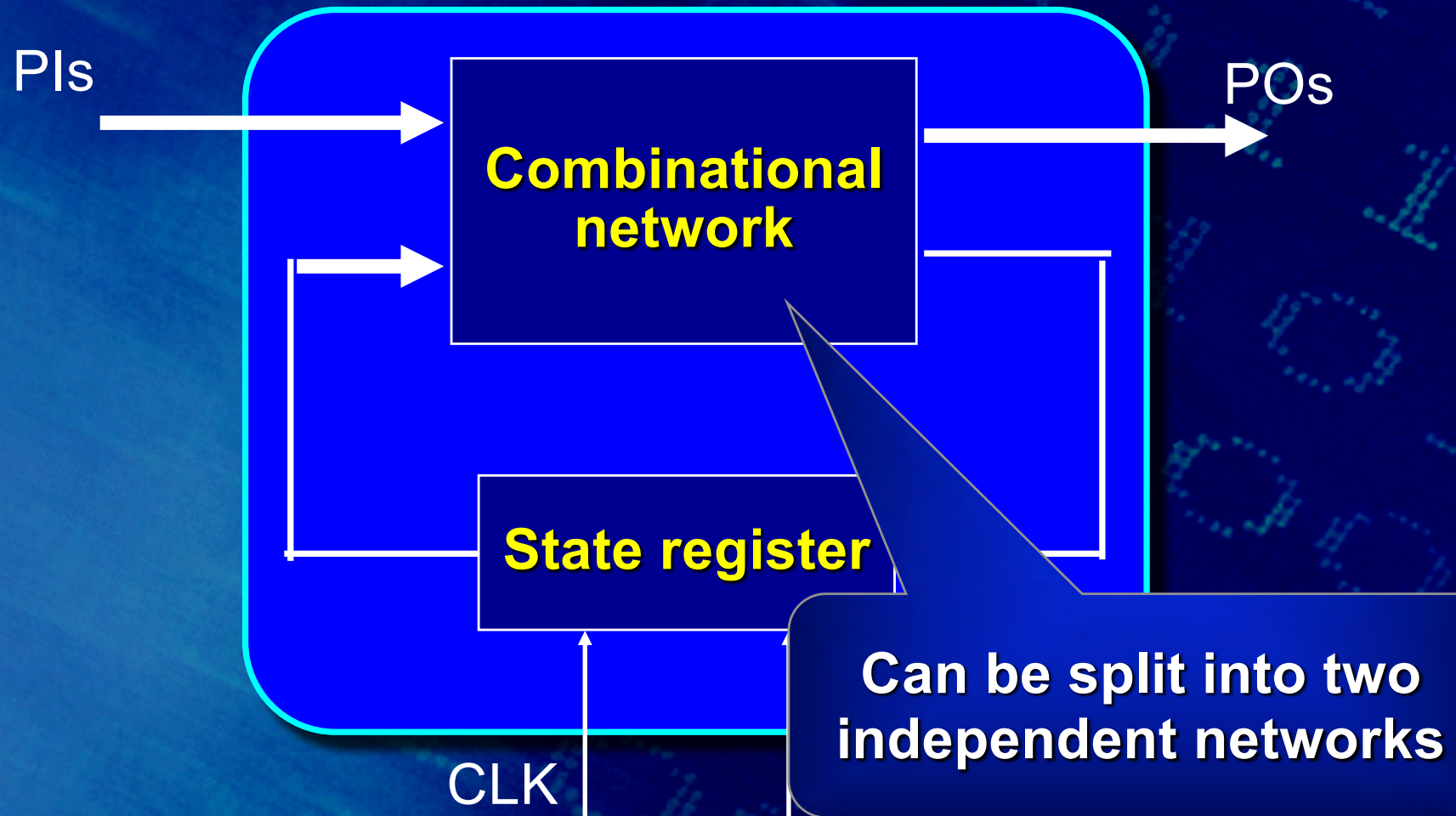

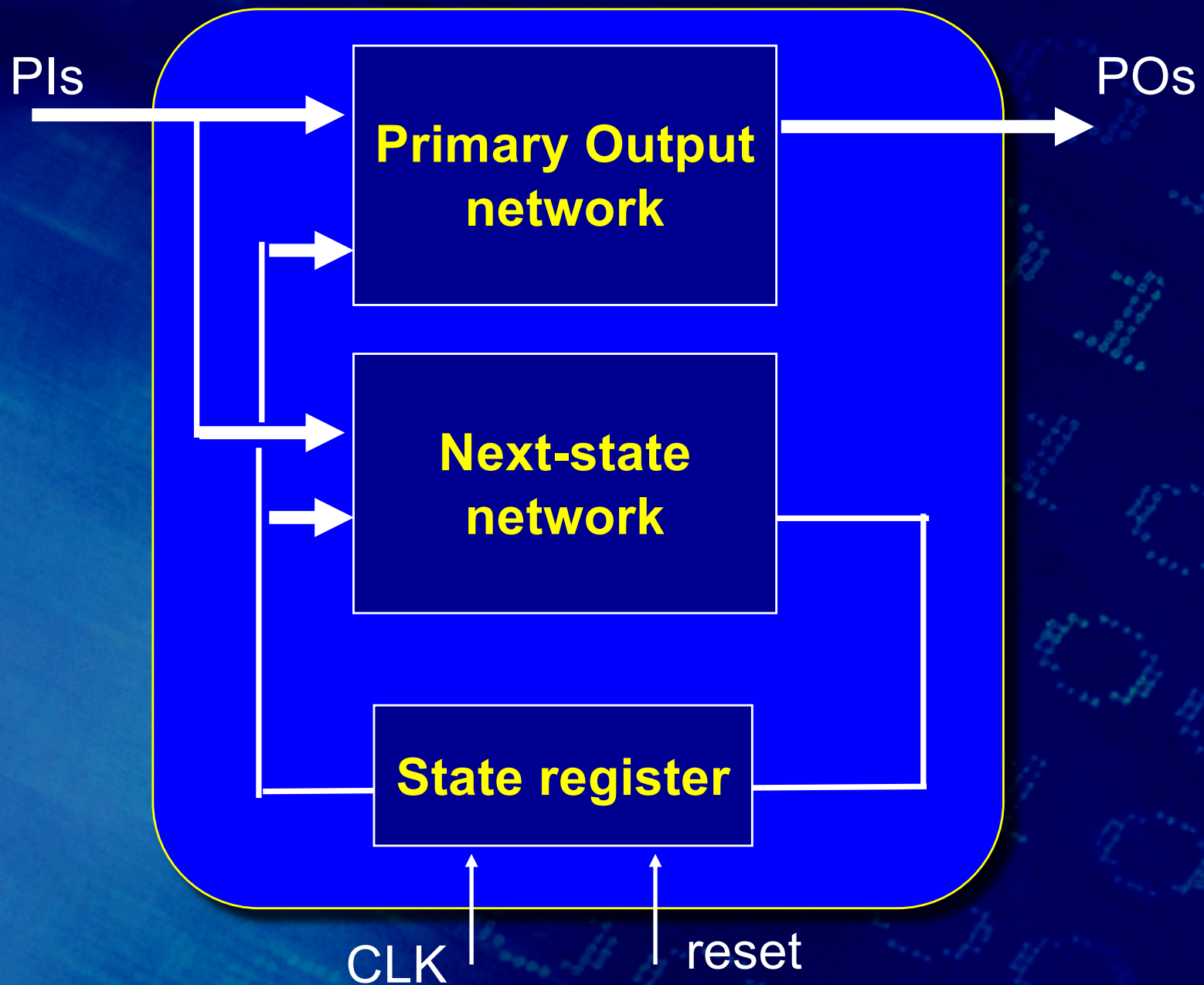

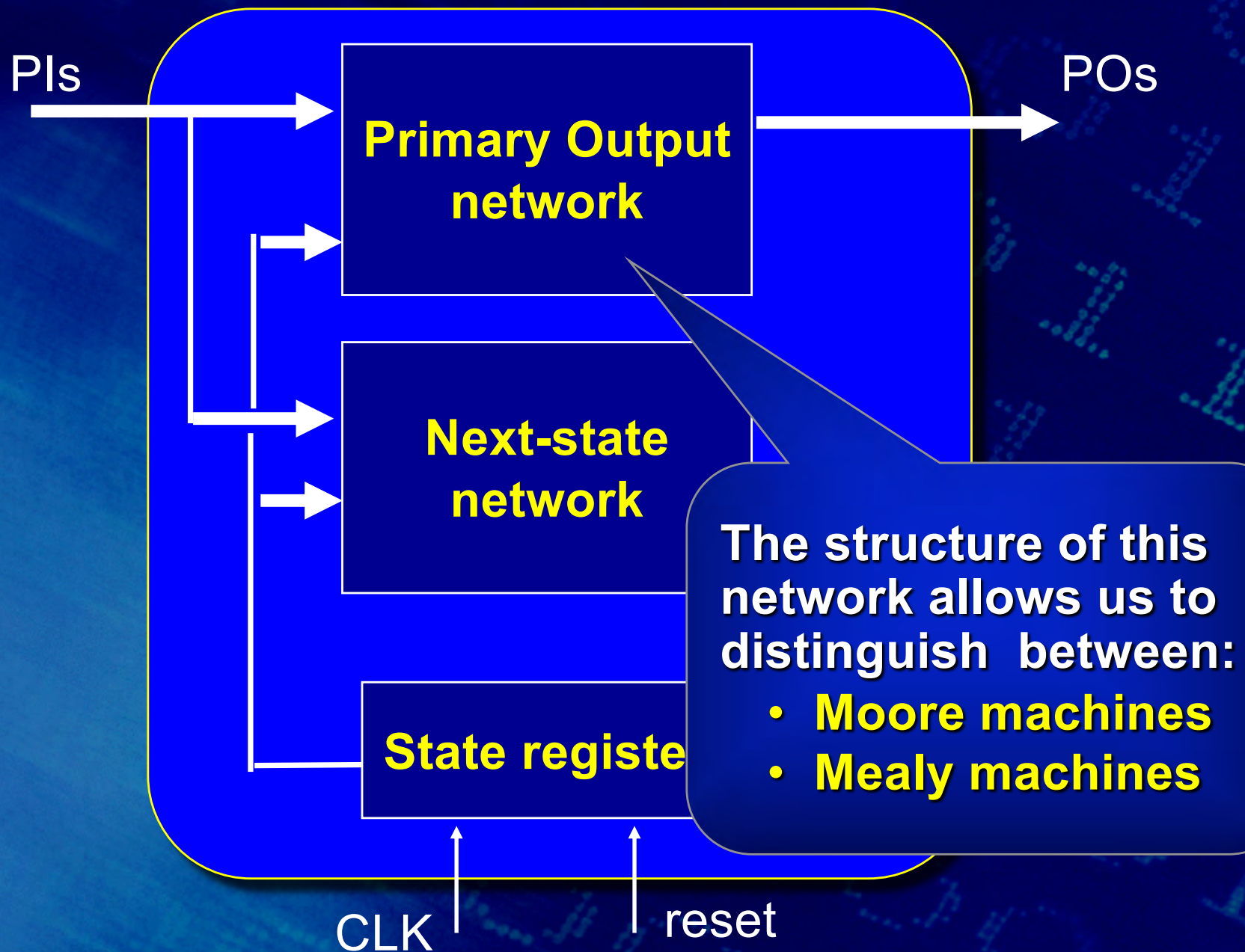


Moore machines

- POs depend on the present state value, only.



POs can change only when state changes.

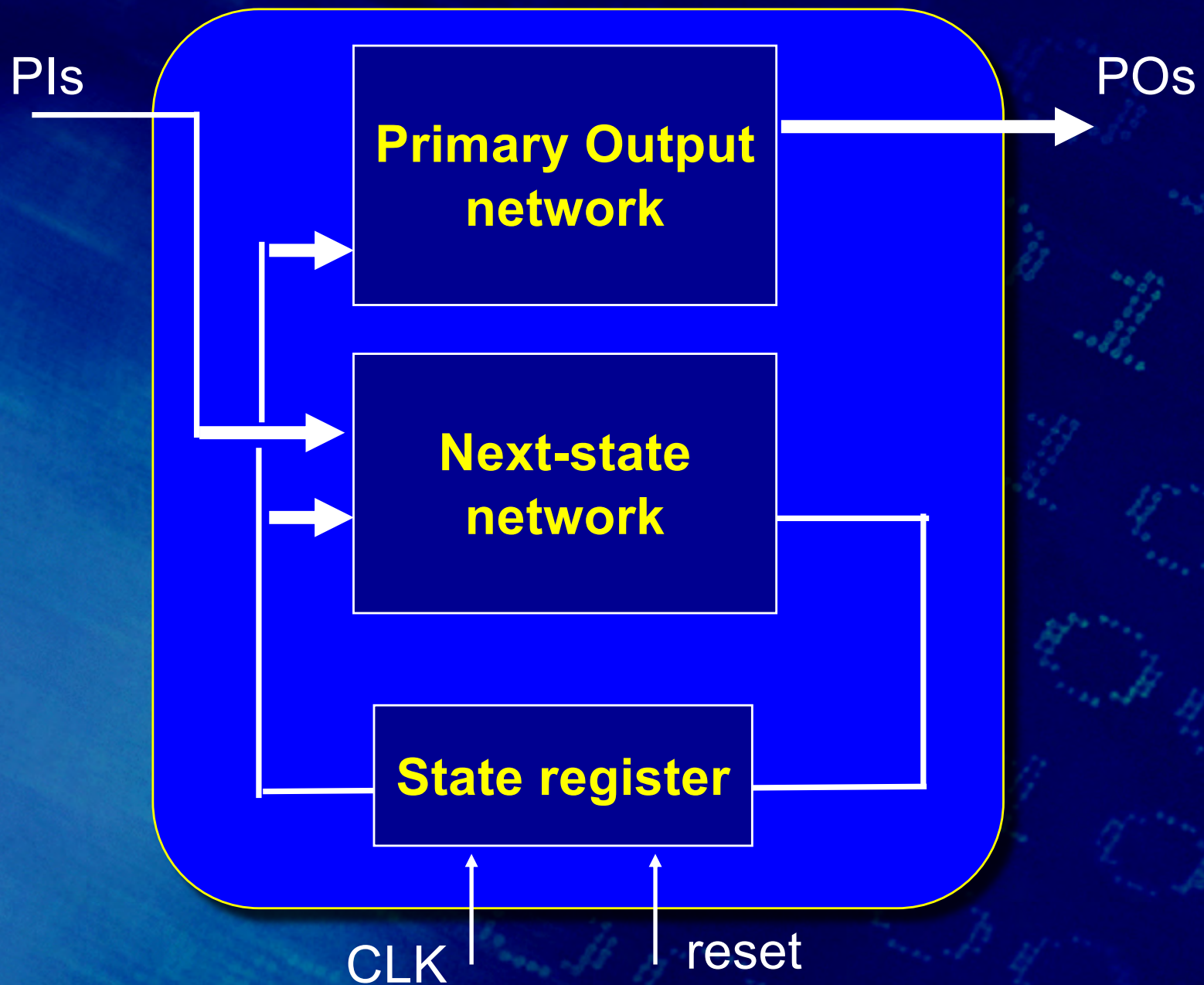



Mealy machines

- POs depend on both the present state value and the PIs values.




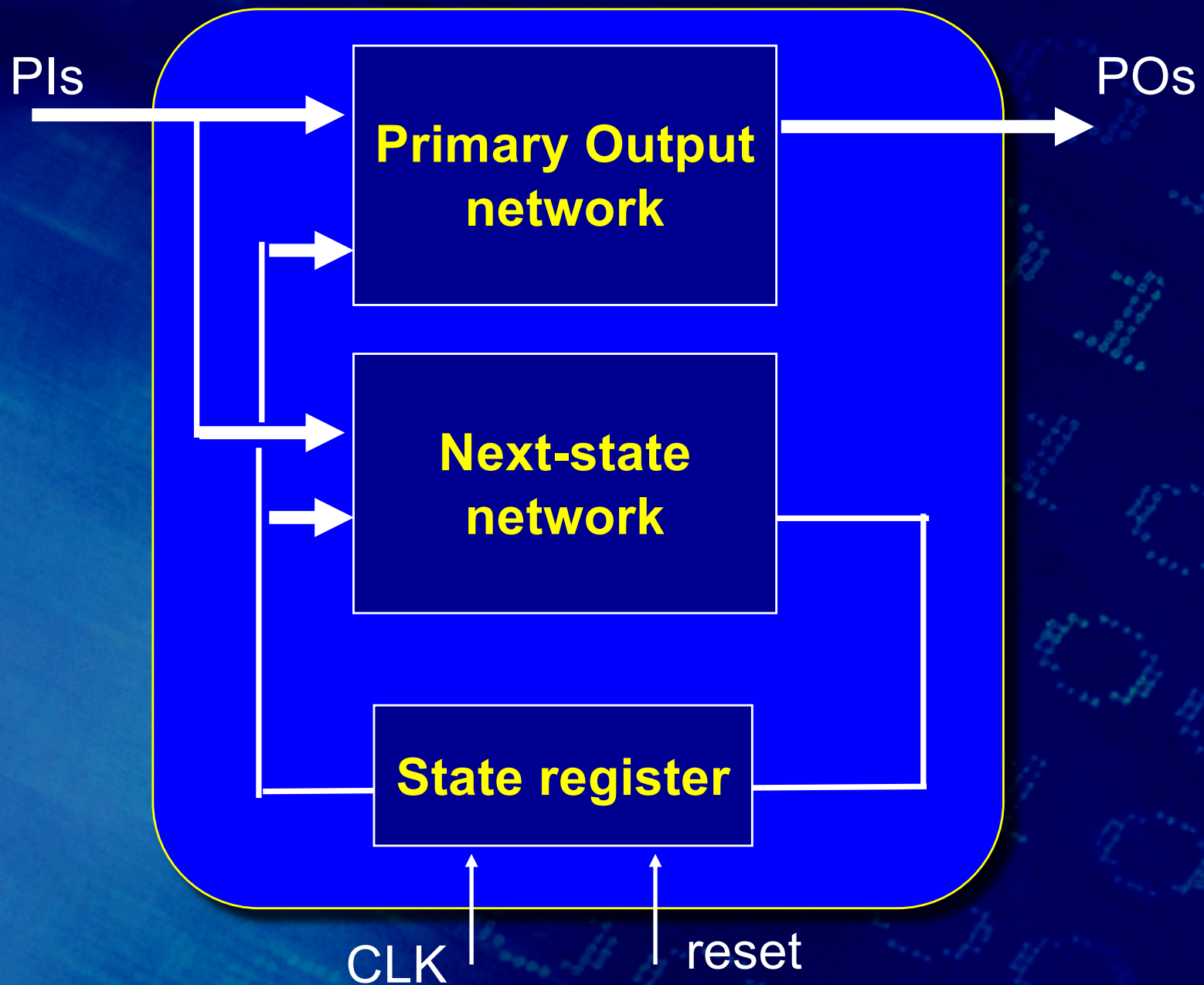POs can change not only when the state changes, but when PIs change, too.



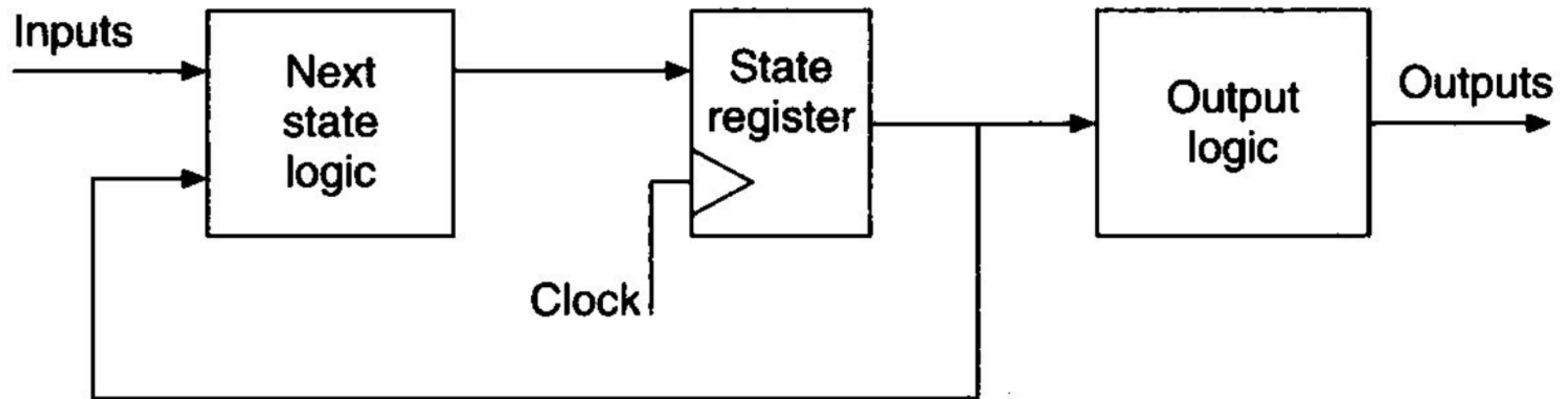

Moore machine

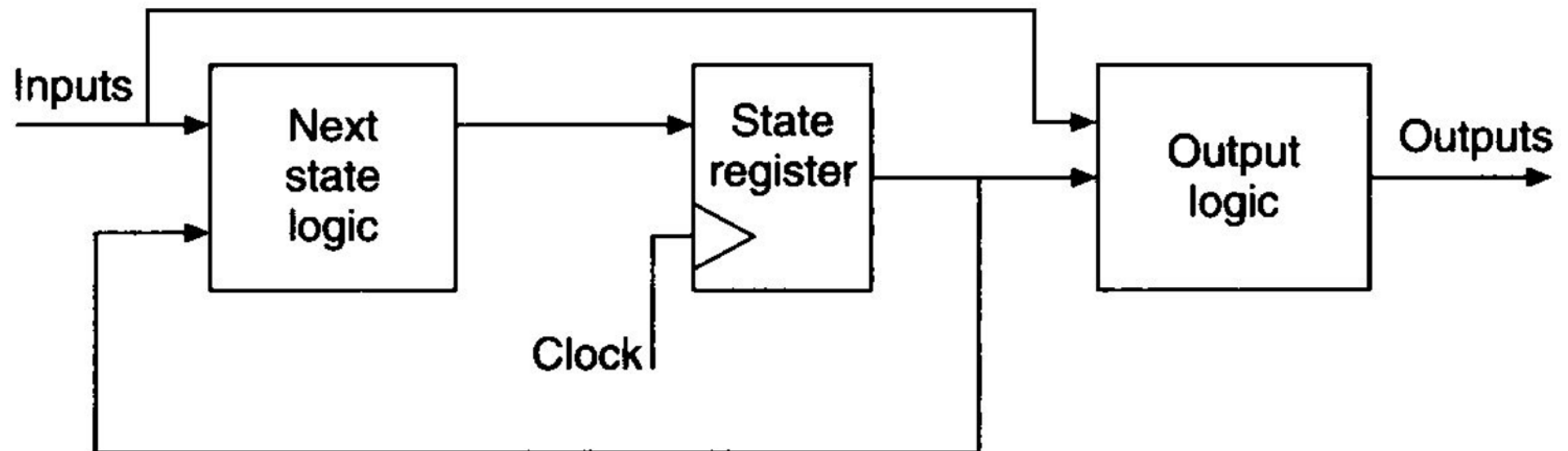

Mealy machine

Outline

- Combinational vs. sequential networks
- Moore vs. Mealy machines
- I/O clustering

System I/O signals

Timing Inputs

Data Inputs

Control Inputs

System

Data Outputs

Status Outputs

Timing Signals

Timing Inputs

Data Inputs

Control Inputs

System

Data Outputs

Status Outputs

They synchronize the overall behavior
of the network by:
sampling data and control inputs
updating data and control outputs


Edge vs. pulse triggering

- Sampling and updating can be triggered by
 - clock's raising or falling edges
 - clock's positive or negative pulses.


Edge triggering behavior

- The same clock edge samples the inputs and concurrently updates the outputs:
 - raising edge → *positive edge triggered*
 - falling edge → *negative edge triggered*


Positive edge triggered

 


Positive edge triggered

 


Positive edge triggered

 


Positive edge triggered

 


Positive edge triggered

 


Negative edge triggered

 


Negative edge triggered

 

Negative edge triggered

 

Negative edge triggered

 

Pulse triggering behavior

- **An edge of the clock samples the inputs values and the other edge updates the outputs**


Positive pulse triggered




Positive pulse triggered




Positive pulse triggered

 


Positive pulse triggered

 

Positive pulse triggered

 

Positive pulse triggered

 

Set-up & Hold Times

- **Sequential devices works properly iff some temporal constraints are satisfied**



Set-up time


The time interval t_s in
which data inputs
and control inputs
must be stable **before**
the clock event



Hold time

The time interval t_h in which data inputs and control inputs must be stable **after** the clock event

Set-up & Hold Times

 

Control Signals

Timing Inputs

They control the behavior of the network, by stating the operations to be performed

Data Inputs

Control Inputs

System

Data Outputs

Status Outputs

Control Inputs classification


- According to their asserting characteristics, Control Inputs are usually classified as:
 - ***Synchronous***
 - ***Asynchronous***

Control Inputs classification


- According to their asserting characteristics, Control Inputs are usually classified as:
 - *Synchronous*
 - ***Asynchronous***

When asserted, they are immediately active, regardless the clock.

Asynchronous reset

 

Asynchronous reset

 


Control Inputs classification


- According to their asserting characteristics, Control Inputs are usually classified as:
 - **Synchronous**
 - Asynchronous

When asserted, they become active at the next clock (edge or pulse), only


Synchronous reset

 

Synchronous reset

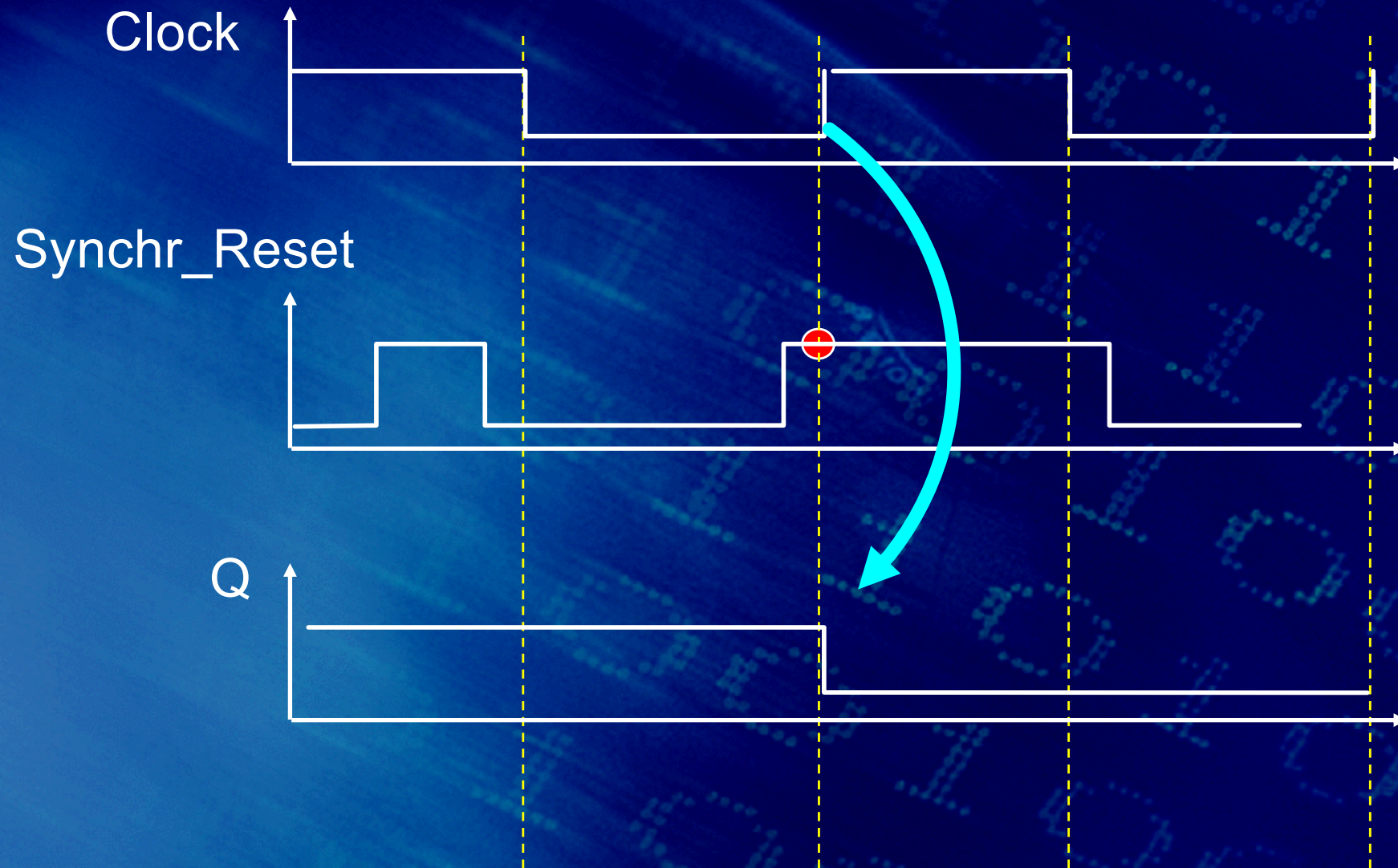

Enable

 

Малые Автюхи, Калининский район, Республики Беларусь

